

Computer Architecture

Ch. 5-4: Designing a Multiple Cycle Controller


Spring, 2005

Sao-Jie Chen (csj@cc.ee.ntu.edu.tw)


Review of a Multiple Cycle Implementation

- **The root of the single cycle processor's problems:**
 - The cycle time has to be long enough for the slowest instruction
- **Solution:**
 - Break the instruction into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
 - ⇒ Cycle time: time it takes to execute the longest step
 - ⇒ Keep all the steps to have similar length
 - This is the essence of the multiple cycle processor
- **The advantages of the multiple cycle processor:**
 - Cycle time is much shorter
 - Different instructions take different number of cycles to complete
 - ⇒ Load takes five cycles
 - ⇒ Jump only takes three cycles
 - Allows a functional unit to be used more than once per instruction

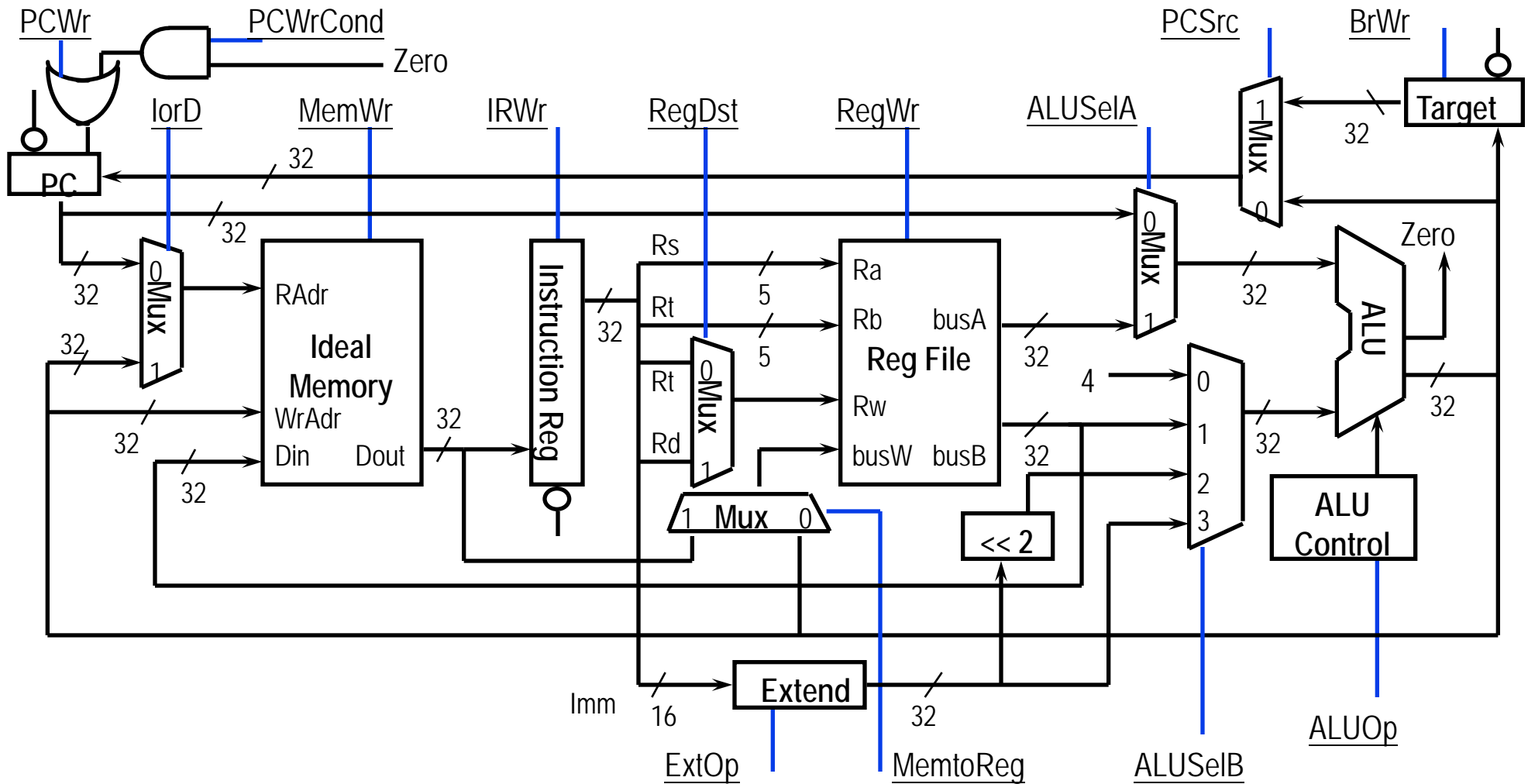Putting it all together: Multiple Cycle Datapath



Instruction Fetch Cycle: Overall Picture

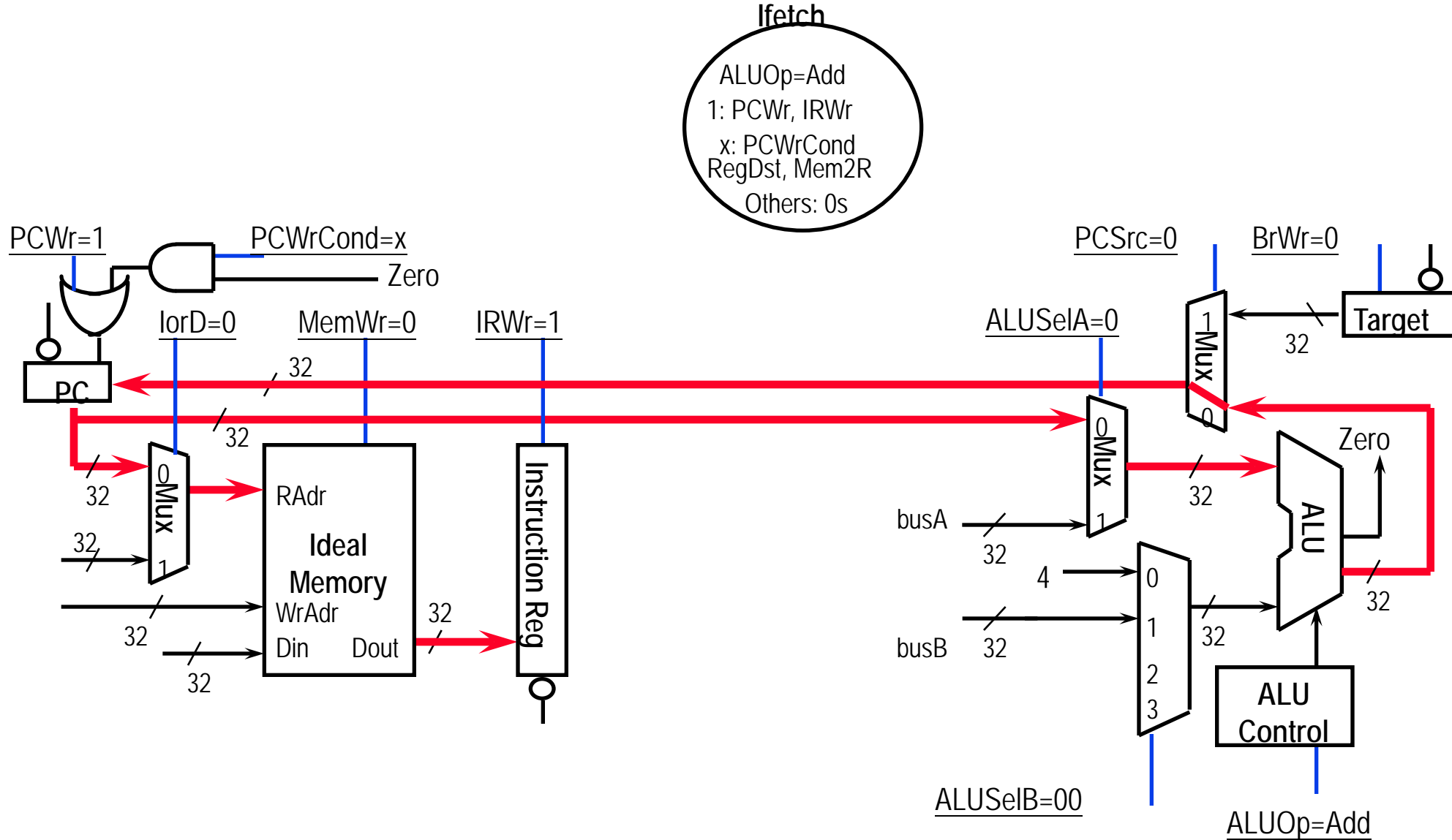


Register Fetch / Instruction Decode (Continued)

• $\text{busA} \leftarrow \text{Reg}[\text{rs}] ; \text{busB} \leftarrow \text{Reg}[\text{rt}] ;$

$\text{Target} \leftarrow \text{PC} + \text{SignExt}(\text{Imm16}) * 4$


Rfetch/Decode

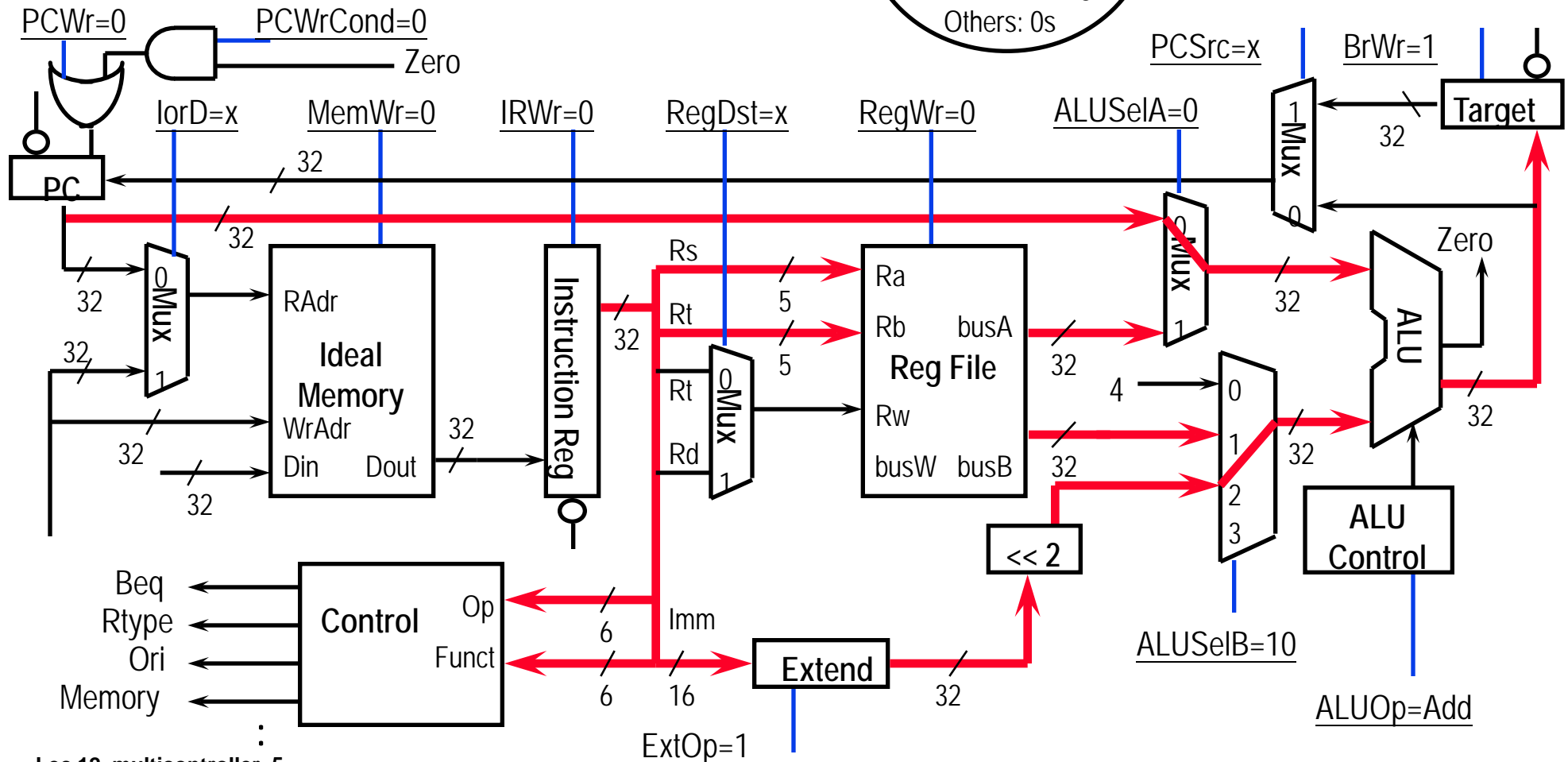ALUOp=Add
1: BrWr, ExtOp
ALUSelB=10
x: RegDst, PCSrc
lorD, MemtoReg
Others: 0s




R-type Execution

- **ALU Output <- busA op busB**

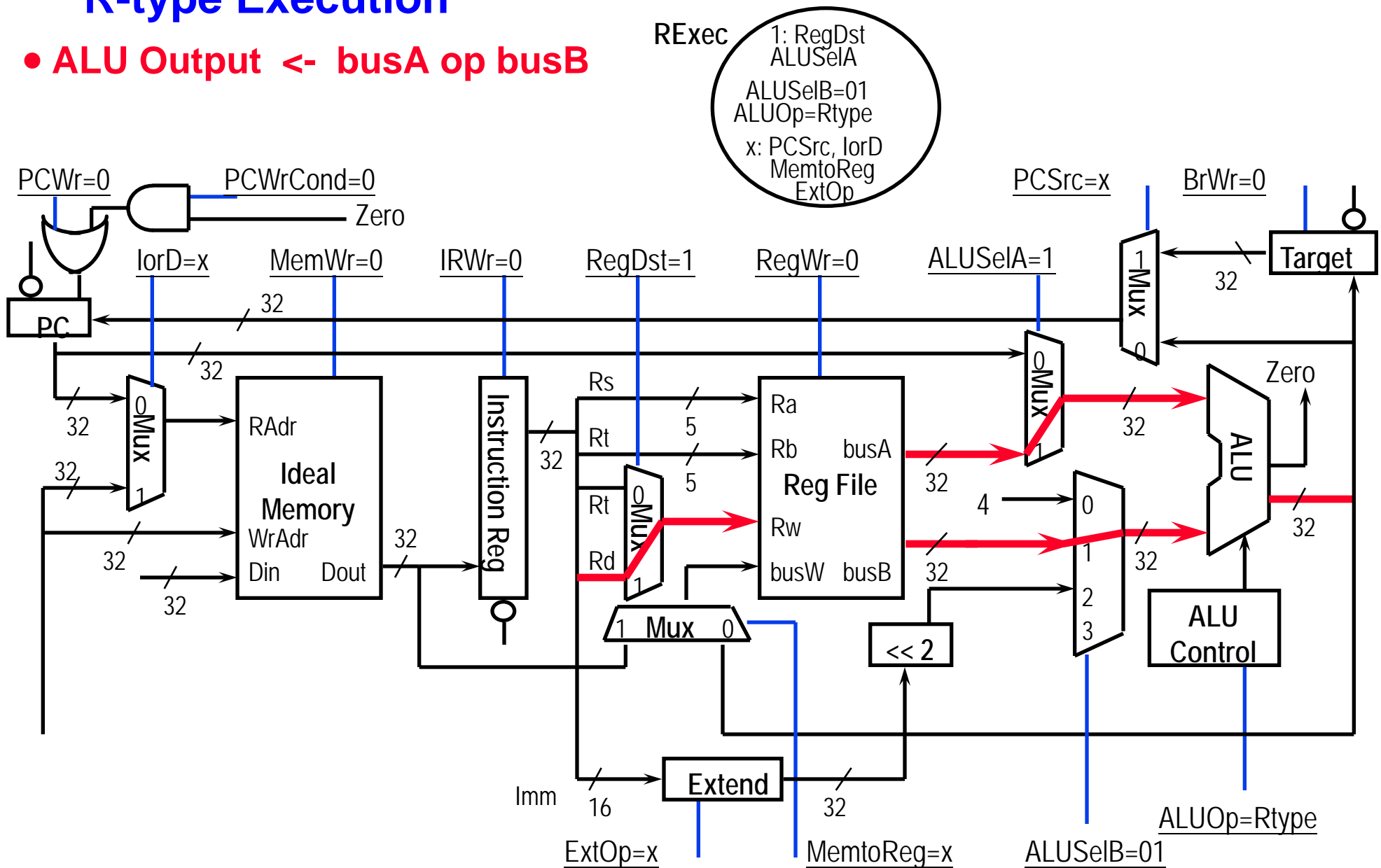

R-type Completion

- $R[rd] \leftarrow \text{ALU Output}$

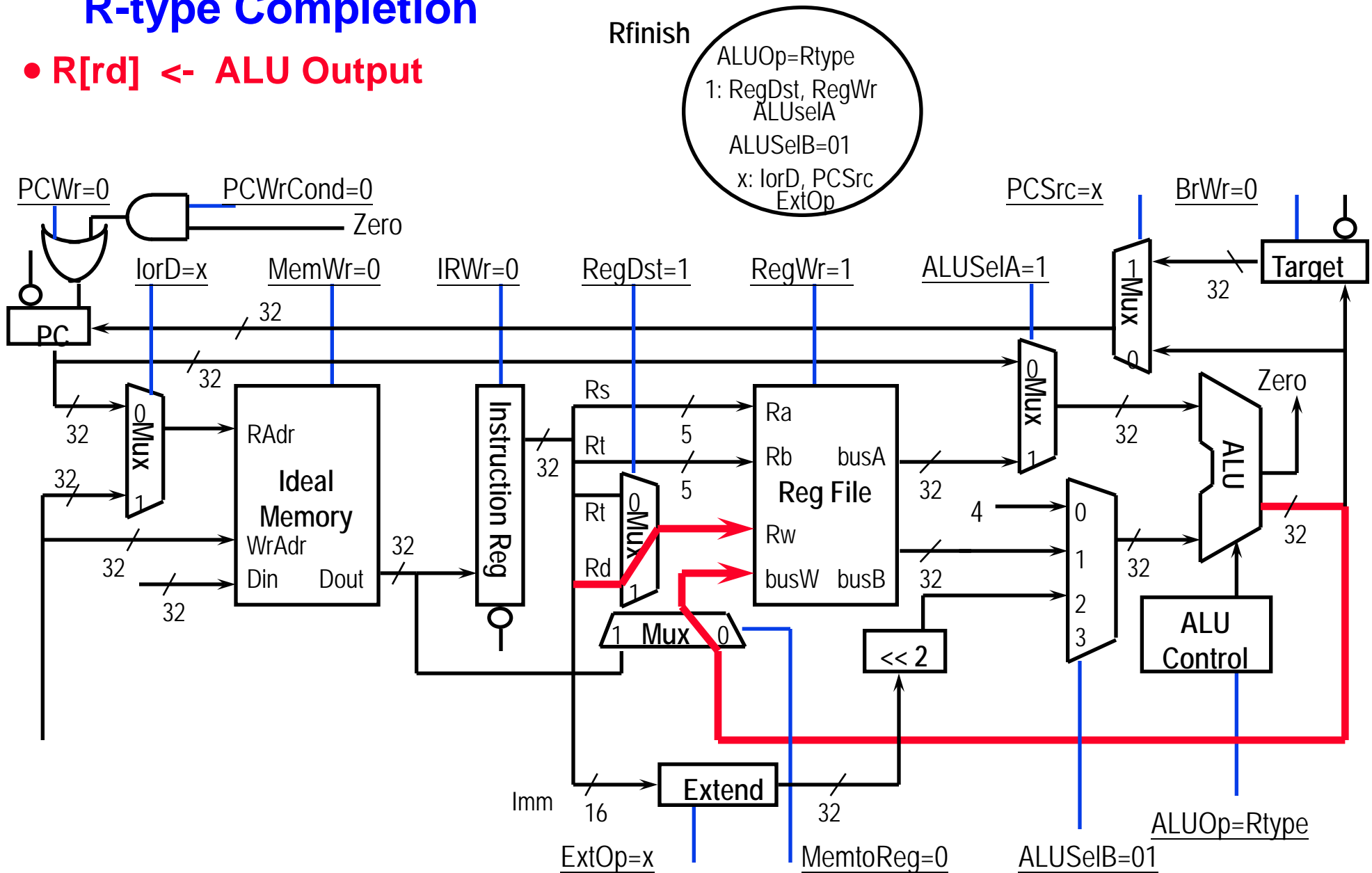

Overview of Next Two Lectures


- Control may be designed using one of several initial representations. The choice of sequence control, and how logic is represented, can then be determined independently; the control can then be implemented with one of several methods using a structured logic technique.

Initial Representation


Sequencing Control
counter

Logic Representation

Implementation Technique

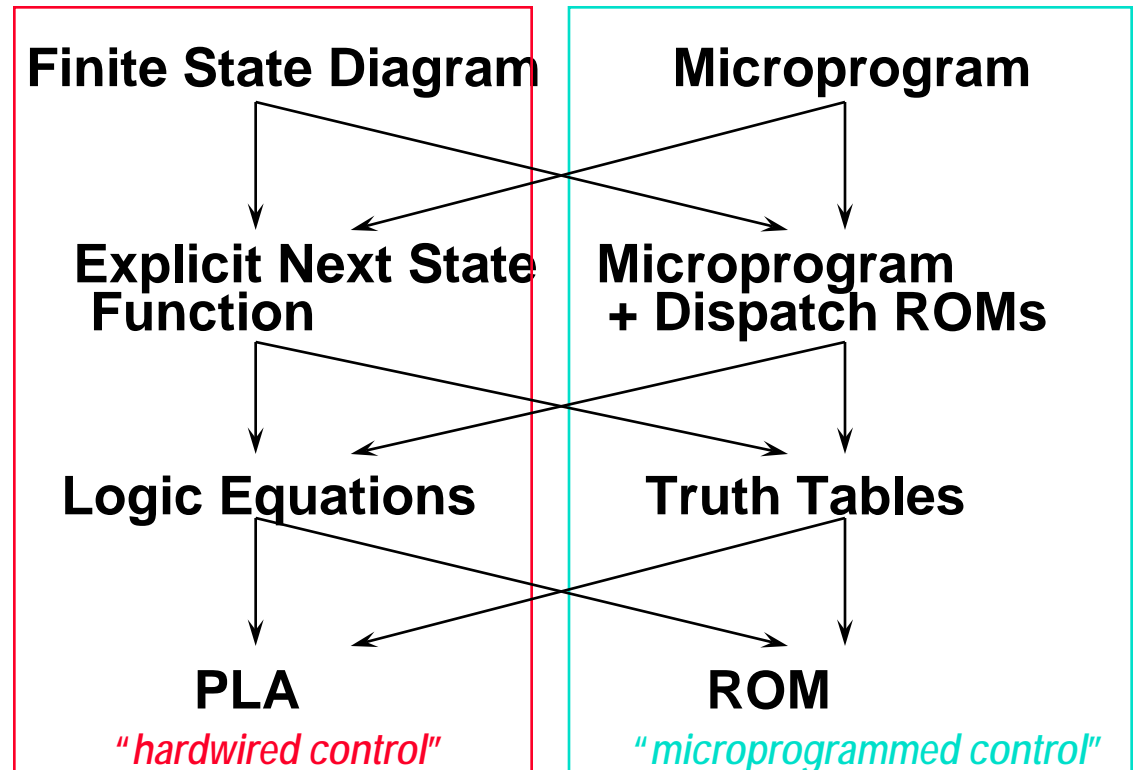

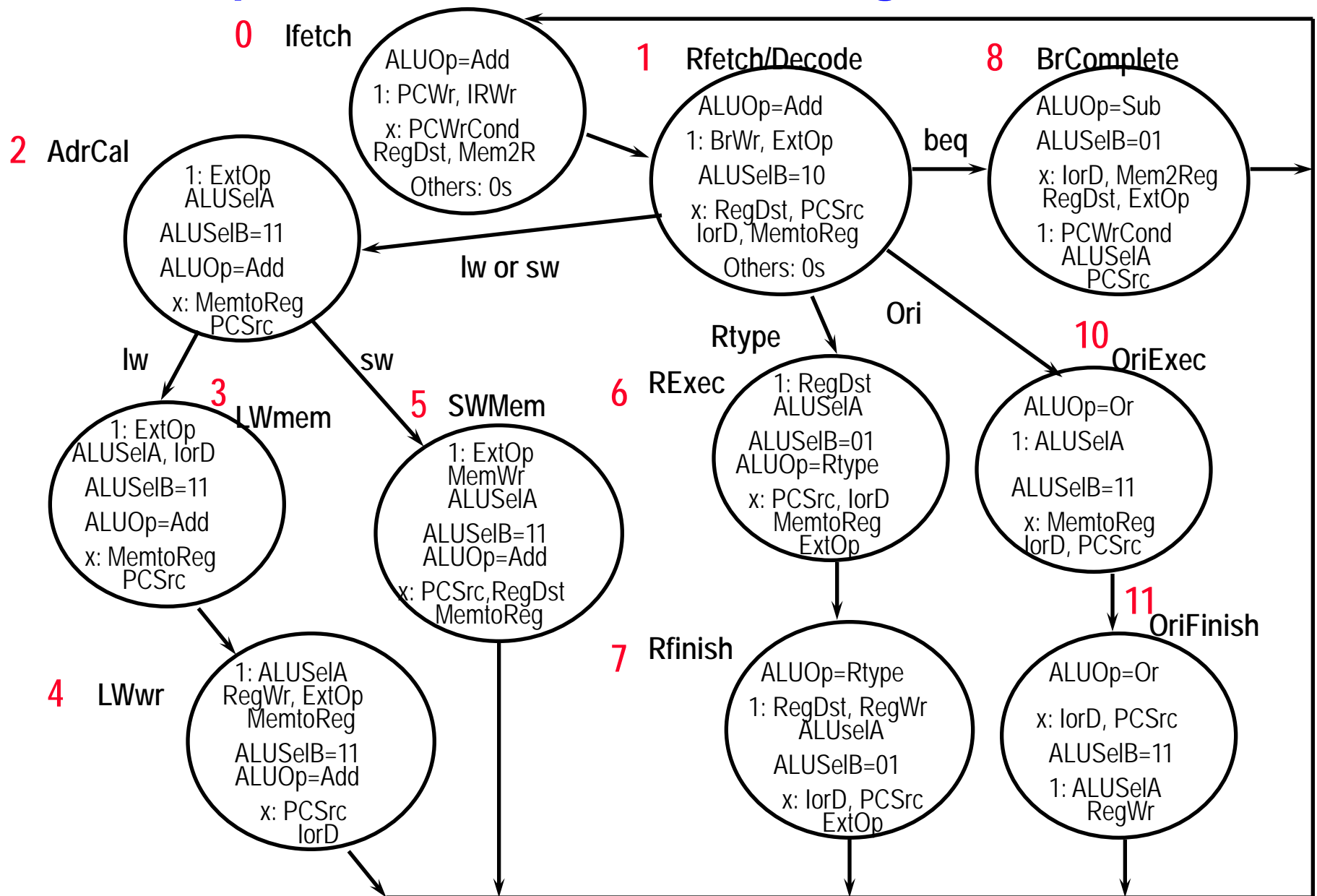
Initial Representation: Finite State Diagram



Review: Finite State Machines

- **Finite state machines:**

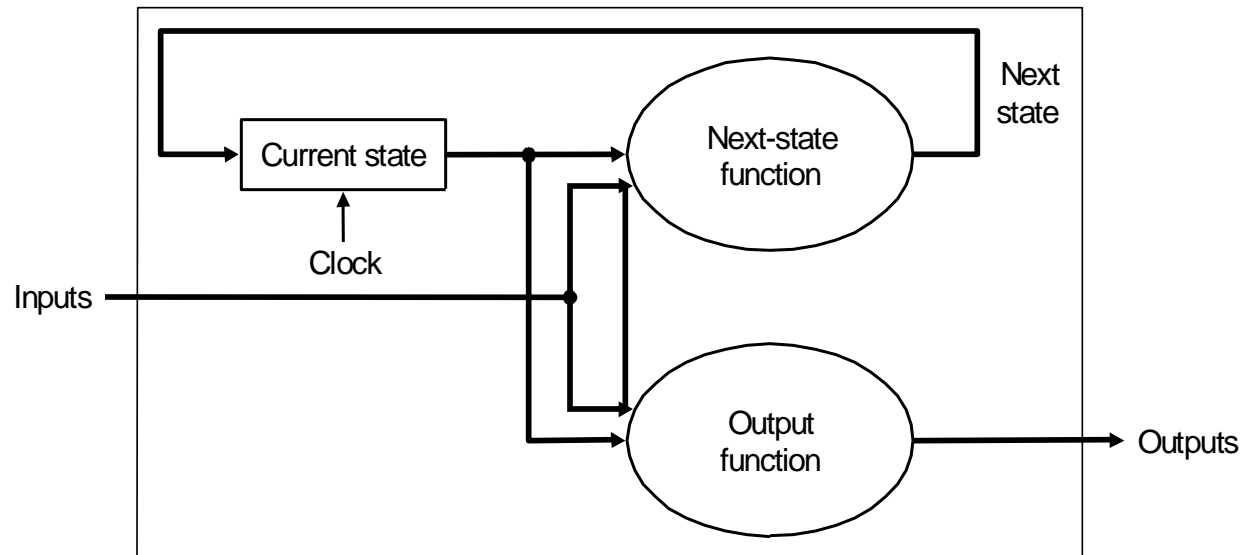
- a set of states and internal storage
- next state function (determined by current state and the input)
- output function (determined by current state and possibly input)




- **We'll use a Moore machine (output based only on current state)**

Finite State Machine for Control

- Implementation:

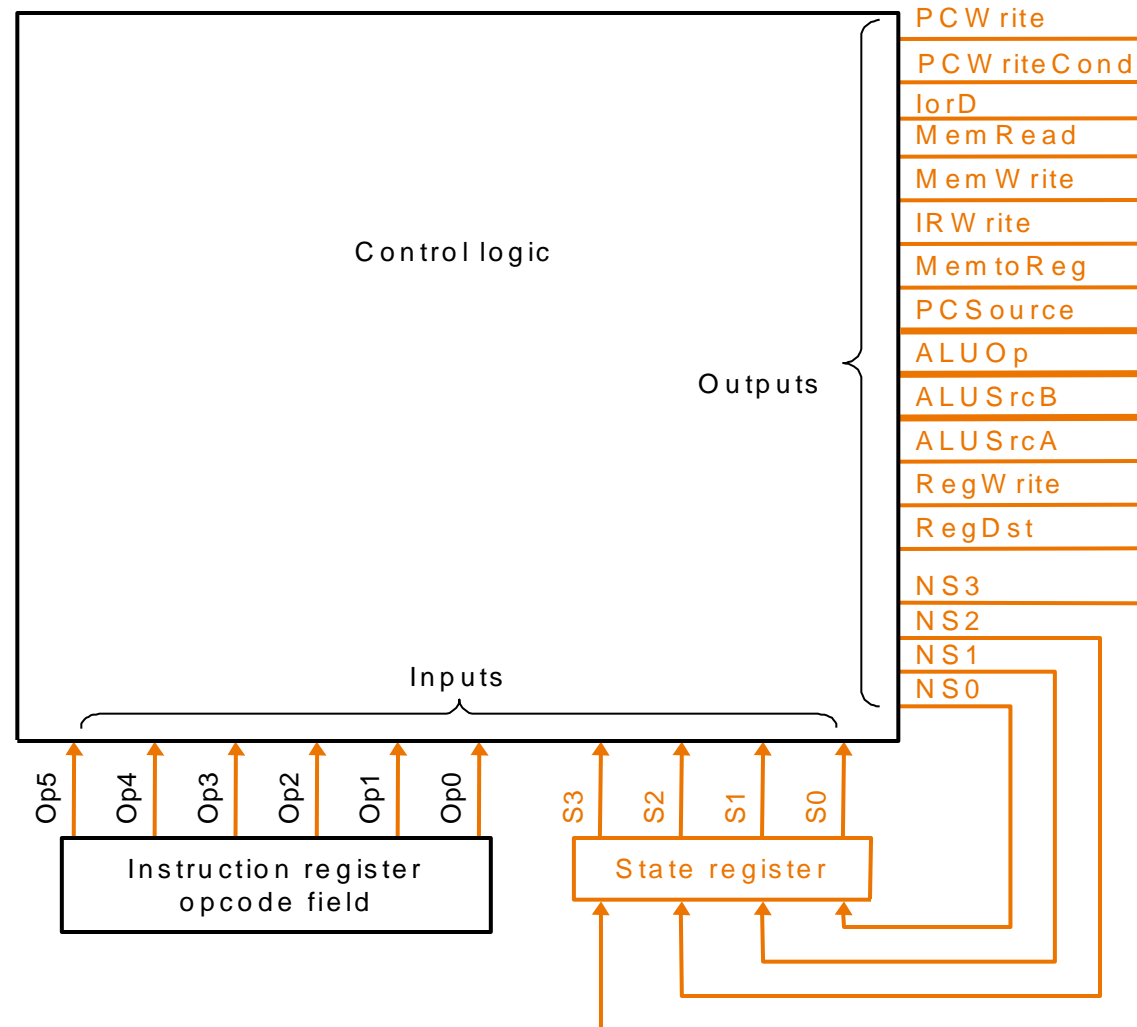

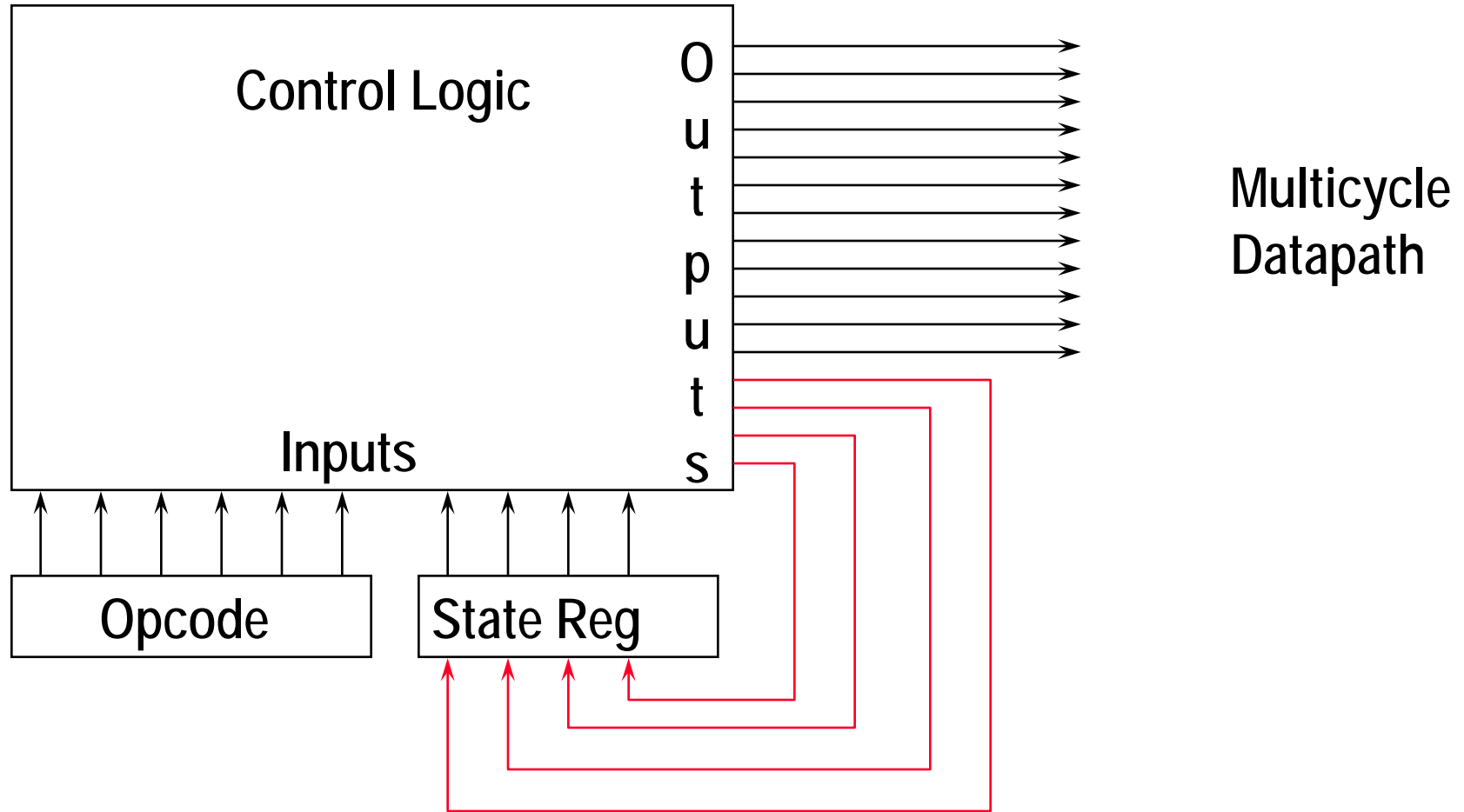Sequencing Control: Explicit Next State Function



- Next state number is encoded just like datapath controls

Logic Representative: Logic Equations

- Next state from current state

- State 0 -> State 1
- State 1 -> S2,S6,S8,S9,S10
- State 2 -> _____
- State 3 -> _____
- State 4 -> State 0
- State 5 -> State 0
- State 6 -> State 7
- State 7 -> State 0
- State 8 -> State 0
- State 9 -> State 0
- State 10 -> State 11
- State 11 -> State 0

Alternatively,
prior state & condition

S4, S5, S7, S8, S9, S11 -> State 0

_____ -> State 1

_____ -> State 2

_____ -> State 3

_____ -> State 4

State 2 & op = sw -> State 5

_____ -> State 6

State 6 -> State 7

_____ -> State 8

State 1 & op = jmp -> State 9

_____ -> State 10

State 10 -> State 11

Logic Representative: Logic Equations

- Next state from current state

- State 0 -> State1
- State 1 -> S2,S6,S8,S9,S10
- State 2 -> State 3 & State 5
- State 3 -> State 4
- State 4 -> State 0
- State 5 -> State 0
- State 6 -> State 7
- State 7 -> State 0
- State 8 -> State 0
- State 9 -> State 0
- State 10 -> State 11
- State 11 -> State 0

Alternatively,
prior state & condition

S4, S5, S7, S8, S9, S11 -> State0

State 0 -> State 1

State 1 & op = lw | sw -> State 2

State 2 & op = lw -> State 3

State 3 -> State 4

State 2 & op = sw -> State 5

State 1 & op = R-type -> State 6

State 6 -> State 7

State 1 & op = beq -> State 8


State 1 & op = jmp -> State 9

State 1 & op = ori -> State 10

State 10 -> State 11

Implementation Technique: Programmed Logic Arrays

 
- Each output line the logical OR of logical AND of input lines or their complement: AND minterms specified in top AND plane, OR sums specified in bottom OR plane



Implementation Technique: Programmed Logic Arrays

State 1 & op = lw | sw -> State 2


lw sw R ori beq jmp lw sw

 

Implementation Technique: Programmed Logic Arrays

State 2 & op = lw | sw -> State 3 | Sate 5



lw sw R ori beq jmp lw sw

 

State 2 -> State 3 & State 5 (ROM2)


Implementation Technique: Programmed Logic Arrays

  State 3 -> State 4, S6 -> S7, S10 -> S11,



Implementation Technique: Programmed Logic Arrays

 - Each output line the logical OR of logical AND of input lines or their complement: AND minterms specified in top AND plane, OR sums specified in bottom OR plane




Multicycle Control

- **Given numbers of FSM, can determine next state as function of inputs, including current state**
- **Turn these into Boolean equations for each bit of the next state lines**
- **Can implement easily using PLA**
- **What if many more states, many more conditions?**
- **What if need to add a state?**

PLA Implementation

 - If I picked a horizontal or vertical line could you explain it?



Next Iteration: Using Sequencer for Next State

- Before Explicit Next State: Next try variation 1 step from right hand side
- Few sequential states in small FSM: suppose added floating point?
- Still need to go to non-sequential states: e.g., state 1 \Rightarrow 2,6,8,9,10

Initial Representation

Sequencing Control
counter

Logic Representation

Implementation Technique

Finite State Diagram

Explicit Next State
Function

Logic Equations

PLA

"hardwired control"

Microprogram


Microprogram
+ Dispatch ROMs

Truth Tables


ROM

"microprogrammed control"

Sequencer-based control unit

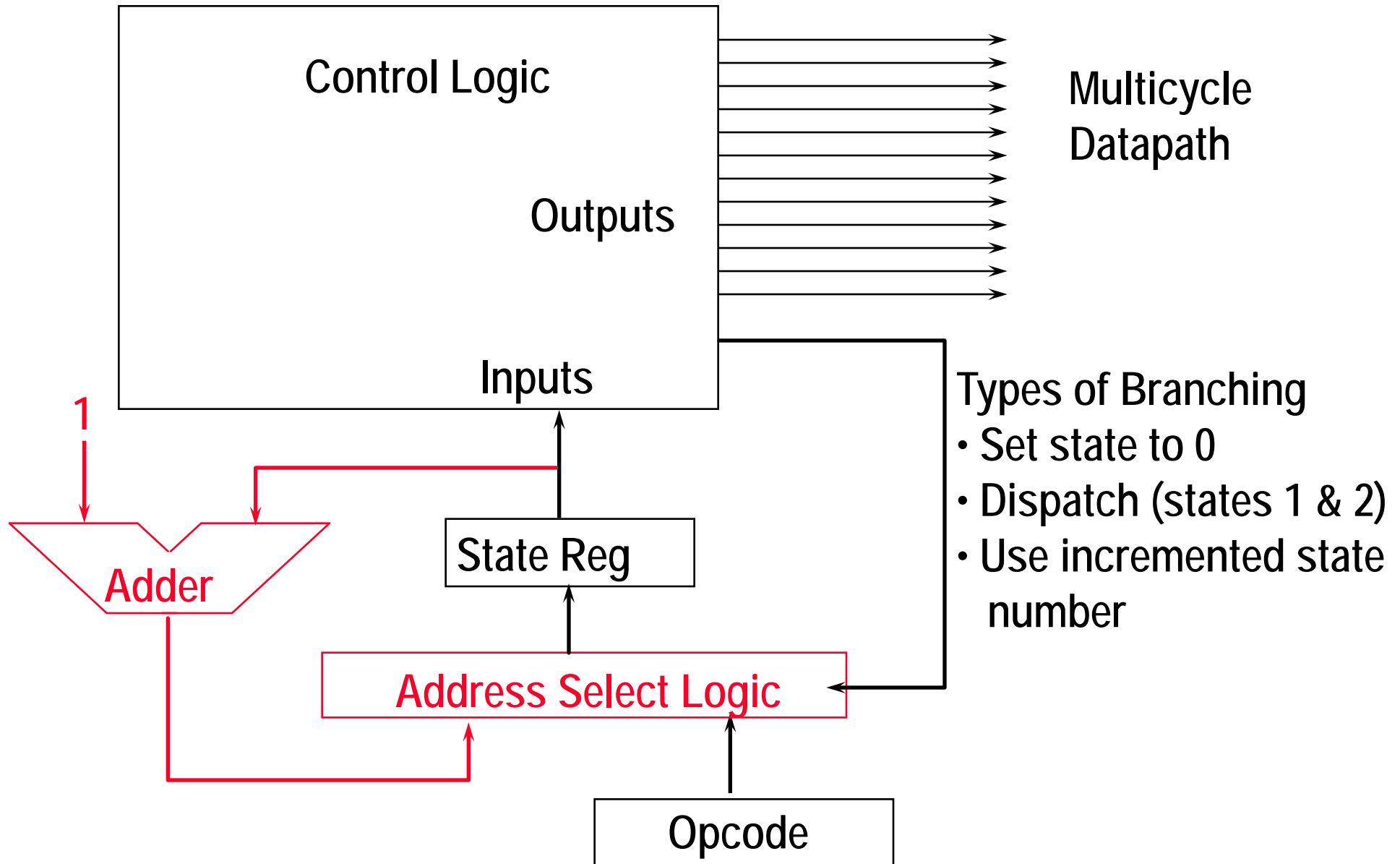

Sequencer-based control unit details

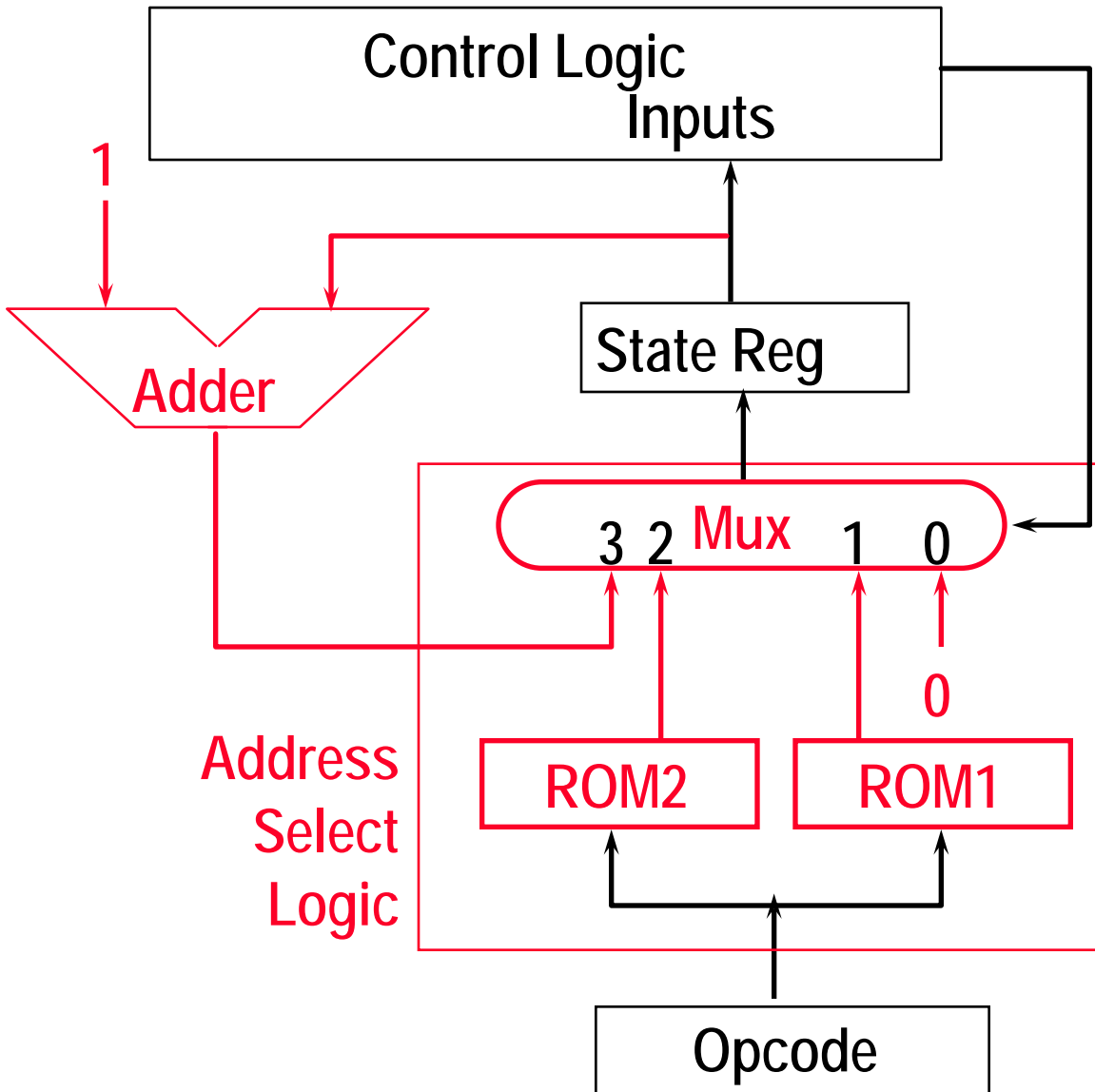

Dispatch ROM 1


<i>Op</i>	<i>Name</i>	<i>State</i>
000000	Rtype	0110
000010	jmp	1001
000100	beq	1000
001011	ori	1010
100011	lw	0010
101011	sw	0010

Dispatch ROM 2

<i>Op</i>	<i>Name</i>	<i>State</i>
100011	lw	0011
101011	sw	0101

ROM Implementation

 - **ROM = "Read Only Memory"**
 - values of memory locations are fixed ahead of time
- **A ROM can be used to implement a truth table**
 - if the address is m -bits, we can address 2^m entries in the ROM.
 - our outputs are the bits of data that the address points to.



0	0	0	0	0	0	1	1
0	0	1	1	1	0	0	0
0	1	0	1	1	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	0	0	0	0	1
1	1	0	0	1	1	0	0
1	1	1	0	1	1	1	1

m is the "height", and n is the "width"

Truth Table for the 16 Datapath Control Outputs (Fig. D.3.6)

Outputs	Input values (S[3–0])									
	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
PCWrite	1	0	0	0	0	0	0	0	0	1
PCWriteCond	0	0	0	0	0	0	0	0	1	0
lorD	0	0	0	1	0	1	0	0	0	0
MemRead	1	0	0	1	0	0	0	0	0	0
MemWrite	0	0	0	0	0	1	0	0	0	0
IRWrite	1	0	0	0	0	0	0	0	0	0
MemtoReg	0	0	0	0	1	0	0	0	0	0
PCSource1	0	0	0	0	0	0	0	0	0	1
PCSource0	0	0	0	0	0	0	0	0	1	0
ALUOp1	0	0	0	0	0	0	1	0	0	0
ALUOp0	0	0	0	0	0	0	0	0	1	0
ALUSrcB1	0	1	1	0	0	0	0	0	0	0
ALUSrcB0	1	1	0	0	0	0	0	0	0	0
ALUSrcA	0	0	1	0	0	0	1	0	1	0
RegWrite	0	0	0	0	1	0	0	1	0	0
RegDst	0	0	0	0	0	0	0	1	0	0

Implementing Control with a ROM (Fig. D.4.5)

- Instead of a PLA, use a ROM with one word per state (“control word”)?

<i>State number</i>	<i>Control Word Bits 18-2</i>	<i>Control Word Bits 1-0</i>
0	100101000000001000	11
1	00000000010011000	01
2	000000000000010100	10
3	001100000000010100	11
4	001100100000010110	00
5	001010000000010100	00
6	000000000001000100	11
7	000000000001000111	00
8	010000000100100100	00
9	100000001000000000	00
10		11
11		00

ROM Implementation


- How many inputs are there?
6 bits for opcode, 4 bits for state = 10 address lines
(i.e., $2^{10} = 1024$ different addresses)
- How many outputs are there?
16 datapath-control outputs, 4 state bits = 20 outputs
- ROM is $2^{10} \times 20 = 20\text{K}$ bits (and a rather unusual size)
- Rather wasteful, since for lots of the entries, the outputs are the same
⇒ i.e., opcode is often ignored

ROM vs PLA

- Break up the table into two parts
 - ⇒ 4 state bits tell you the 16 outputs, $2^4 \times 16$ bits of ROM
 - ⇒ 10 bits tell you the 4 next state bits, $2^{10} \times 4$ bits of ROM
 - ⇒ Total: 4.3K bits of ROM
- PLA is much smaller
 - ⇒ can share product terms
 - ⇒ only need entries that produce an active output
 - ⇒ can take into account don't cares
- Size is $(\text{\#inputs} \times \text{\#product-terms}) + (\text{\#outputs} \times \text{\#product-terms})$
For this example = $(10 \times 17) + (20 \times 17) = 510$ PLA cells
- PLA cells usually about the size of a ROM cell (slightly bigger)

Another Implementation Style

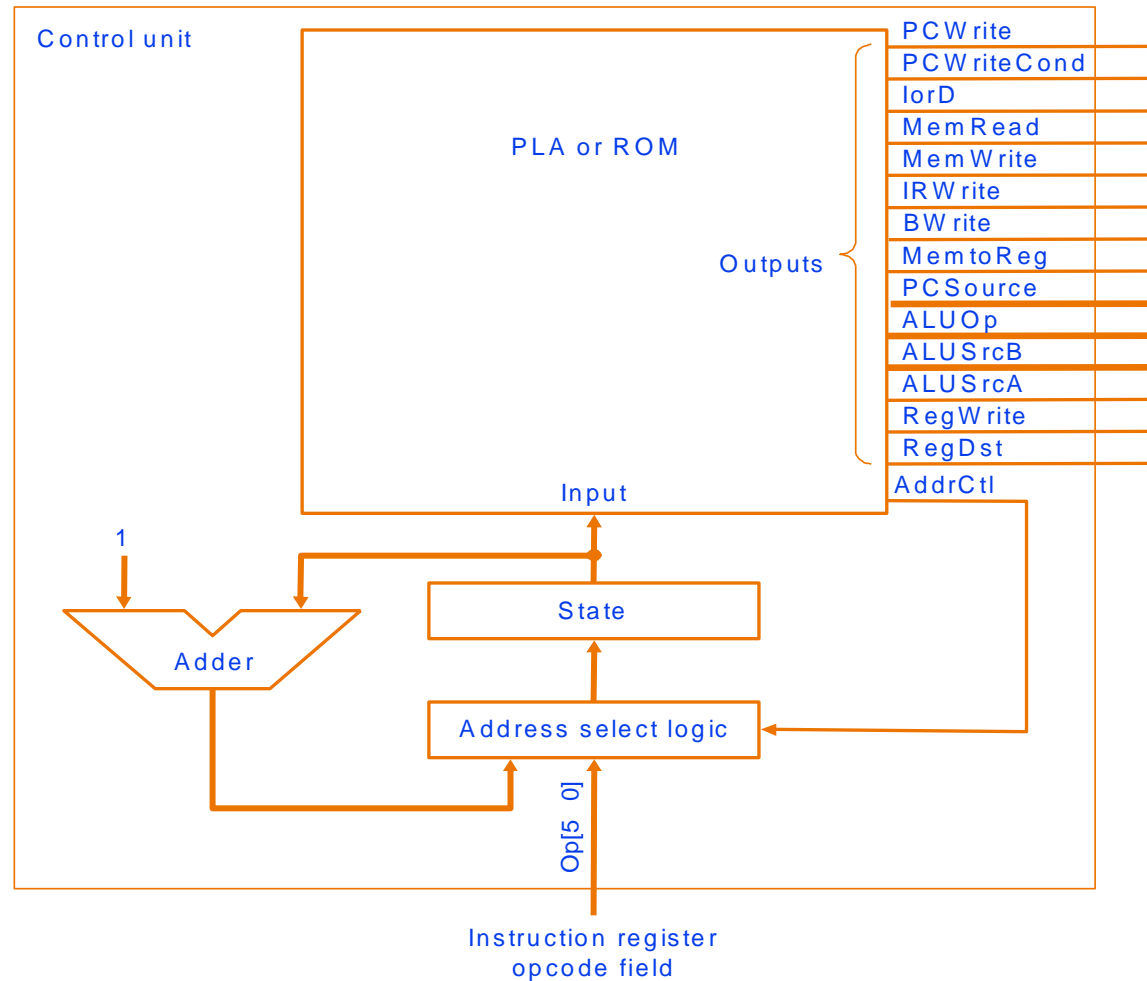- **Complex instructions:** the "next state" is often current state + 1




Next Iteration: Using Microprogram for Representation

Initial Representation

Sequencing Control

Logic Representation

Implementation Technique

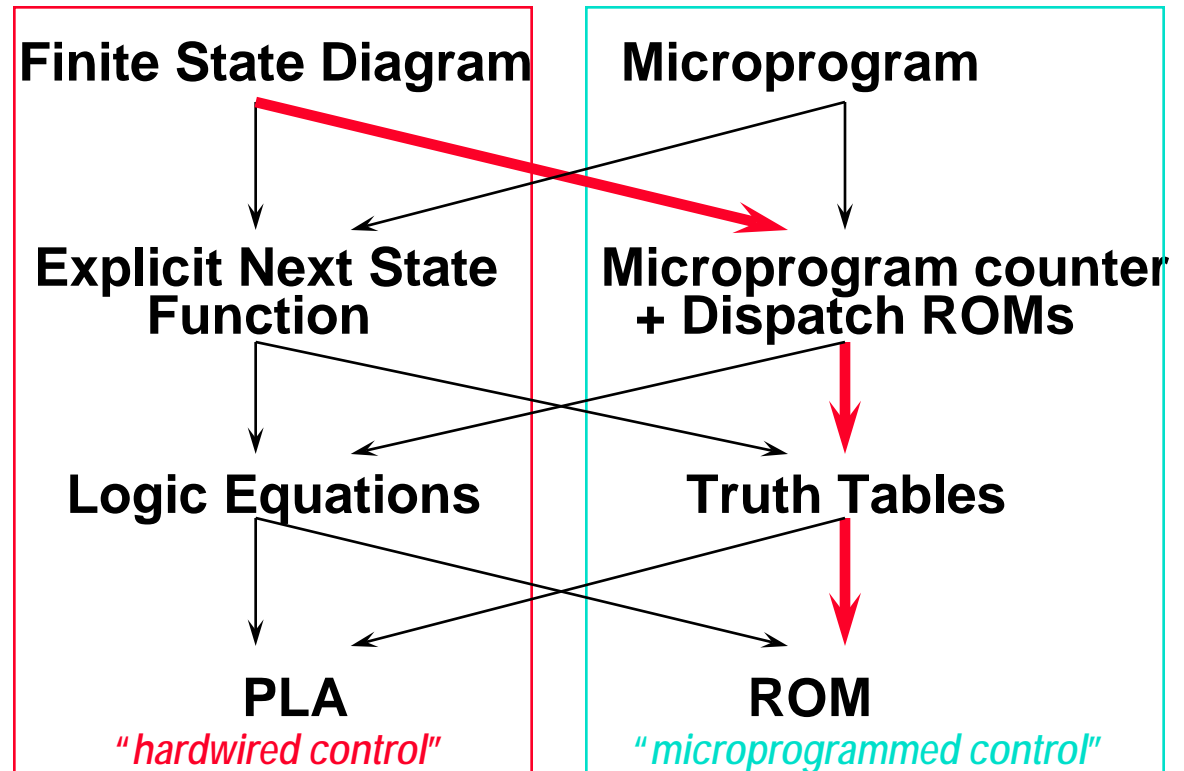


- ROM can be thought of as a sequence of control words
- Control word can be thought of as instruction: "Microinstruction"
- Rather than program in binary, use assembly language

Details (Figs. D.4.2, D.4.3, D.4.4)

Dispatch ROM 1		
Op	Opcode name	Value
000000	R-format	0110
000010	jmp	1001
000100	beq	1000
100011	lw	0010
101011	sw	0010

Dispatch ROM 2		
Op	Opcode name	Value
100011	lw	0011
101011	sw	0101

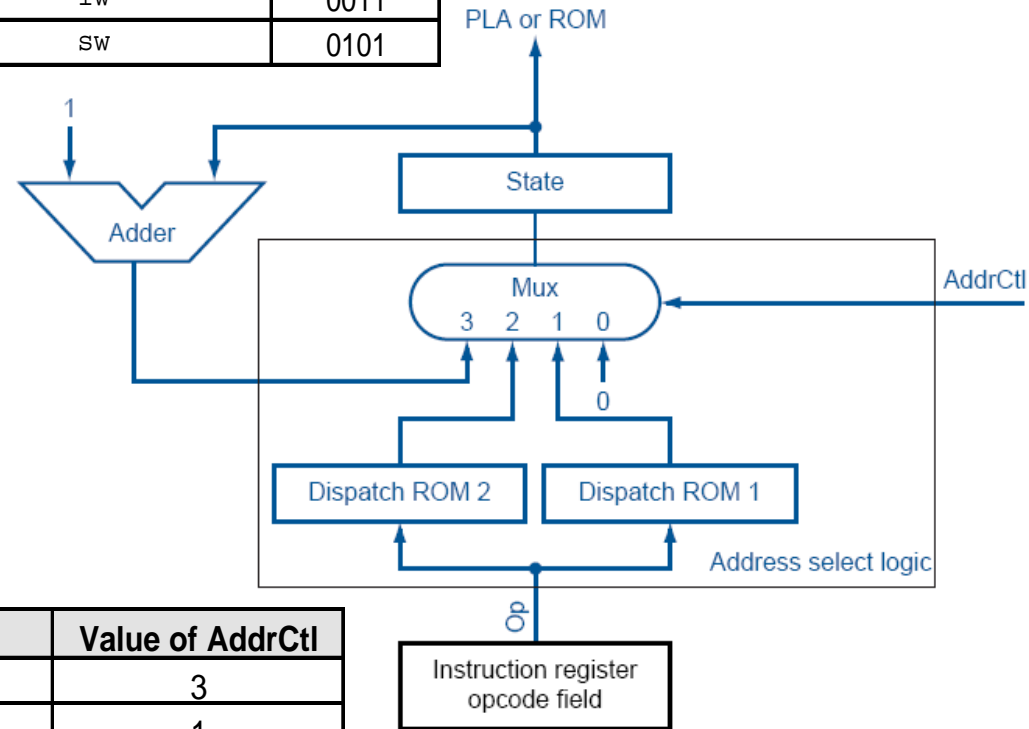

State number	Address-control action	Value of AddrCtl
0	Use incremented state	3
1	Use dispatch ROM 1	1
2	Use dispatch ROM 2	2
3	Use incremented state	3
4	Replace state number by 0	0
5	Replace state number by 0	0
6	Use incremented state	3
7	Replace state number by 0	0
8	Replace state number by 0	0
9	Replace state number by 0	0

Microprogramming

- **Control is the hard part of processor design**

Datapath is fairly regular and well-organized

Memory is highly regular

Control is irregular and global

Microprogramming:

⇒ **A Particular Strategy for Implementing the Control Unit of a processor by "programming" at the level of register transfer operations**


Microarchitecture:

⇒ **Logical structure and functional capabilities of the hardware as seen by the microprogrammer**

Historical Note:

**IBM 360 Series first to distinguish between architecture & organization
Same instruction set across wide range of implementations, each with
different cost/performance**

Macroinstruction Interpretation

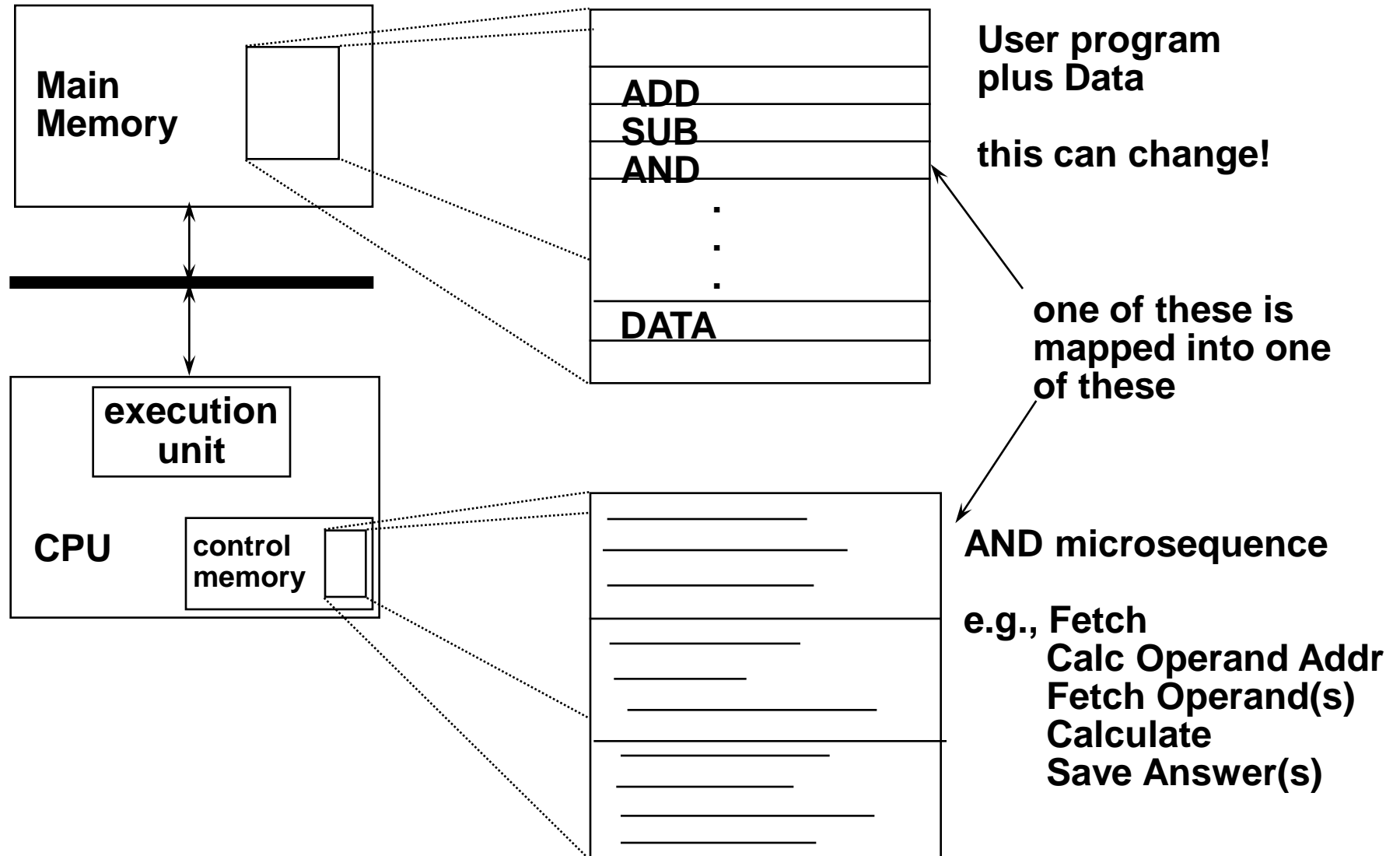

Variations on Microprogramming

- **Horizontal Microcode**


control field for each control point in the machine

μ seq	μ addr	A-mux	B-mux	bus enables	register enables	
-----------	------------	-------	-------	-------------	------------------	--


- **Vertical Microcode**

compact microinstruction format for each class of microoperation

branch:	μ seq-op	μ add
execute:	ALU-op	A,B,R
memory:	mem-op	S, D

 

Controller Implementation

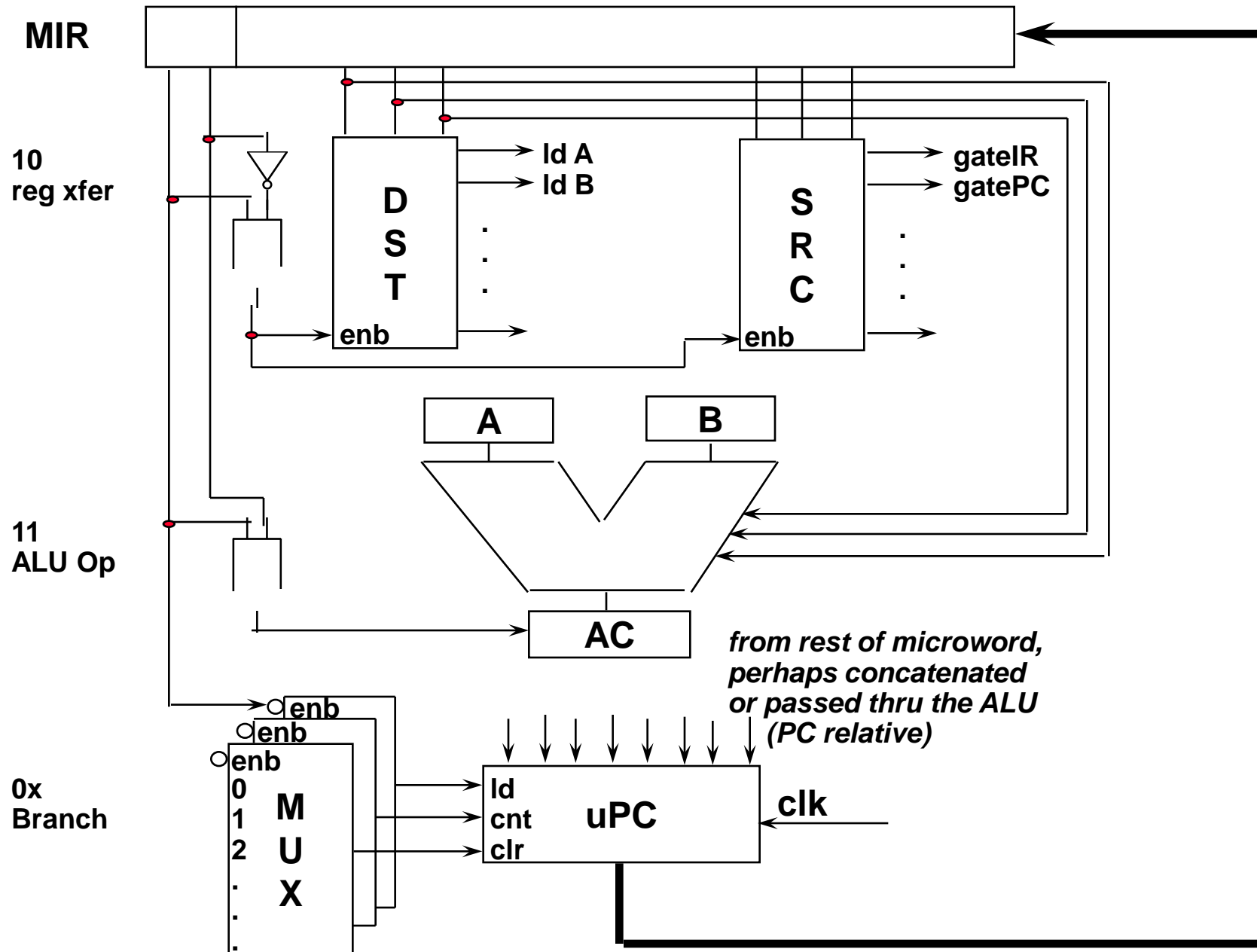

Microprogramming Pros and Cons

- **Ease of design**
- **Flexibility**
 - Easy to adapt to changes in organization, timing, technology
 - Can make changes late in design cycle, or even in the field
- **Can implement very powerful instruction sets (just more control memory)**
- **Generality**
 - Can implement multiple instruction sets on same machine
 - Can tailor instruction set to application
- **Compatibility**
 - Many organizations, same instruction set
- **Costly to implement**
- **Slow**

Microprogramming one inspiration for RISC

- If simple instruction could execute at very high clock rate
- If you could even write compilers to produce microinstructions
- If most programs use simple instructions and addressing modes
- If microcode is kept in RAM instead of ROM so as to fix bugs
- If same memory used for control memory could be used instead as cache for “macroinstructions” ...?
- Then why not skip instruction interpretation by a microprogram and simply compile directly into lowest language of machine?

Summary: Multicycle Control

- Microprogramming and hardwired control have many similarities, perhaps biggest difference is initial representation and ease of change of implementation, with ROM generally being easier than PLA

