


Computer Architecture

Ch. 3-2: ALU Design, Add/Sub

Spring, 2005

Sao-Jie Chen (csj@cc.ee.ntu.edu.tw)

 Review: Functional Specification of the ALU



- **ALU Control Lines (ALUop)**

000

001

010

110

111

Function

And

Or

Add

Subtract

Set-on-less-than

MIPS arithmetic instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comments</i>
add	add \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; exception possible
subtract	sub \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; exception possible
add immediate	addi \$1,\$2,80	$\$1 = \$2 + 80$	+ constant; exception possible
add unsigned	addu \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; no exceptions
subtract unsigned	subu \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; no exceptions
add imm. unsign.	addiu \$1,\$2,80	$\$1 = \$2 + 80$	+ constant; no exceptions
multiply	mult \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit signed product
multiply unsigned	multu \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit unsigned product
divide	div \$2,\$3	Lo = $\$2 \div \3 , Hi = $\$2 \bmod \3	Lo = quotient, Hi = remainder
divide unsigned	divu \$2,\$3	Lo = $\$2 \div \3 , Hi = $\$2 \bmod \3	Unsigned quotient & remainder
Move from Hi	mfhi \$1	$\$1 = \text{Hi}$	Used to get copy of Hi
Move from Lo	mflo \$1	$\$1 = \text{Lo}$	Used to get copy of Lo

MIPS logical instructions


<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comment</i>
and	and \$1,\$2,\$3	$\$1 = \$2 \& \$3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$\$1 = \$2 \$3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$\$1 = \$2 \oplus \$3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$\$1 = \sim(\$2 \$3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$\$1 = \$2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$\$1 = \$2 10$	Logical OR reg, constant
xor immediate	xori \$1, \$2,10	$\$1 = \$2 \oplus 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$\$1 = \$2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$\$1 = \$2 \ll \$3$	Shift left by variable
shift right logical	srlv \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right by variable
shift right arithm.	srav \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right arith. by variable

Additional MIPS ALU requirements

- **Xor, Nor, Xori**
=> Logical XOR, logical NOR or use 2 steps: $(A \text{ OR } B) \text{ XOR } 1111...1111$
- **Sll, Srl, Sra**
=> Need left shift, right shift, right shift arithmetic by 0 to 31 bits
- **Mult, MultU, Div, DivU**
=> Need 32-bit multiply and divide, signed and unsigned

Add XOR to ALU

- Expand Multiplexor

 


Shifters

- Three different kinds:

logical-- value shifted in is always "0"



 arithmetic-- on right shifts, sign extend




rotating-- shifted out bits are wrapped around (not in MIPS)



Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!

Barrel Shifter

- Technology-dependent solutions:

 

Compare and Branch

- Compare and Branch

- **BEQ rs, rt, offset** if $R[rs] == R[rt]$ then PC-relative branch
- **BNE rs, rt, offset** \neq

- Compare to zero and branch

- **BLEZ rs, offset** if $R[rs] \leq 0$ then PC-relative branch
- **BGTZ rs, offset** $>$
- **BLT** $<$
- **BGEZ** \geq
- **BLTZAL rs, offset** if $R[rs] < 0$ then branch and link (into R 31)
- **BGEZAL** \geq

MIPS ALU requirements



- **Add, AddU, Sub, SubU, AddI, AddIU**
=> 2's complement adder with overflow detection & inverter
- **SLTI, SLTIU (set less than)**
=> 2's complement adder with inverter, check sign bit of result
- **BEQ, BNE (branch on equal or not equal)**
=> 2's complement adder with inverter, check if result = 0
- **And, Or, Andi, Ori**
=> Logical AND, logical OR
- ALU from last lecture supports these ops


Tailoring the ALU to the MIPS

- Need to support the set-on-less-than instruction (**slt**)
 - remember: `slt` is an arithmetic instruction
 - produces a 1 if $rs < rt$ and 0 otherwise
 - use subtraction: $(a-b) < 0$ implies $a < b$
- Need to support test for equality (**beq \$t5, \$t6, \$t7**)
 - use subtraction: $(a-b) = 0$ implies $a = b$

Supporting slt

- Can we figure out the idea?

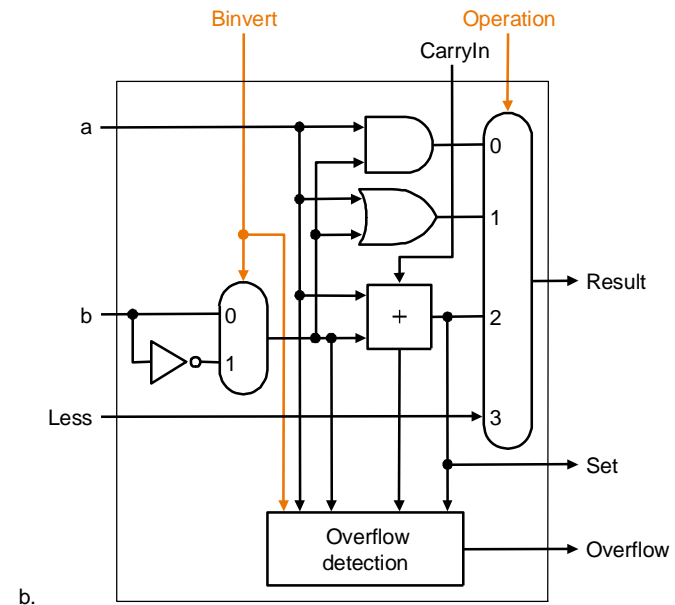 

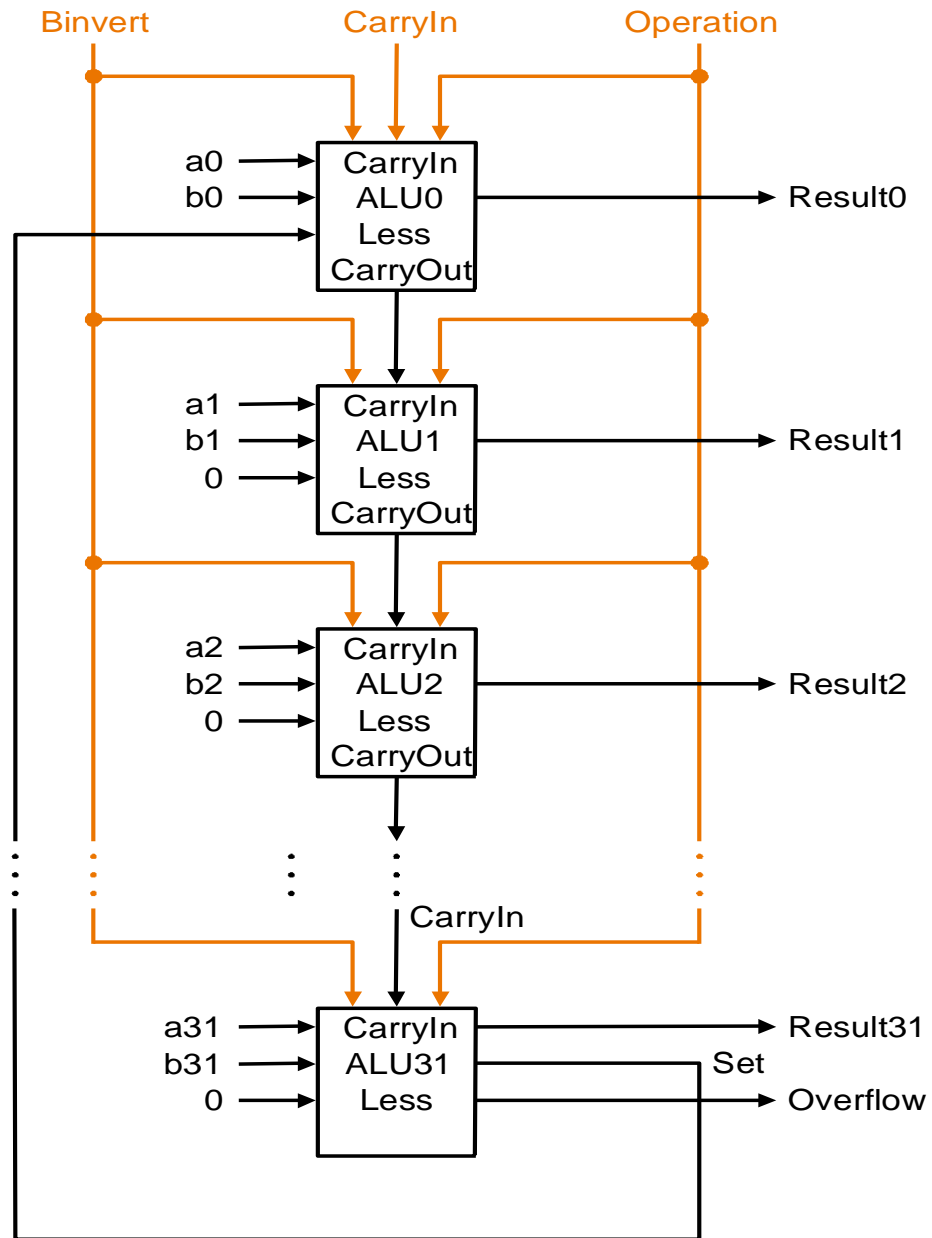

Addition & Subtraction

- Just like in grade school (carry/borrow 1s)

$$\begin{array}{r} 0111 \\ + 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0111 \\ - 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0110 \\ - 0101 \\ \hline \end{array}$$

- Two's complement operations easy
 - subtraction using addition of negative numbers

$$\begin{array}{r} 0111 \\ + 1010 \\ \hline \end{array}$$

- Overflow (result too large for finite computer word):
 - e.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 0111 \\ + 0001 \\ \hline 1000 \\ \hline \end{array}$$

*note that overflow term is somewhat misleading,
it does not mean a carry “overflowed”*



Overflow Detection

Overflow: the result is too large (or too small) to represent properly

  - Example: $-8 \leq 4\text{-bit binary number} \leq 7$
- When adding operands with different signs, overflow cannot occur!
- Overflow occurs when adding:
 - 2 positive numbers and the sum is negative
 - 2 negative numbers and the sum is positive


Homework exercise: Prove you can detect overflow by:

- **Carry into MSB \neq Carry out of MSB**




Overflow Detection Logic

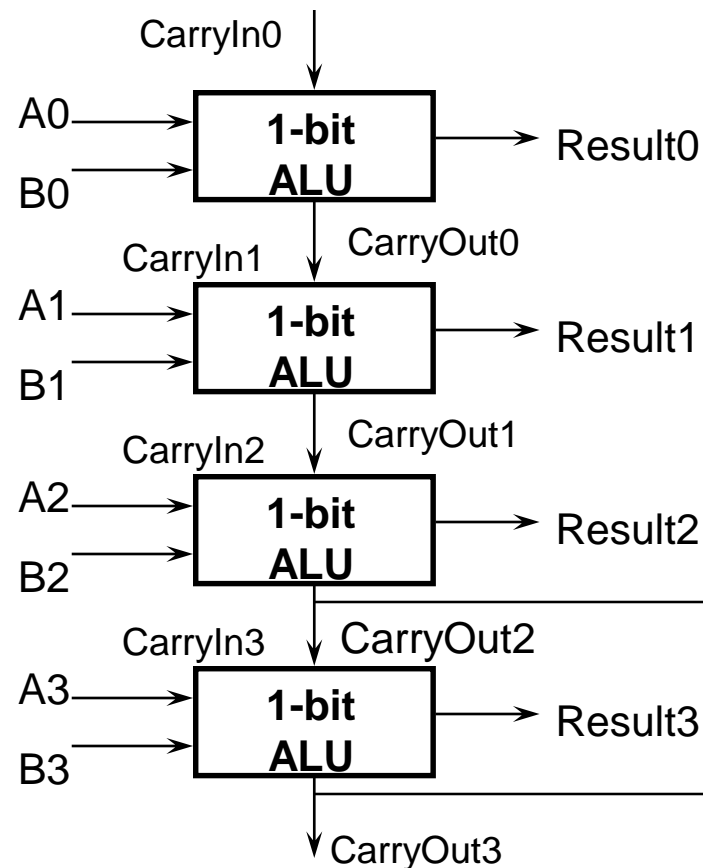- **Carry into MSB \neq Carry out of MSB**
 - For a N-bit ALU: **Overflow = CarryIn[N - 1] XOR CarryOut[N - 1]**




X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

 

Zero Detection Logic

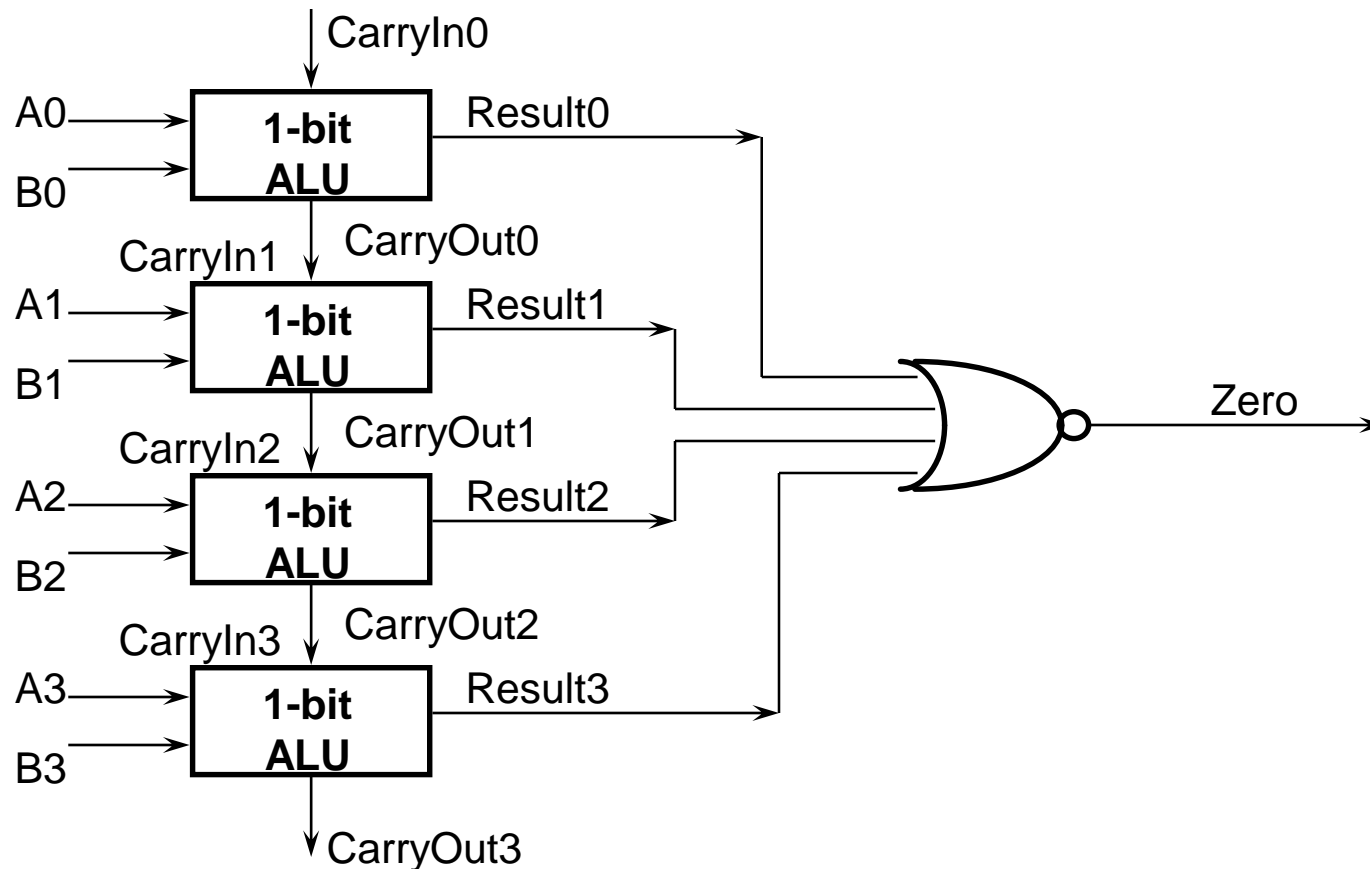- **Zero Detection Logic is just a one BIG NOR gate**
 - Any non-zero input to the NOR gate will cause its output to be zero




Test for equality

- **Notice control lines:**

000 = and
001 = or
010 = add
110 = subtract
111 = slt

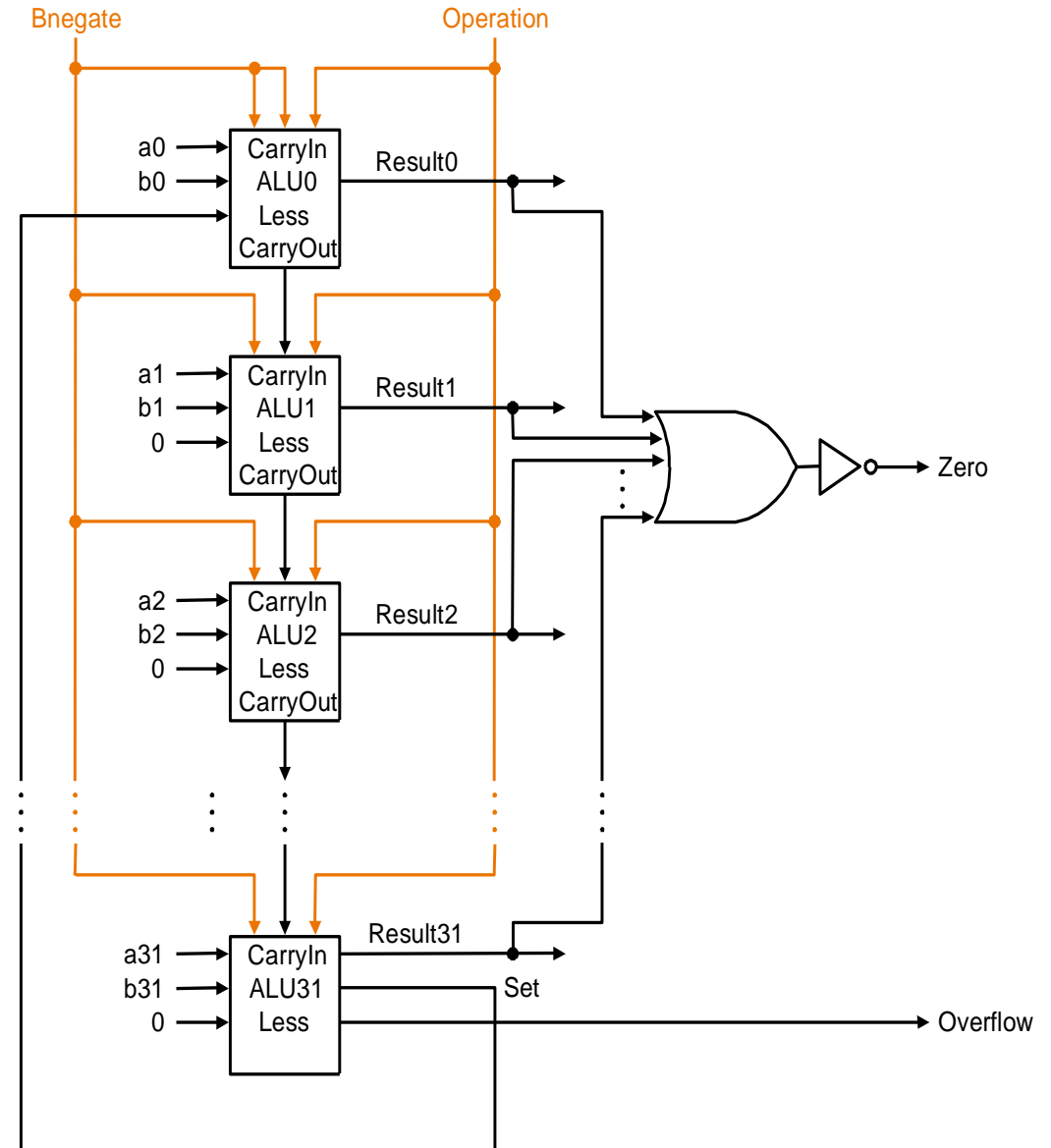- **Note:** *zero is a 1 when the result is zero!*





Conclusion

- **We can build an ALU to support the MIPS instruction set**
 - key idea: use multiplexor to select the output we want
 - we can efficiently perform subtraction using two's complement
 - we can replicate a 1-bit ALU to produce a 32-bit ALU
- **Important points about hardware**
 - all of the gates are always working
 - the speed of a gate is affected by the number of inputs to the gate
 - the speed of a circuit is affected by the number of gates in series (on the “critical path” or the “deepest level of logic”)
- **Our primary focus: comprehension, however,**
 - Clever changes to organization can improve performance (similar to using better algorithms in software)
 - we'll look at two examples for addition and multiplication

The Disadvantage of Ripple Carry

 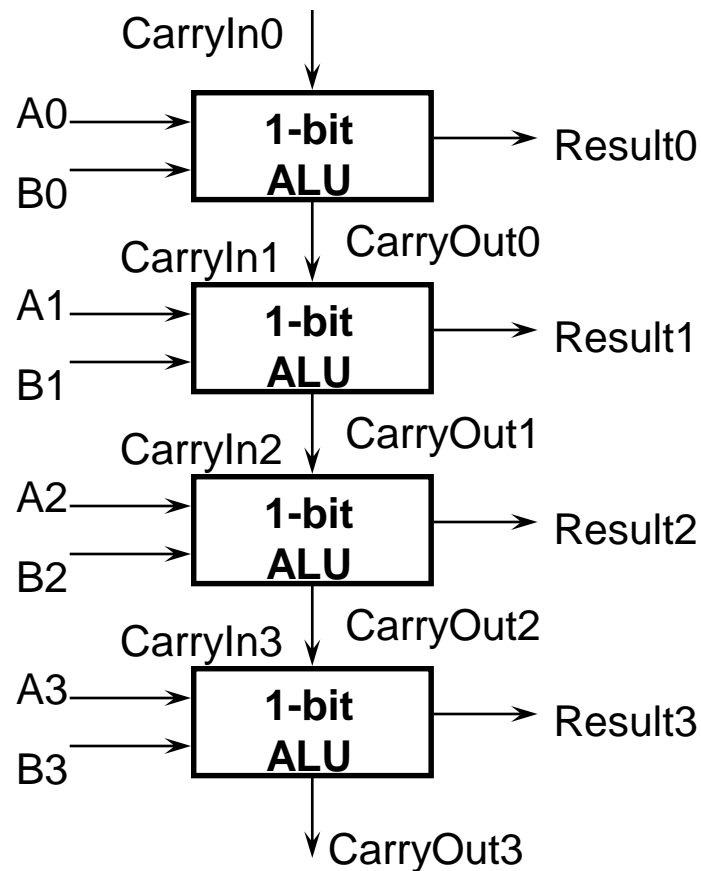- The adder we just built is called a **Ripple Carry Adder**
 - The carry bit may have to propagate from LSB to MSB
 - Worst case delay for a N-bit adder: **$2N$ -gate delay**



Problem: ripple carry adder is slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition?
 - two extremes: ripple carry and **sum-of-products**

Can you see the ripple? How could you get rid of it?

Use sum-of-products

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0$$

$$c_2 = b_1 c_1 + a_1 c_1 + a_1 b_1$$

$$c_3 = b_2 c_2 + a_2 c_2 + a_2 b_2$$

$$c_4 = b_3 c_3 + a_3 c_3 + a_3 b_3$$


$$c_2 = (b_1 + a_1) (b_0 c_0 + a_0 c_0 + a_0 b_0) + a_1 b_1$$

$$c_3 = (b_2 + a_2) (b_1 c_1 + a_1 c_1 + a_1 b_1) + a_2 b_2$$

$$c_4 = \dots$$

Not feasible! Why?

The Theory Behind Carry Lookahead

 

- Recalled: $\text{CarryOut} = (B \& \text{CarryIn}) \mid (A \& \text{CarryIn}) \mid (A \& B)$
 - $\text{Cin1} = \text{Cout0} = (B0 \& \text{Cin0}) \mid (A0 \& \text{Cin0}) \mid (A0 \& B0)$
 - $\text{Cin2} = \text{Cout1} = (B1 \& \text{Cin1}) \mid (A1 \& \text{Cin1}) \mid (A1 \& B1)$
- Substituting Cin1 into Cin2:
 - $$\text{Cin2} = \begin{array}{l} (A1 \& B0 \& \text{Cin0}) \mid (A1 \& A0 \& \text{Cin0}) \mid (A1 \& A0 \& B0) \mid \\ (B1 \& B0 \& \text{Cin0}) \mid (B1 \& A0 \& \text{Cin0}) \mid (B1 \& A0 \& B0) \mid (A1 \& B1) \end{array}$$
- Now define two new terms:
 - Generate Carry at Bit i $g_i = A_i \& B_i$
 - Propagate Carry via Bit i $p_i = A_i \text{ or } B_i$

Carry-lookahead adder

- An approach in-between our two extremes

- Motivation:

- If we didn't know the value of carry-in, what could we do?

- When would we always generate a carry?

$$g_i = a_i b_i$$

- When would we propagate the carry?

$$p_i = a_i + b_i$$

- Did we get rid of the ripple?

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 c_3$$


$$c_4 =$$

Feasible! Why?


The Theory Behind Carry Lookahead (Continued)

- Using the two new terms we just defined:
 - Generate Carry at Bit i $g_i = A_i \& B_i$
 - Propagate Carry via Bit i $p_i = A_i \text{ or } B_i$
- We can rewrite:
 - $Cin1 = g_0 \mid (p_0 \& Cin0)$
 - $Cin2 = g_1 \mid (p_1 \& g_0) \mid (p_1 \& p_0 \& Cin0)$
 - $Cin3 = g_2 \mid (p_2 \& g_1) \mid (p_2 \& p_1 \& g_0) \mid (p_2 \& p_1 \& p_0 \& Cin0)$
- Carry going into bit 3 is 1 if
 - We generate a carry at bit 2 (g_2)
 - Or we generate a carry at bit 1 (g_1) and bit 2 allows it to propagate (p_2) $\Rightarrow (p_2 \& g_1)$
 - Or we generate a carry at bit 0 (g_0) and bit 1 as well as bit 2 allows it to propagate ($p_2 \& p_1 \& g_0$)
 - Or we have a carry input at bit 0 ($Cin0$) and bit 0, 1, and 2 all allow it to propagate ($p_2 \& p_1 \& p_0 \& Cin0$)


Carry Look Ahead (Design trick: peek)

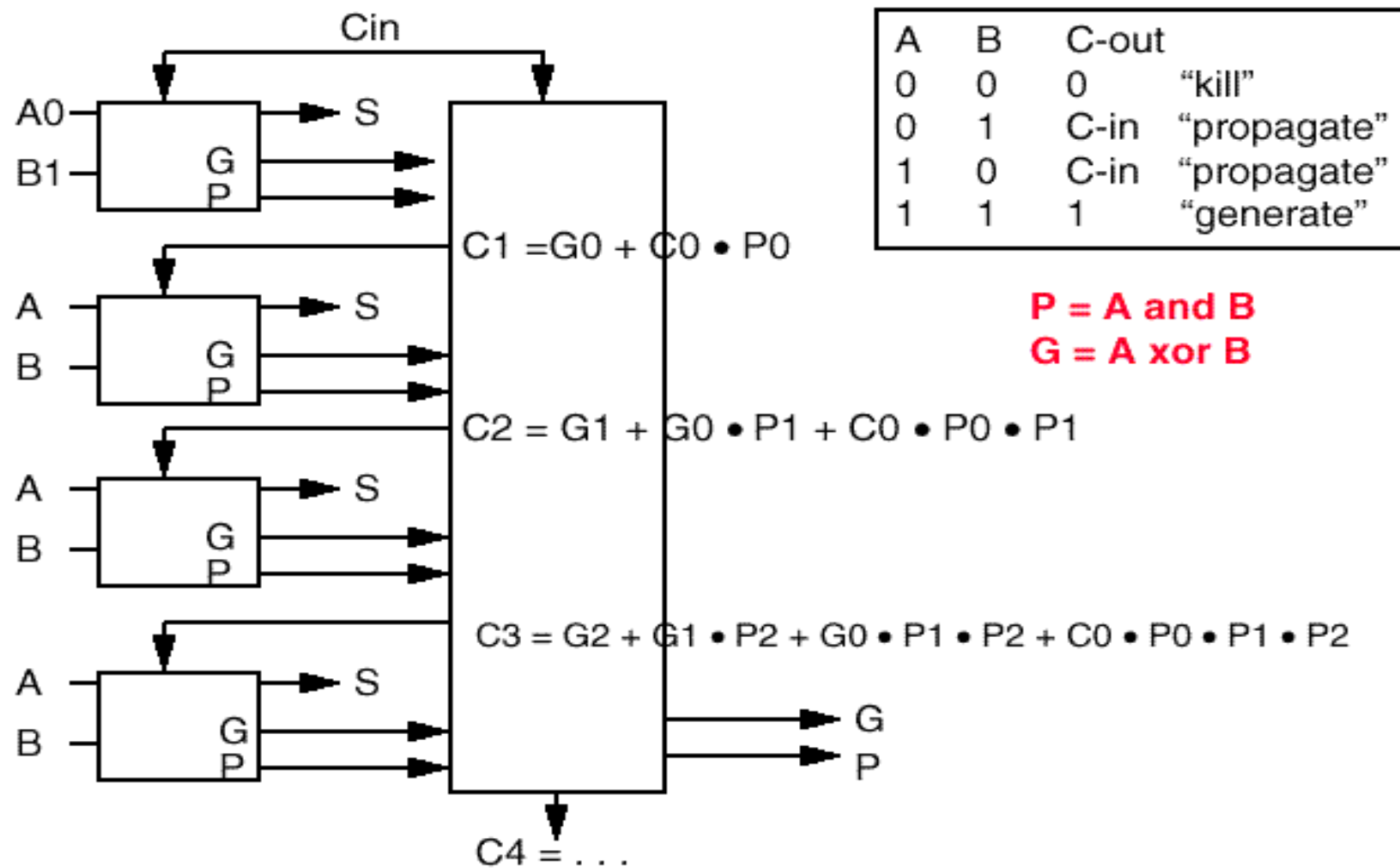


Plumbing as Carry Lookahead Analogy

 

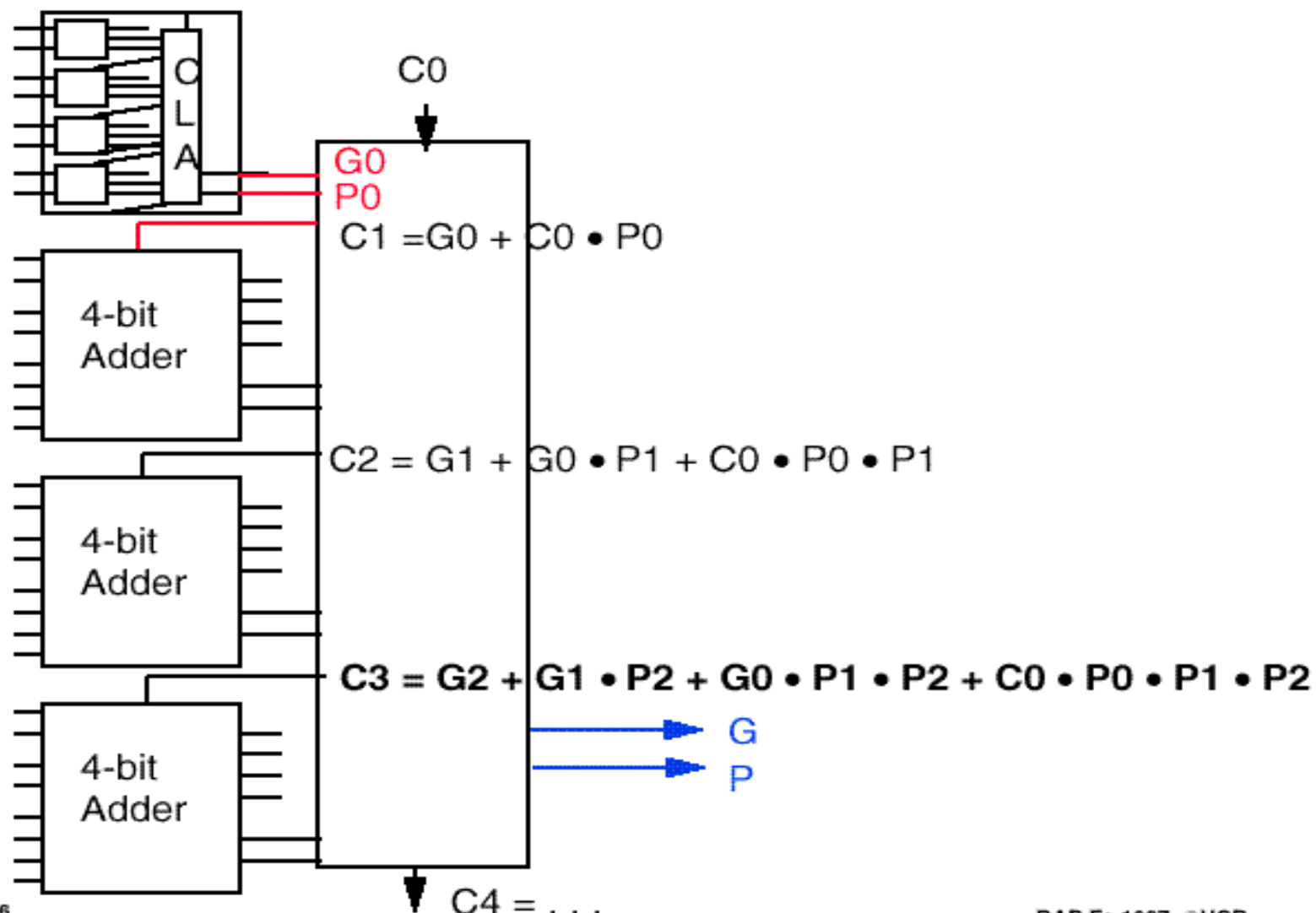Cascaded Carry Look-ahead (16-bit): Abstraction




2nd level Carry, Propagate as Plumbing

 


A Partial Carry Lookahead Adder

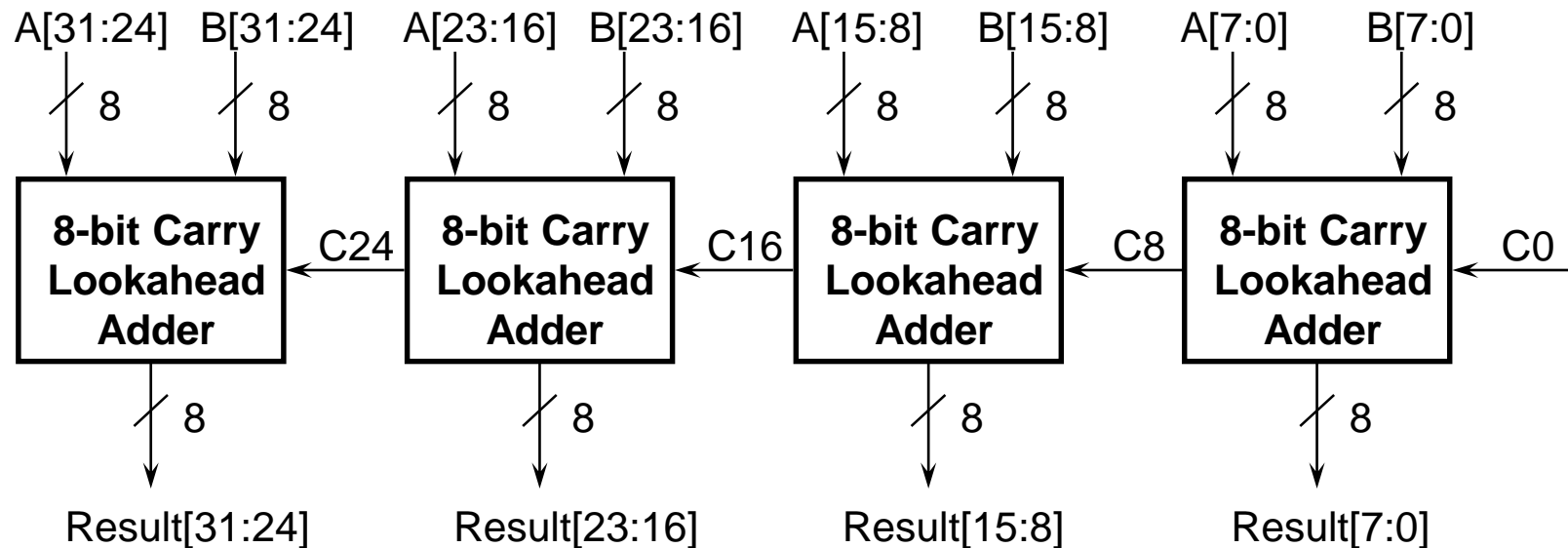- It is very expensive to build a “full” carry lookahead adder
 - Just imagine the length of the equation for C_{in31}
- Common practices:
 - Connects several N-bit Lookahead Adders to form a big adder
 - Example: connects four 8-bit carry lookahead adders to form a 32-bit partial carry lookahead adder




Carry Select Adder

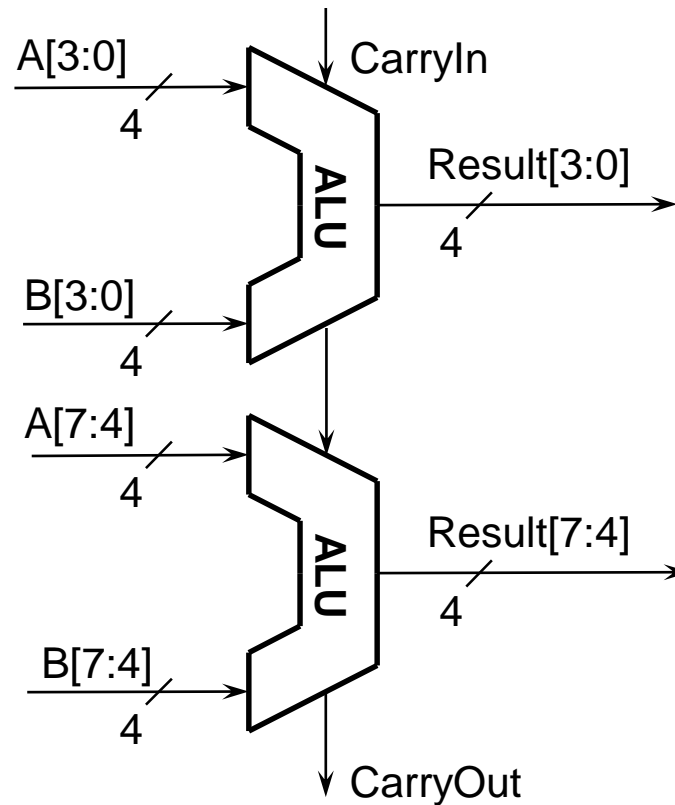- Consider building a 8-bit ALU
 - Simple: connects two 4-bit ALUs in series



Carry Select Adder (Continued)

 - Consider building a 8-bit ALU
 - Expensive but faster: uses three 4-bit ALUs



Summary

- **An Overview of the Design Process**
 - Design is an iterative process-- successive refinement
 - Do NOT wait until you know everything before you start
- **An Introduction to Binary Arithmetic**
 - If you use 2's complement representation, subtract is easy.
- **ALU Design**
 - Designing a Simple 4-bit ALU
 - Other ALU Construction Techniques
- **On-line Design Notebook**
 - Open a window and keep an editor running while you work
 - Refer to the handout as an example

To Get More Information

- Chapter 3 of your text book:
 - David Patterson & John Hennessy, *Computer Organization & Design*, 3rd Ed., @2004, Morgan Kaufmann Publishers.
- A good book :
 - David Winkel & Franklin Prosser, *The Art of Digital Design: An Introduction to Top-Down Design*, 2nd Ed., @1987, Prentice-Hall, Inc.