

CIRCUIT SIMULATION-1


CIRCUIT NETWORK ANALYSIS

Circuit Simulation


Input: Circuit description and
input stimulus

Output: Approximate voltage or
current waveforms.

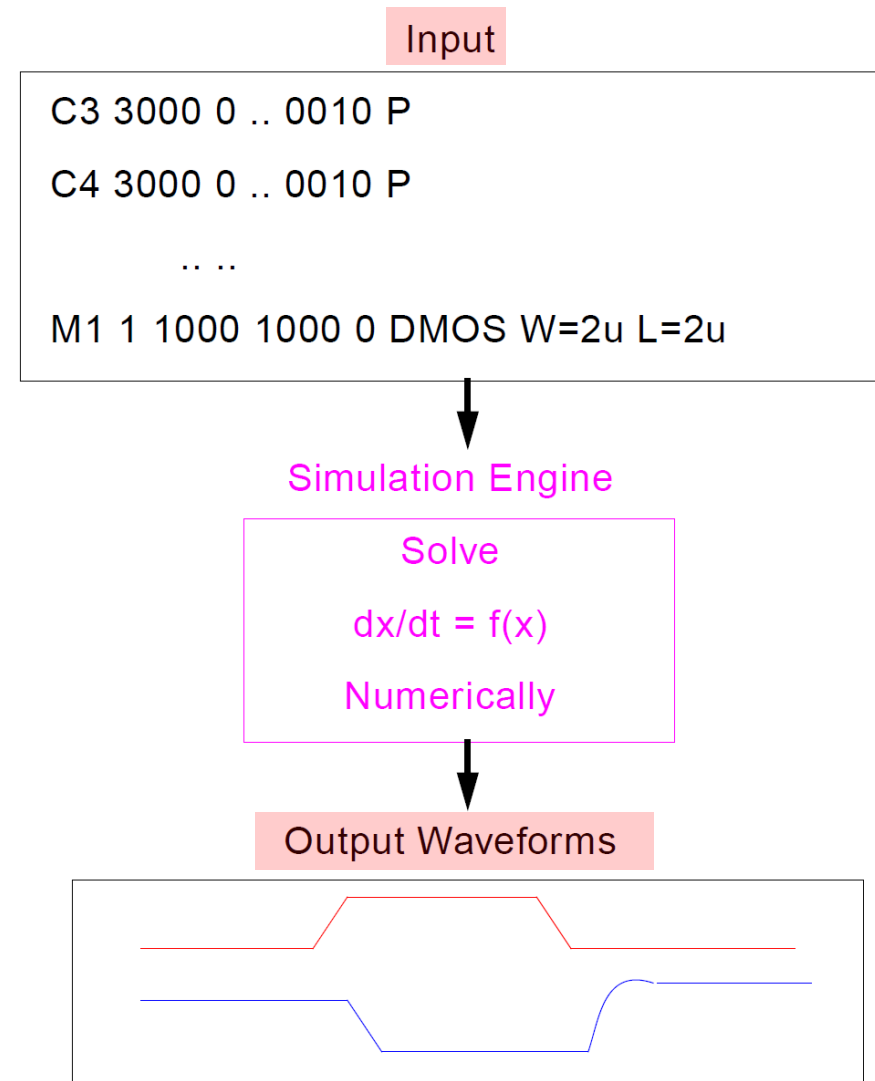T. L. Pillage, R. A. Rohrer, and C.
Visweswariah, *Electronic Circuit &
System Simulation Methods*,
McGraw-Hill, Inc. 1995.




Simulation Program Structure

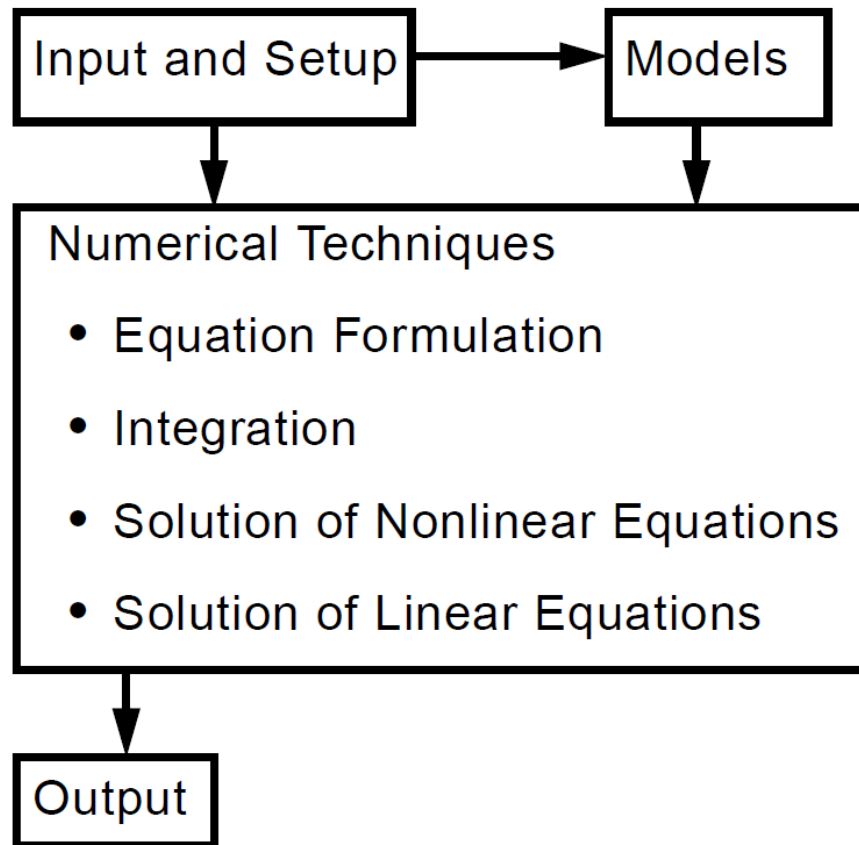

Types of Analysis

- **DC Analysis**
- **DC Transfer Curves**
- **Transient Analysis**
- **AC Analysis Noise, Distortion, Sensitivity**

Modeling

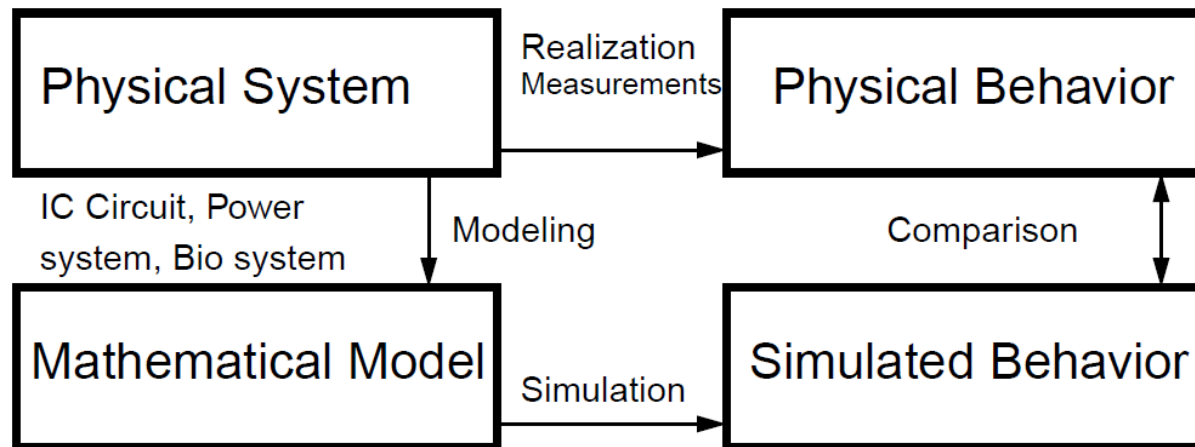



Formulation of Circuit Equations

- **KCL (Kirchoff's Current Law):** branch currents sum to zero at every node.
- **KVL (Kirchoff's Voltage Law):** branch voltage sum to zero around every loop.
- **BCR (Branch Constitutive Relationships):** *i.e.*, device models, or equations for all the circuit components.

BCR Branch Equations

Mathematical models of circuit components are expressed:

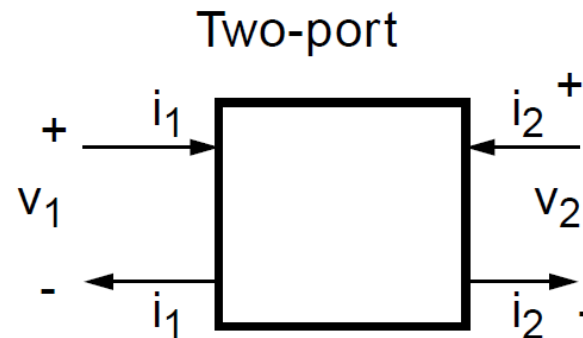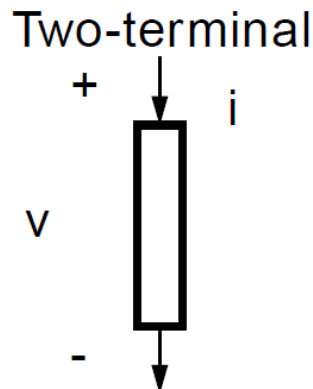
- in terms of ideal elements --Inductors, Capacitors, Resistors, Current Sources, Voltage Sources, Two-ports,
- in terms of physical quantities - current, voltage, charge, flux




where i , v are branch currents and voltages respectively.

Ideal Elements: Linear Two-Terminal


- **Resistor:** $i = (1/R)v$; $v = R i$

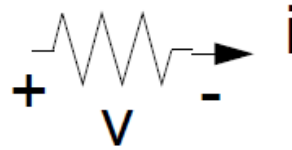

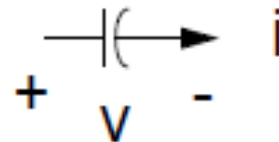- **Capacitor:** $q = C v$; $i = dq/dt = C dv/dt$




- **Inductor:** $v = L di/dt$

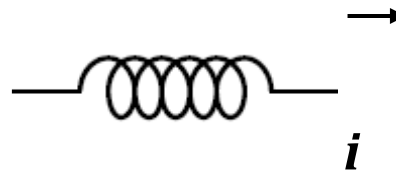


Controlled Sources

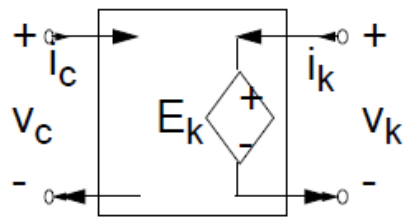
- **VCVS (Voltage Controlled Voltage Source):** $v_k = E_k v_c; \quad i_c = 0.$



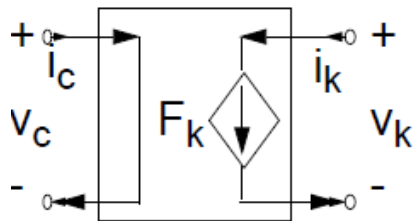- **CCCS (Current Controlled Current Source):** $i_k = F_k i_c; \quad v_c = 0.$



Matrix Forms of KVL and KCL

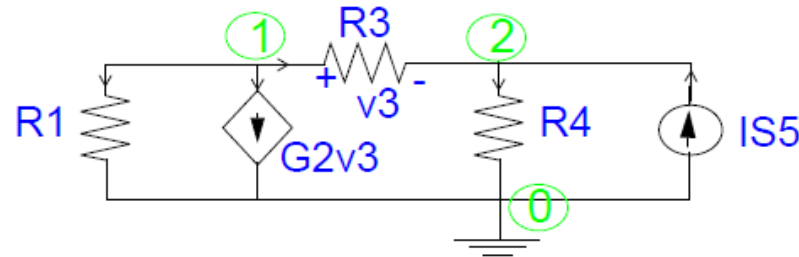

- KCL: $A i = 0$

$$\begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

- KVL: $v - A^T e = 0$

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} - \begin{bmatrix} 1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Equation Assembly for Linear Circuits

- (1) Sparse Tableau Analysis (STA)
- (2) Modified Nodal Analysis (MNA)
- (3) Tree/link Analysis

(1) STA: Sparse Tableau Analysis [Brayton, Gustavson, Hachtel (1969-71)]

- Write KCL: $A i = 0$, n equations for each node
- Write KVL: $v - A^T e = 0$, b equations for each branch
- Write Branch Equations:

$K_i i$ for current controlled;

$K_v v$ for voltage controlled.

$$K_i i + K_v v = S; \quad b \text{ equations}$$

$$\begin{bmatrix} A & 0 & 0 \\ 0 & I & -A^T \\ K_i & K_v & 0 \end{bmatrix} \begin{bmatrix} i \\ v \\ e \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ S \end{bmatrix} \left. \vphantom{\begin{bmatrix} A & 0 & 0 \\ 0 & I & -A^T \\ K_i & K_v & 0 \end{bmatrix}} \right\} \begin{array}{l} n + 2b \\ \text{equations} \end{array}$$

sparse tableau

$n + 2b$ unknowns

$n = \# \text{ nodes}$
 $b = \# \text{ branches}$

Equation Assembly for Linear Circuits


(2) Nodal Analysis [McCalla, Nagel, Rohrer, Ruehli, Ho]

Step 1: Write KCL

$$i1 + i2 + i3 = 0 \quad \text{on node ①}$$

$$-i3 + i4 - i5 = 0 \quad \text{on node ②}$$

(I)

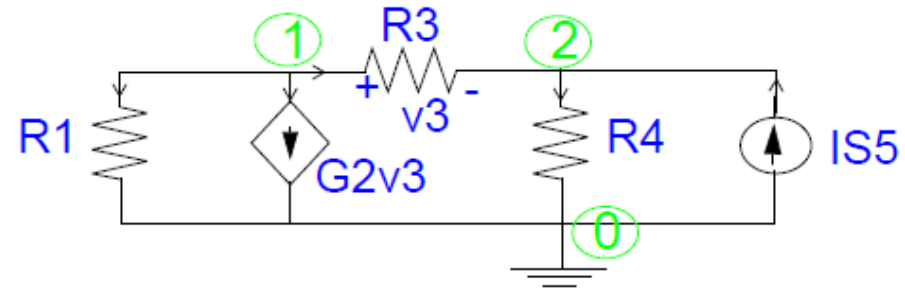

Step 2: Use branch equations to eliminate branch currents from (I)

$$\frac{1}{R1} v1 + G2v3 + \frac{1}{R3} v3 = 0 \quad \text{node ①}$$

$$-\frac{1}{R3} v3 + \frac{1}{R4} v4 = IS5 \quad \text{node ②} \quad \text{(II)}$$

Step 3: Use KVL to eliminate branch voltages from (II)

$$\frac{1}{R1} e1 + G2(e1 - e2) + \frac{1}{R3} (e1 - e2) = 0 \quad \text{node ①}$$

$$-\frac{1}{R3} (e1 - e2) + \frac{1}{R4} e2 = IS5 \quad \text{node ②} \quad \text{(III)}$$

Nodel Analysis in Matrix Form: $Y_n e = IS$

$$\begin{bmatrix} \frac{1}{R1} + G2 + \frac{1}{R3} & -G2 - \frac{1}{R3} \\ -\frac{1}{R3} & \frac{1}{R3} + \frac{1}{R4} \end{bmatrix} \begin{bmatrix} e1 \\ e2 \end{bmatrix} = \begin{bmatrix} 0 \\ IS5 \end{bmatrix}$$

Y_n and IS can be directly assembled from the input data.

Note that the system matrix can be written as the sum of 4 matrices:


$$\begin{bmatrix} \frac{1}{R1} + G2 + \frac{1}{R3} & -G2 - \frac{1}{R3} \\ -\frac{1}{R3} & \frac{1}{R3} + \frac{1}{R4} \end{bmatrix} = \begin{bmatrix} \frac{1}{R1} & 0 \\ 0 & 0 \end{bmatrix} + \begin{bmatrix} G2 & -G2 \\ 0 & 0 \end{bmatrix} + \begin{bmatrix} \frac{1}{R3} & -\frac{1}{R3} \\ -\frac{1}{R3} & \frac{1}{R3} \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & \frac{1}{R4} \end{bmatrix}$$

Each matrix relates to a specific element.

The contribution of an element is called *element stamp*.

Nodal Analysis Elements (1)

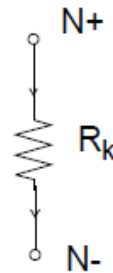Resistor: R_k N^+ N^- R_k value (SPICE Input Format)




Resistor “Stamp”:

$$\begin{array}{c} N^+ \\ \vdots \\ N^- \end{array} \begin{bmatrix} & N^+ & \dots & N^- \\ 1/R_k & & -1/R_k & \\ \vdots & & & \vdots \\ -1/R_k & & 1/R_k & \end{bmatrix}$$

Nodal Analysis Elements (2)

VCCS: G_k N+ N- NC+ NC- G_k value


VCCS “Stamp”:

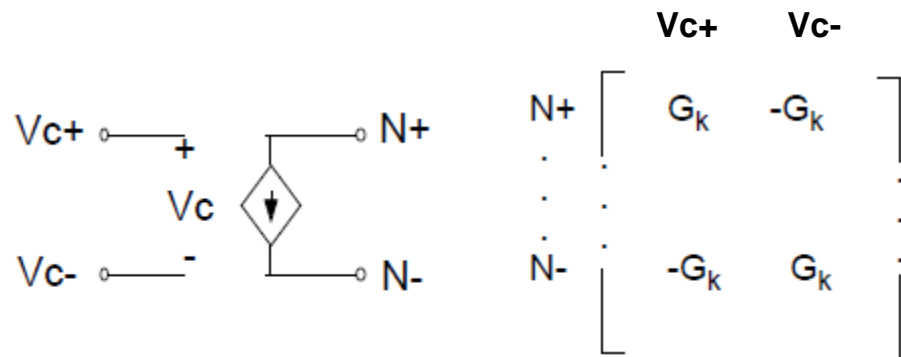

Independent Current Source: I_k N+ N- I_k value

Stamp:
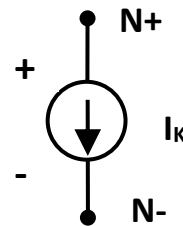
$$\begin{array}{c}
 N+ \\
 \vdots \\
 N-
 \end{array}
 \begin{bmatrix}
 \\
 \\
 \\
 \end{bmatrix}
 =
 \begin{bmatrix}
 -I_k \\
 \\
 +I_k
 \end{bmatrix}$$



MNA: Modified Nodal Analysis (1)


Step 1: Write KCL

$$i_1 + i_2 + i_3 = 0 \quad \text{on node ①}$$

$$-i_3 + i_4 - i_5 - i_6 = 0 \quad \text{on node ②}$$

$$i_6 + i_8 = 0 \quad \text{on node ③}$$

$$i_7 - i_8 = 0 \quad \text{on node ④}$$

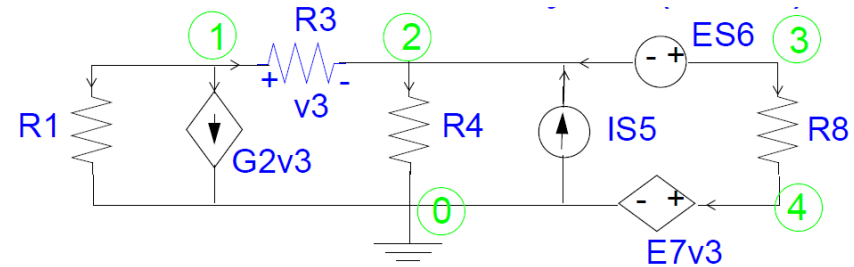

Step 2: Use branch equations to eliminate as many branch currents as possible

$$\frac{1}{R_1} v_1 + G_2 v_3 + \frac{1}{R_3} v_3 = 0 \quad \text{node ①}$$

$$-\frac{1}{R_3} v_3 + \frac{1}{R_4} v_4 - i_6 = IS_5 \quad \text{node ②}$$

$$i_6 + \frac{1}{R_8} v_8 = 0 \quad \text{node ③}$$

$$i_7 - \frac{1}{R_8} v_8 = 0 \quad \text{node ④}$$

MNA: Modified Nodal Analysis (2)

Step 3: Write down unused branch equations

$$v_6 = ES_6 \quad (\text{b6})$$

$$v_7 - E_7 v_3 = 0 \quad (\text{b7})$$

Step 4: Use KVL to eliminate branch voltages from previous equations

$$\frac{1}{R_1} e_1 + G_2(e_1 - e_2) + \frac{1}{R_3}(e_1 - e_2) = 0 \quad \text{node } \textcircled{1}$$

$$-\frac{1}{R_3}(e_1 - e_2) + \frac{1}{R_4} e_2 - i_6 = IS_5 \quad \text{node } \textcircled{2}$$

$$i_6 + \frac{1}{R_8}(e_3 - e_4) = 0 \quad \text{node } \textcircled{3}$$

$$i_7 - \frac{1}{R_8}(e_3 - e_4) = 0 \quad \text{node } \textcircled{4}$$

$$(e_3 - e_2) = ES_6 \quad (\text{b6})$$

$$e_4 - E_7(e_1 - e_2) = 0 \quad (\text{b7})$$

MNA in Matrix Form

$$\begin{bmatrix} \frac{1}{R1} + G2 + \frac{1}{R3} & -G2 - \frac{1}{R3} & 0 & 0 & 0 & 0 \\ -\frac{1}{R3} & \frac{1}{R3} + \frac{1}{R4} & 0 & 0 & -1 & 0 \\ 0 & 0 & \frac{1}{R8} & -\frac{1}{R8} & 1 & 0 \\ 0 & 0 & -\frac{1}{R8} & \frac{1}{R8} & 0 & 1 \\ 0 & -1 & 1 & 0 & 0 & 0 \\ E7 & -E7 & 0 & -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} e1 \\ e2 \\ e3 \\ e4 \\ i6 \\ i7 \end{bmatrix} = \begin{bmatrix} 0 \\ IS5 \\ 0 \\ 0 \\ ES6 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} Y_n & B \\ C & 0 \end{bmatrix} \begin{bmatrix} e \\ i \end{bmatrix} = MS$$

node voltages

solve for some branch currents


- **MNA** matrix and **MS** can be directly assembled from the input by inspection.

Nodal Analysis Elements (3)

Floating Voltage Source: **ESK N+ N- E_k**

Stamp:


	N+	N-	i_k	RHS
N+	0	0	1	0
N-	0	0	-1	0
branch k	1	-1	0	E_k

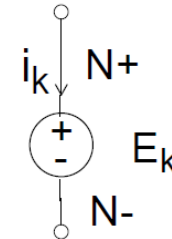

CCVS (Current controlled voltage source): **FSK N+ N- NC+ NC- F_k**

Stamp:

	N+	N-	NC+	NC-	i_k	i_j
N+					1	
N-					-1	
NC+						1
NC-						-1
branch k	1	-1				$-F_k$
branch j			1	-1		

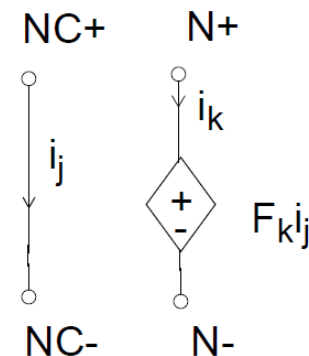

General Rules for MNA


1. A branch current is **always** introduced as an additional variable for a **voltage source** or an **inductor**.
2. For current sources, resistors, conductances, and capacitors, the branch current is introduced only if
 - any circuit element depends on that branch current
 - the branch current is requested as an output

Nodal Analysis Elements (4)

CCCS: Current controlled current source

Stamp:

	N+	N-	NC+	NC-	i_j
N+					E_j
N-					$-E_j$
NC+					1
NC-					-1
branch j			1	-1	

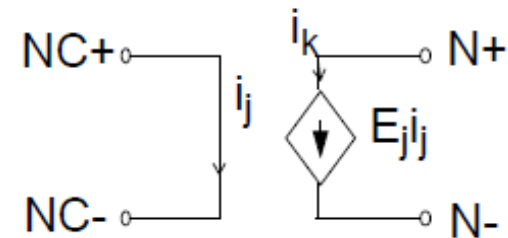

Advantages of MNA

1. MNA can be applied to any circuit.
2. MNA equations can be assembled “directly” (e.g., from SPICE input deck) from input data.
3. MNA matrix is close to Y_n .

CIRCUIT SIMULATION-2

SIMULATOR DESIGN

LU Decomposition (1)

Given $Ax = b$, decompose it into: $A = LU$, $LUx = b$

$$\begin{bmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & & \ddots & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{bmatrix} = \begin{bmatrix} l_{11} & l_{11}u_{12} & l_{11}u_{13} & \dots \\ l_{21} & l_{21}u_{12} + l_{22} & l_{21}u_{13} + l_{22}u_{23} & \dots \\ \vdots & & \ddots & \vdots \\ l_{n1} & l_{n1}u_{12} + l_{n2} & l_{n1}u_{13} + l_{n2}u_{23} + l_{n3} & \dots \end{bmatrix}$$

To find l_{ij} and u_{jk}

1st col.: $l_{i1} = a_{i1}$ for $i = 1$ to n .

2nd col.: $l_{i2} = a_{i2} - l_{i1}u_{12}$ for $i = 2$ to n .

LU Decomposition (2)

$$\text{1st row: } u_{1k} = \frac{a_{1k}}{l_{11}} \quad \text{for } k = 2 \text{ to } n$$

$$\text{2nd row: } u_{2k} = \frac{a_{2k} - l_{21}u_{1k}}{l_{22}}$$

$$(\text{Eq. 1}) \quad l_{ij} = a_{ij} - \sum_{m=1}^{j-1} l_{im}u_{mj}, \quad n \geq i \geq j$$

$$(\text{Eq. 2}) \quad u_{jk} = \frac{a_{jk} - \sum_{m=1}^{j-1} l_{jm}u_{mk}}{l_{jj}}, \quad k > j$$

Algorithm LU-Decomposition

1. Set $j = 1$ goto 3.
2. Use (Eq. 1) to compute col. j in L , if $j = n$ stop.
3. Use (Eq. 2) to compute row j in U .
4. Set $j = j+1$ goto 2.

Solution Finding (1)

To solve $\mathbf{x} = \mathbf{A}^{-1}\mathbf{b}$, we decompose $\mathbf{A} = \mathbf{LU}$ to obtain $\mathbf{LUx} = \mathbf{b}$.

Let $\mathbf{Ux} = \mathbf{z}$, we have then $\mathbf{Lz} = \mathbf{b}$

$$\mathbf{Lz} = \begin{bmatrix} l_{11} & & & \\ l_{21} & l_{22} & & \\ \vdots & & \ddots & \\ l_{n1} & l_{n2} & \cdots & l_{nn} \end{bmatrix} \begin{bmatrix} z_1 \\ z_2 \\ \vdots \\ z_n \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix}$$
$$\begin{aligned} l_{11}z_1 &= b_1 \\ l_{21}z_1 + l_{22}z_2 &= b_2 \\ &\vdots \\ l_{n1}z_1 + l_{n2}z_2 + \cdots + l_{nn}z_n &= b_n \end{aligned}$$

Solution Finding (2)

==> Forward Substitution:

$$z_1 = \frac{b_1}{l_{11}},$$

$$z_i = \frac{b_i - \sum_{m=1}^{i-1} l_{im} z_m}{l_{ii}}, \quad \text{for } i = 2 \dots n$$

Now, we can solve \mathbf{x} from $\mathbf{U}\mathbf{x} = \mathbf{z}$:

$$\mathbf{U}\mathbf{x} = \begin{bmatrix} 1 & u_{12} & u_{13} & & u_{1n} \\ & 1 & u_{23} & & u_{2n} \\ & & 1 & \dots & u_{3n} \\ & & & \ddots & \\ & & & & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ \vdots \\ x_n \end{bmatrix} = \begin{bmatrix} z_1 \\ z_2 \\ z_3 \\ \vdots \\ z_n \end{bmatrix}$$

$$\begin{aligned}
 x_1 + u_{12}x_2 + \dots + u_{1n}x_n &= z_1 \\
 x_2 + \dots + u_{2n}x_n &= z_2 \\
 &\vdots \\
 x_{n-1} + u_{n-1,n}x_n &= z_{n-1} \\
 x_n &= z_n
 \end{aligned}$$

Solution Finding (3)

$$Ux = \begin{bmatrix} 1 & u_{12} & u_{13} & & u_{1n} \\ & 1 & u_{23} & & u_{2n} \\ & & 1 & \dots & u_{3n} \\ & & & \ddots & \\ & & & & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ \vdots \\ x_n \end{bmatrix} = \begin{bmatrix} z_1 \\ z_2 \\ z_3 \\ \vdots \\ z_n \end{bmatrix}$$
$$\begin{aligned} x_1 + u_{12}x_2 + \dots + u_{1n}x_n &= z_1 \\ x_2 + \dots + u_{2n}x_n &= z_2 \\ &\vdots \\ x_{n-1} + u_{n-1,n}x_n &= z_{n-1} \\ x_n &= z_n \end{aligned}$$


==> Backward Substitution:

$$x_n = z_n$$

$$x_i = z_i - \sum_{m=i+1}^n u_{im}x_m, \quad \text{for } i = n-1, n-2, \dots, 1$$


Tree (Digraph) Representation of RLC-gm Network

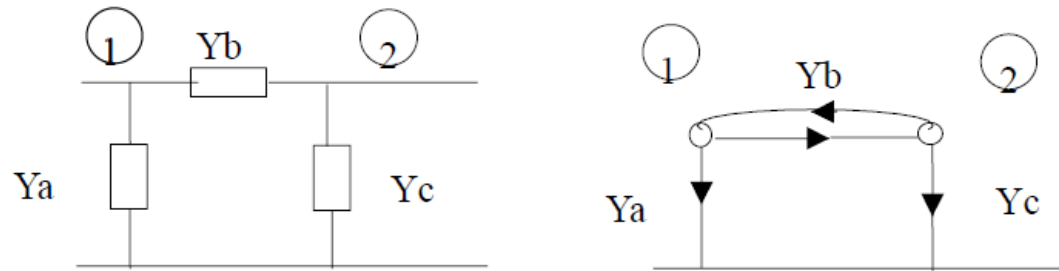Use $\mathbf{I} = \mathbf{YV}$ as example, where \mathbf{Y} is a node-admittance matrix



* Matrix representation:

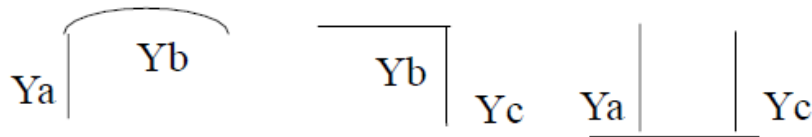
$$\mathbf{Y} = \begin{bmatrix} Y_a + Y_b & -Y_b \\ -Y_b & Y_b + Y_c \end{bmatrix}$$



$$\begin{aligned} \Delta &= Y_a Y_b + Y_a Y_c + Y_b Y_b + Y_b Y_c - Y_b Y_b \\ &= Y_a Y_b + Y_a Y_c + Y_b Y_c \end{aligned}$$

* Tree representation: $\delta = Y_a Y_b + Y_b Y_c + Y_a Y_c$

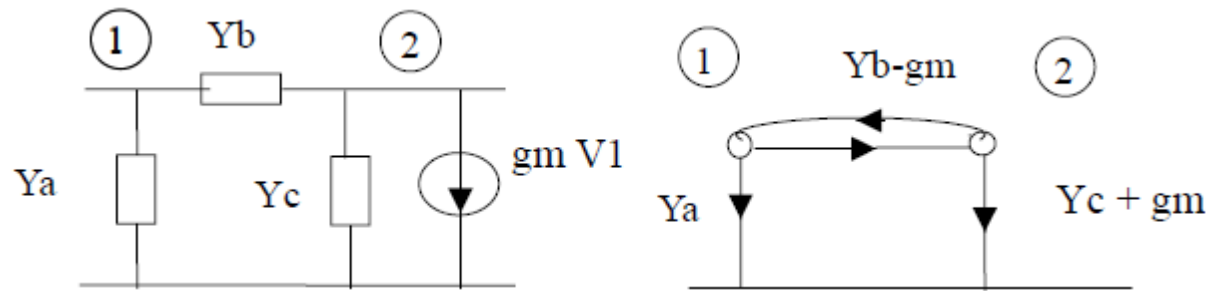
Tree Representation Example (adding a current to Y_c)



* **Matrix representation:**

$$Y = \begin{bmatrix} Y_a + Y_b & -Y_b \\ -Y_b + g_m & Y_b + Y_c \end{bmatrix} \quad \begin{aligned} \Delta &= Y_a Y_b + Y_a Y_c + Y_b Y_b + Y_b Y_c - Y_b Y_b + Y_b g_m \\ &= Y_a Y_b + Y_a Y_c + Y_b Y_c + Y_b g_m \end{aligned}$$

* **Tree representation:**

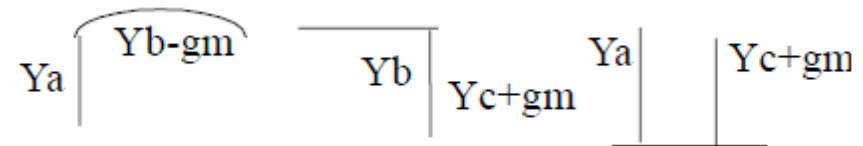


$$\delta = Y_a Y_b + Y_b Y_c + Y_a Y_c + Y_b g_m$$

* **Relationship between Δ and δ :** $\Delta_{jj} = \delta_{jj}$

$$\Delta_{jk} = \delta_{jj} - \delta_{jk}$$


Network with Voltage Source Input (1)

A. General Case (n: reference point)

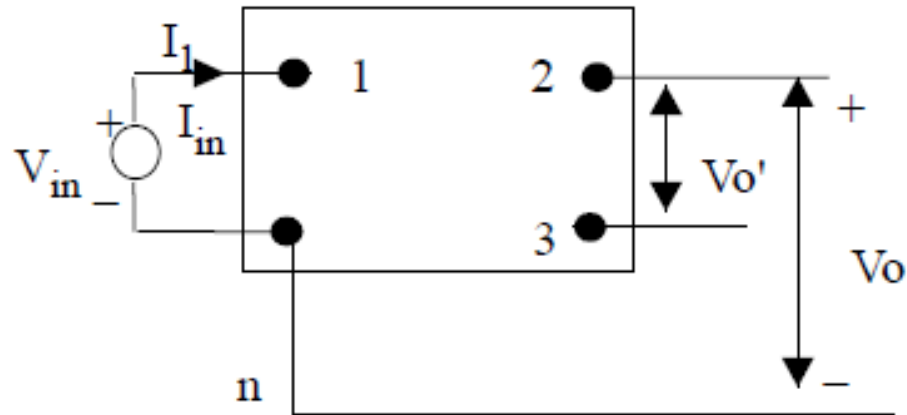


(a1) Voltage Source cases:
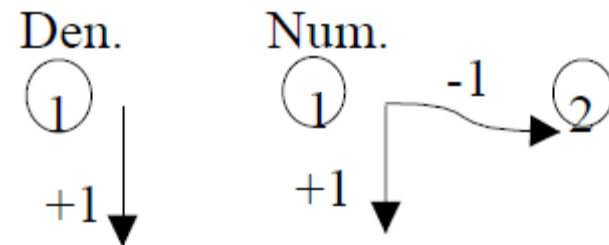
$$\begin{aligned} \frac{V_o}{V_{in}} &= \frac{V_2}{V_1} = \frac{\Delta_{12}}{\Delta_{11}} \\ &= \frac{\delta_{11} - \delta_{12}}{\delta_{11}} = \frac{\text{Numerator}}{\text{Denominator}} \end{aligned}$$





Network with Voltage Source Input (2)

A. General Case (n: reference point)

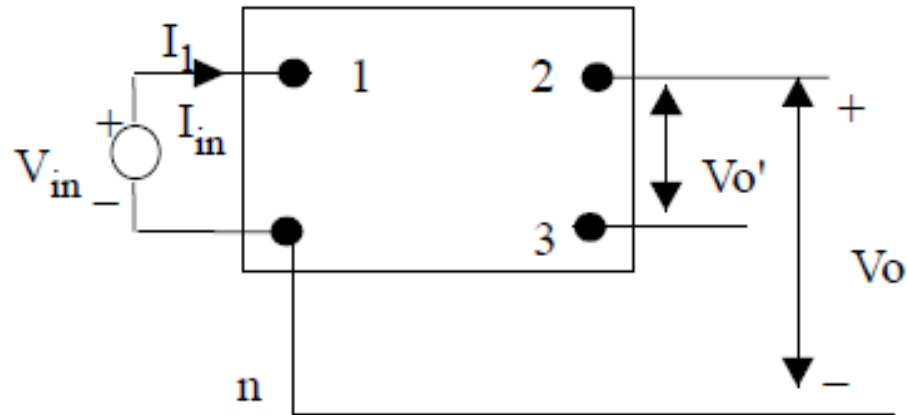


(a2) Voltage Source cases (Cont.):
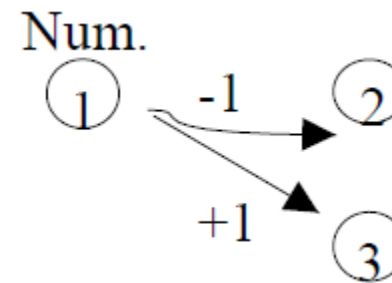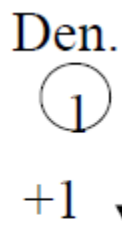
$$\begin{aligned} \frac{V_{o'}}{V_{in}} &= \frac{V_2 - V_3}{V_1} = \frac{\Delta_{12} - \Delta_{13}}{\Delta_{11}} \\ &= \frac{\delta_{13} - \delta_{12}}{\delta_{11}} = \frac{\text{Num.}}{\text{Den.}} \end{aligned}$$



Network with Current Source Input (1)

A. General Case (n: reference point)

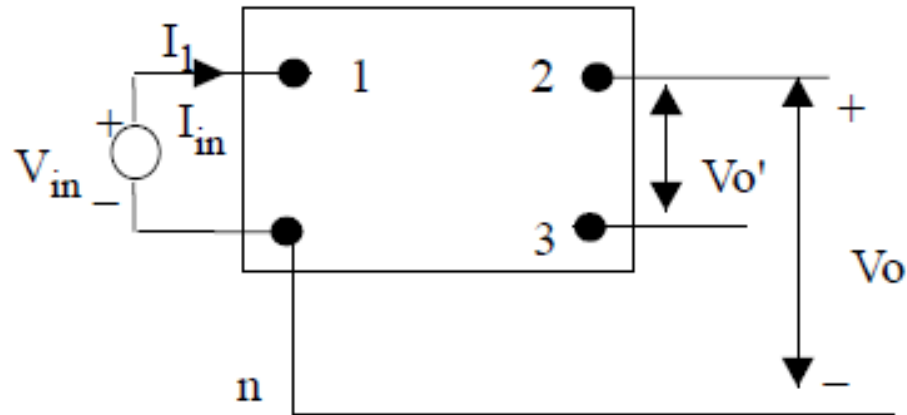


(b1) Current Source Cases:

$$\frac{V_o}{I_{in}} = \frac{V_2}{I_1} = \frac{\Delta_{12}}{\Delta}$$


$$= \frac{\delta_{11} - \delta_{12}}{\delta} = \frac{\text{Num.}}{\text{Den.}}$$

Den.
Whole
Tree

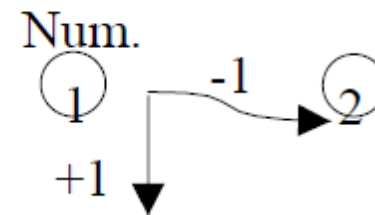

Network with Current Source Input (2)


A. General Case (n: reference point)

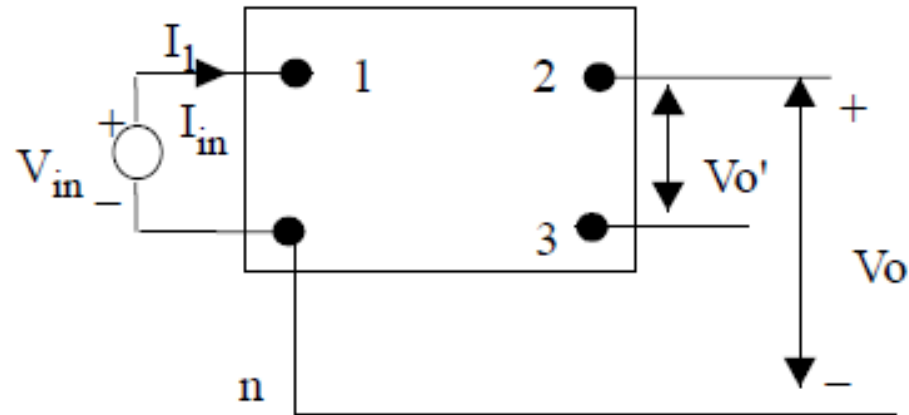


(b2) Current Source cases (Cont.):

$$\begin{aligned}\frac{V_{o'}}{I_{in}} &= \frac{V_2 - V_3}{I_1} = \frac{\Delta_{12} - \Delta_{13}}{\Delta} \\ &= \frac{\delta_{13} - \delta_{12}}{\delta} = \frac{\text{Num.}}{\text{Den.}}\end{aligned}$$

Den.
Whole
Tree

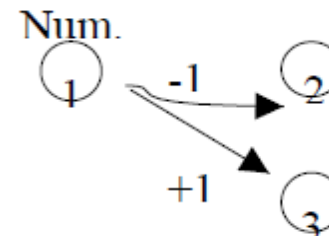

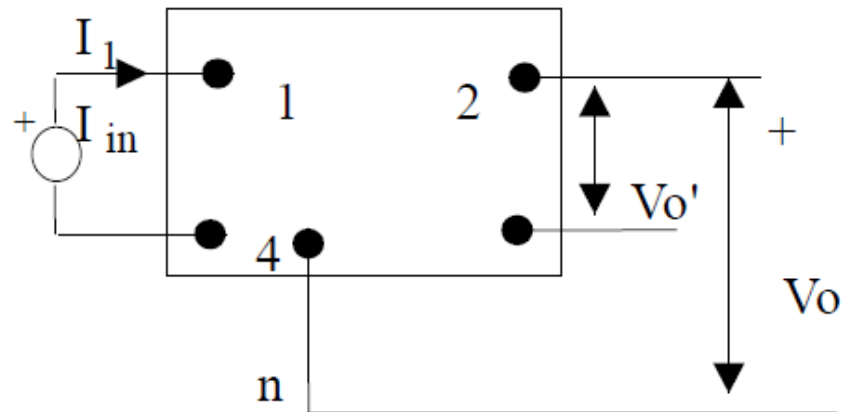
B. Special Case with Current Source not Grounded




$$\frac{V_o}{I_{in}} = \frac{V_2}{I_{14}} = \frac{\Delta_{12} - \Delta_{42}}{\Delta}$$

$$= \frac{\delta_{11} - \delta_{12} - (\delta_{44} - \delta_{42})}{\delta} = \frac{\text{Num.}}{\text{Den.}}$$


Den.
Whole
Tree

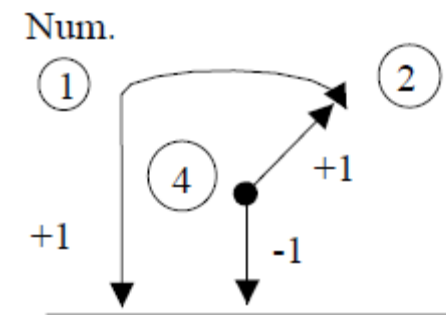

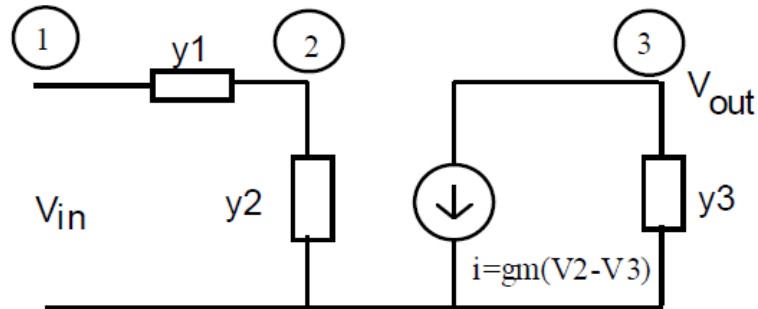Example: Use digraph to find V_{out} / V_{in} (1)



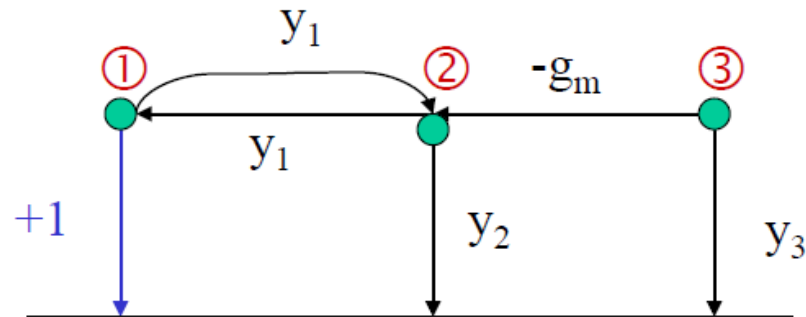
Denominator: voltage source \Rightarrow add a **+1** branch to node ①-0, and we have:



$$V_{in} = \Delta_{11} = \delta_{11} = -y_1 g_m + y_1 y_3 + y_2 y_3 - y_2 g_m \quad (a)$$

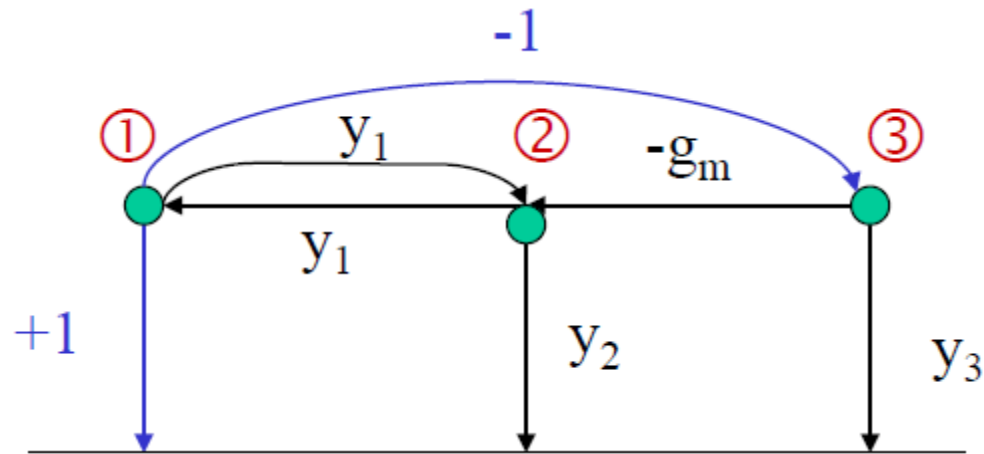Example: Use digraph to find V_{out} / V_{in} (2)

Numerator: add +1, -1 branches to nodes ①-0, ①-③,
and we have:



$$\delta_{11} = -y_1 g_m + y_1 y_3 + y_2 y_3 - y_2 g_m \quad (b)$$

$$\delta_{13} = y_2 g_m - y_2 y_3 - y_1 y_3 \quad (c)$$

$$V_{out} = \Delta_{13} = \delta_{11} - \delta_{13} = (b) - (c) = -y_1 g_m \quad (d)$$

$$\Rightarrow V_{out} / V_{in} = (d) / (a) = -y_1 g_m / (-y_1 g_m + y_1 y_3 + y_2 y_3 - y_2 g_m)$$

Newton-Raphson Algorithm and its Application (1)


Solve for $f(x) = 0$, we have

$$\Delta x = x^{j+1} - x^j = \frac{-f(x^j)}{f'(x^j)}$$

* For a diode, we have:

$$i^m = I_D = I_0 (e^{v^m/v_T} - 1)$$

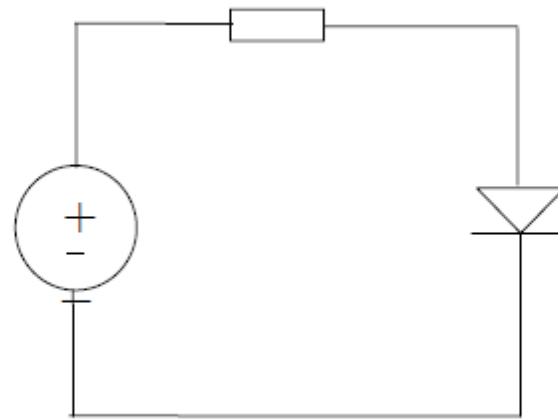
$$g_m = \frac{di^m}{dv} = \frac{I_s}{v_T} (e^{v^m/v_T})$$



Newton-Raphson Algorithm and its Application (2)

* Use N-R method to find i^{m+1} , v^{m+1} and its companion (or associated discrete circuit) models:

$$(\text{Eq. 3}) \quad i^{m+1} = (i^m - g_m v^m) + g_m v^{m+1}$$

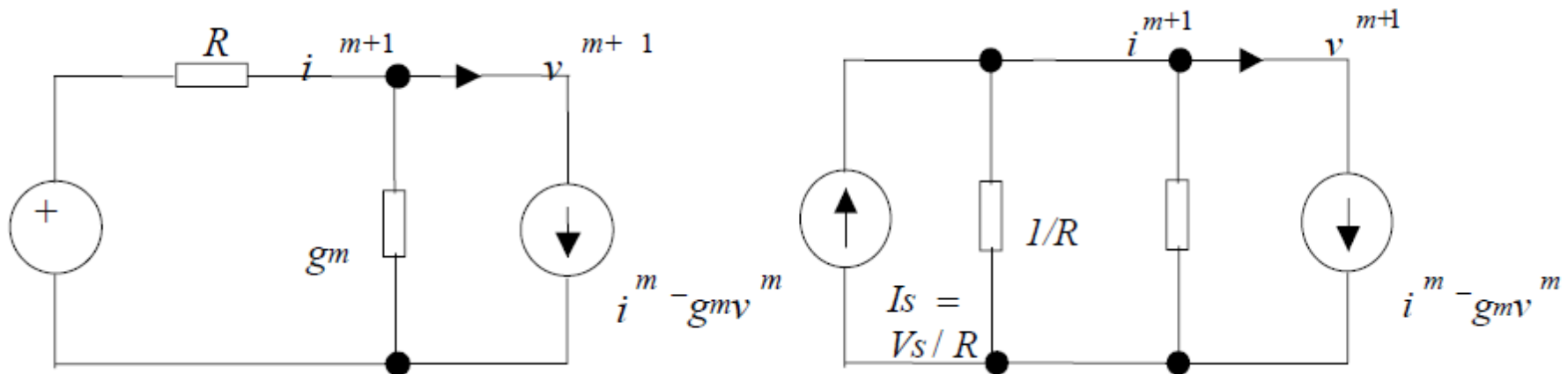

(Eq. 4)

$$v^{m+1} = \frac{I_s - (i^m - g_m v^m)}{1/R + g_m}$$

Notes


1. If given only i^m , use $i^m = I_0(e^{v^m/v_T} - 1)$ to find v^m .
2. If we want i^{m+1} , find v^{m+1} first by (Eq. 4), then use (Eq. 3) to find i^{m+1} .

Numerical Integration (1)

(1) Forward Euler (FE): slope

$$\dot{x}_n = \frac{\Delta x}{T}$$

$$x_{n+1} = x_n + T\dot{x}_n$$

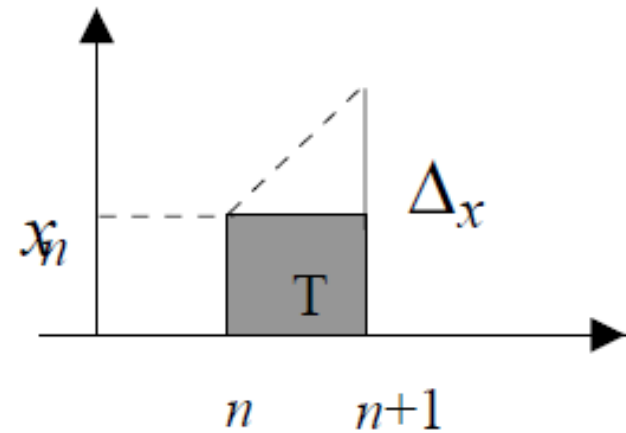


* ST-plane of FE: $ST = e^{j\theta} - 1$

Numerical Integration (2)

(2) Backward Euler (BE): slope

$$\dot{x}_{n+1} = \frac{\Delta x}{T}$$

$$x_{n+1} = x_n + T\dot{x}_{n+1}$$

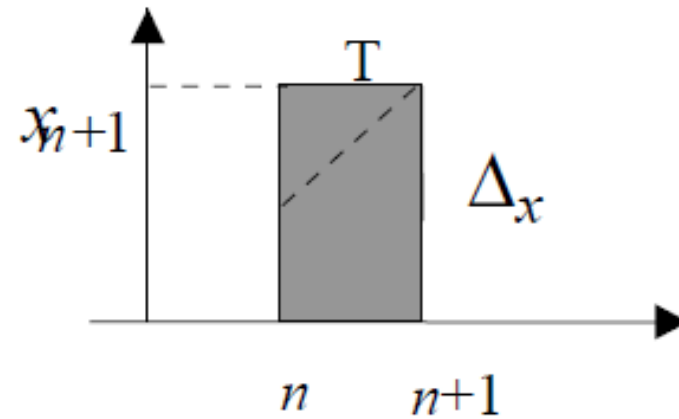


* ST plane of BE: $ST = 1 - e^{j\theta}$

Numerical Integration (3)

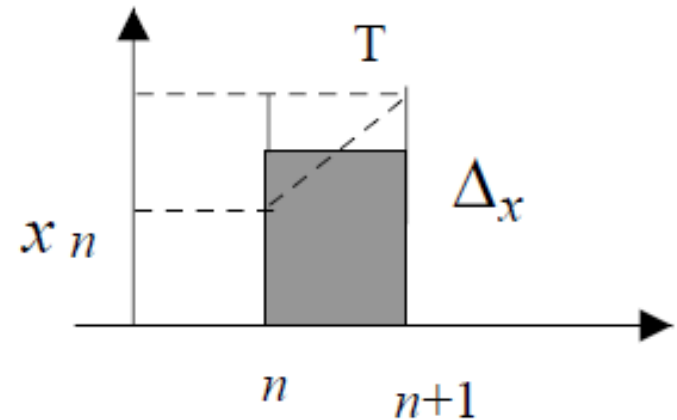(3) Trapezoid (Trap): slope

$$\frac{\dot{x}_n + \dot{x}_{n+1}}{2} = \frac{\Delta x}{T}$$

$$x_{n+1} = x_n + \frac{T}{2}(\dot{x}_n + \dot{x}_{n+1})$$



* ST plane of Trap:

$$ST = \frac{2(e^{j\theta} - 1)}{e^{j\theta} + 1} = 2j \tan \frac{\theta}{2}$$

Now, we have:

$$x_n = e^{At_n} = x(t_n)$$

$$x_{n+1} = x(t_n + T) = e^{A(t_n + T)} = e^{AT} x_n = z x_n$$

$$x_{n-1} = x(t_n - T) = e^{A(t_n - T)} = e^{-AT} x_n = z^{-1} x_n$$

$$\dot{x}_n = Ax_n = Ae^{At_n}$$

$$\dot{x}_{n+1} = Ax_{n+1}$$

(Eq. 5)

Procedure to Find ROC (Stability Problem)

1. Take z-tx of the system differential equation by (Eq. 5)

$$\text{for } x_n = e^{At_n}, x_{n+1} = e^{At} x_n, \dot{x}_n = Ax_n, \dot{x}_{n+1} = Ax_{n+1}, \dots$$

2. AT ==> ST, get Eq. for $ST = \frac{C(z+b)}{(z+a)} = \frac{C(e^{j\theta} + b)}{(e^{j\theta} + a)}$

3. Plot on ST plane for $e^{j\theta}=1, -1, j, -j, 0$ to find the curve and **Region of Convergence** (ROC) .

Or, if we can rearrange the ST formula to get

$|z| = (a+ST)/(b+ST)$. By substituting ST with $x+jy$, and by setting

$|z| = (a+x+jy) / (b+x+jy) = 1$, we can find the equation for ST plane and its ROC too.

To find Coefficients for Best Accuracy (1)

Use (Eq. 5) and $e^{AT} = (1 + AT + \frac{AT^2}{2} + \frac{AT^3}{3!} + \dots)$, we can get the answer by comparison of coefficients.

* For Forward Euler:


1. Since we have $x_{n+1} = x_n + T\dot{x}_n$,

that is, $zx_n = x_n + T(Ax_n)$, $AT = z - 1$

2. Its ST-plane: $ST = e^{j\theta} - 1 = z - 1$; $z = 1 + S_iT$


3. Thus, $|z| = |1 + S_iT| = |1 + x + jy| = 1$, or $(x+1)^2 + y^2 = 1$,

we can then plot the ROC as:

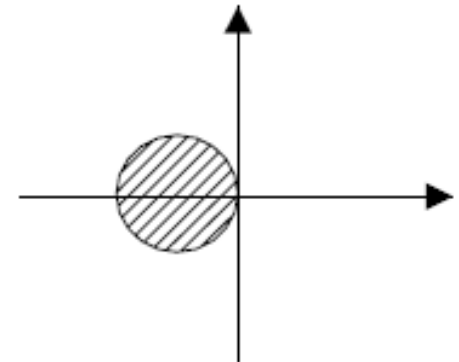


To find Coefficients for Best Accuracy (2)

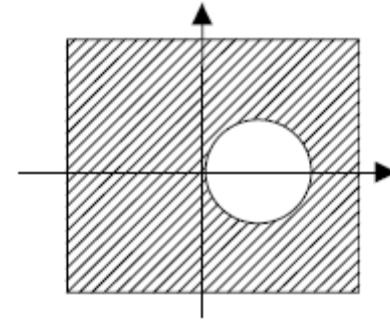* For Backward Euler: $ST = 1 - e^{-j\theta}$,



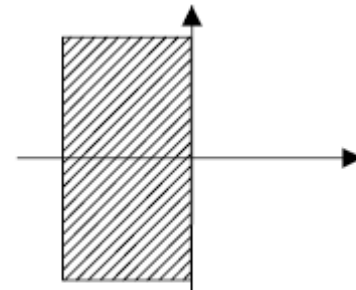* For Trap: $ST = \frac{2(e^{j\theta} - 1)}{e^{j\theta} + 1} = 2j \tan \frac{\theta}{2}$




Time Response (1)

For a general system, by defining $u_k = u_0/s^k$, we have:

$$\begin{aligned}\frac{Out}{In} &= \frac{a_0 + a_1s + a_2s^2 + \dots + a_ns^n}{b_0 + b_1s + b_2s^2 + \dots + b_ns^n} \\ &= \frac{a_0u_n + a_1u_{n-1} + a_2u_{n-2} + \dots + a_nu_0}{b_0u_n + b_1u_{n-1} + b_2u_{n-2} + \dots + b_nu_0}\end{aligned}$$

We have also:

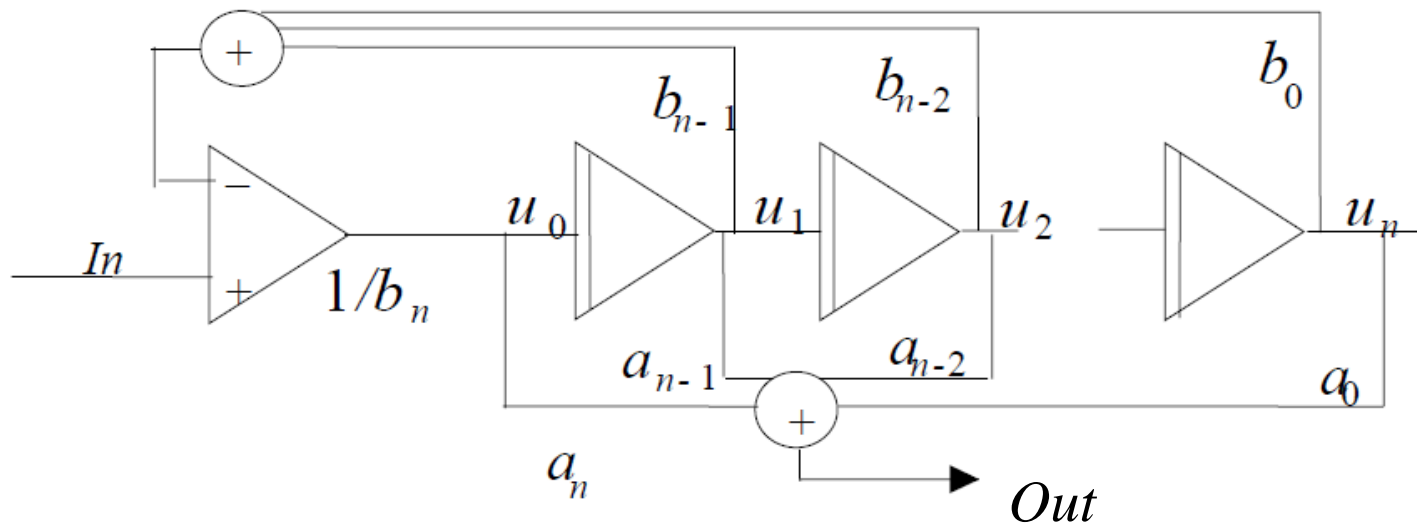

Time Response (2)

$$In = b_n u_0 + \sum_{k=1}^n b_{n-k} u_k, \quad u_0 = \left(In - \sum_{k=1}^n b_{n-k} u_k \right) / b_n$$

If we use BE:

$$\begin{aligned} u_{k,n+1} &= u_{k,n} + T \cdot u_{k-1,n+1} \\ &= u_{k,n} + \sum_{j=1}^{k-1} (T)^j \cdot u_{k-j,n} + (T)^k \cdot u_{0,n+1} \end{aligned}$$

we can then solve for BE the following (Eq. 6) :

$$u_{0,n+1} = \frac{In - \sum_{k=1}^n \left\{ b_{n-k} \left[u_{k,n} + \sum_{j=1}^{k-1} (T)^j \cdot u_{k-j,n} \right] \right\}}{\sum_{k=0}^n (T)^k \cdot b_{n-k}}$$

Time Response (3)

* Use Trapezoid, we have:

$$\begin{aligned}u_{k,n+1} &= u_{k,n} + \frac{T}{2} \cdot [u_{k-1,n} + u_{k-1,n+1}] \\&= u_{k,n} + 2 \sum_{j=1}^{k-1} \left(\frac{T}{2}\right)^j \cdot u_{k-j,n} + \left(\frac{T}{2}\right)^k \cdot [u_{0,n} + u_{0,n+1}]\end{aligned}$$

we can solve for Trap the following (Eq. 7) :

$$u_{0,n+1} = \frac{In - \sum_{k=1}^n \left\{ b_{n-k} \left[u_{k,n} + 2 \sum_{j=1}^{k-1} \left(\frac{T}{2}\right)^j \cdot u_{k-j,n} + \left(\frac{T}{2}\right)^k \cdot u_{0,n} \right] \right\}}{\sum_{k=0}^n \left(\frac{T}{2}\right)^k \cdot b_{n-k}}$$

Linear Multi-Step (LMS) Algorithm

Step 0. Set up initial values: $u_{0,n} = In(0)/b_n$,

$$u_{k,n} = 0, \text{ for } k = 1, \dots, n$$

Step 1. Find new $u_{0,n+1}$ using (Eq. 6) or (Eq. 7) .

Step 2. Find all new u_k by using old u_k and u_{k-1}

$$u_{k,n+1} = u_{k,n} + T \cdot u_{k-1,n+1} \quad \text{or}$$

$$u_{k,n+1} = u_{k,n} + \frac{T}{2} \cdot [u_{k-1,n} + u_{k-1,n+1}]$$

Step 3. Find output **time function** value by

$$Out = \sum_{k=0}^n a_{n-k} u_{k,n+1}$$

Step 4. Set $u_{k,n} = u_{k,n+1}$, for $k = 0, \dots, n$ then goto Step 1.

Frequency Response

$$F(s) = \frac{a_0 + a_1s + a_2s^2 + \dots + a_ns^n}{b_0 + b_1s + b_2s^2 + \dots + b_ns^n}$$

Substitute $s = j\omega$ into it, plot **Frequency** in Hz, **Amplitude** in DB, and **Phase** in Deg.

$$DB = 10 \log \left| \frac{V_{in}}{V_{out}} \right|^2 = 20 \log \left| \frac{V_{in}}{V_{out}} \right|$$

$$A + jB = \sqrt{A^2 + B^2} \angle \theta$$