

Computer Architecture

Ch. 3-1: Design Process & ALU Design

Fall, 2014

Sao-Jie Chen (csj@ntu.edu.tw)

The Design Process

“To Design Is To Represent”

- Design activity yields description/representation of an object

⇒ Traditional craftsman does not distinguish between the concept-utilization and the artifact

⇒ Separation comes about because of complexity

⇒ The concept is captured in one or more *representation languages*

⇒ This process IS design

- *Design Begins With Requirements*

⇒ Functional Capabilities: what it will do

⇒ Performance Characteristics: Speed, Power, Area, Cost, . . .


Design Process (cont.)

- ***Design Finishes as Assembly***

⇒ Design understood in terms of components and how they have been assembled

⇒ Top Down *decomposition* of complex functions (behaviors) into more primitive functions

 ⇒ bottom-up *composition* of primitive building blocks into more complex assemblies



- ***Design is a “creative process,” not a simple method***

Design Refinement

Informal System Requirement



Initial Specification



Intermediate Specification



Final Architectural Description



Intermediate Specification of Implementation



Final Internal Specification



Physical Implementation

**refinement
increasing level of detail**



Design as Representation (Example)

(1) Functional Specification

"VHDL Behavior"

Inputs: 2 x 16 bit operands: A, B; 1 bit carry input: Cin.

Outputs: 1 x 16 bit result: S; 1 bit carry output: Co.


Operations: PASS, ADD (A plus B plus Cin), SUB (A minus B minus Cin), AND, XOR, OR, COMPARE (equality)

Performance: left unspecified for now!

(2) Block Diagram

"VHDL Entity"

Understand the data and control flows

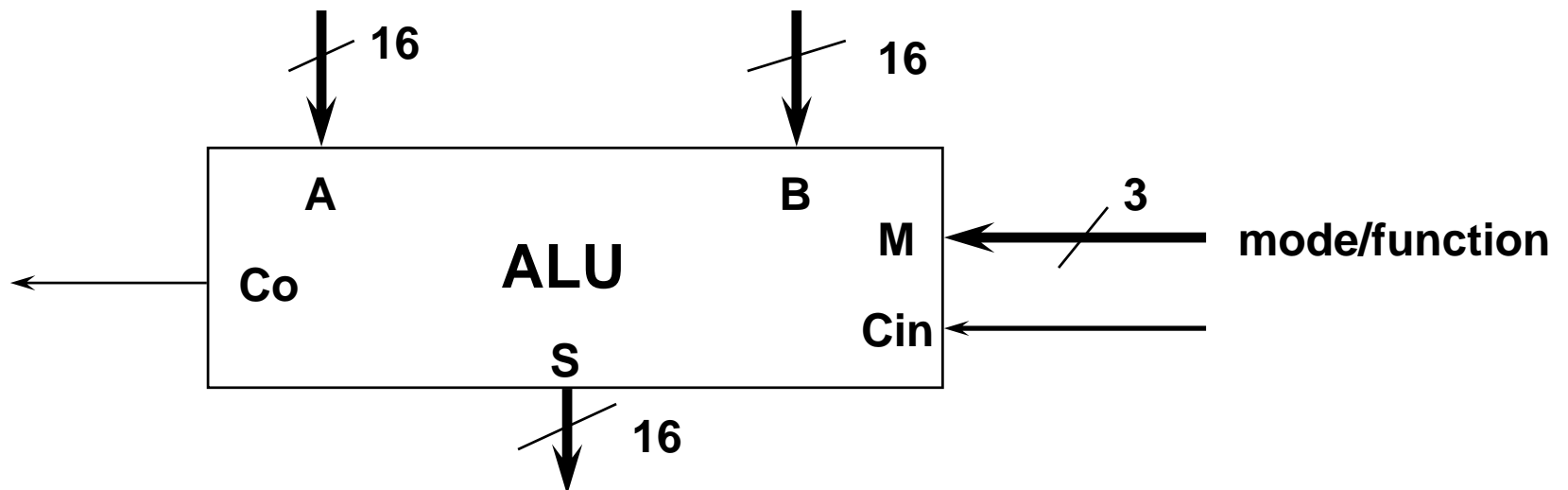

Elements of the Design Process

- **Divide and Conquer**
 - Formulate a solution in terms of simpler components.
 - Design each of the components (subproblems)
- **Generate and Test**
 - Given a collection of building blocks, look for ways of putting them together that meets requirement
- **Successive Refinement**
 - Solve *most* of the problem (i.e., ignore some constraints or special cases), examine and correct shortcomings.
- **Formulate High-Level Alternatives**
 - Articulate many strategies to *in mind* while pursuing any one approach.
- **Work on the Things you Know How to Do**
 - The unknown will become *obvious* as you make progress.

Summary of the Design Process


- Hierarchical Design to manage complexity
- Top Down vs. Bottom Up vs. Successive Refinement
- Importance of Design Representations:

Block Diagrams

Decomposition into Bit Slices

Truth Tables (TT), K-Maps

Circuit Diagrams

 

Other Descriptions: state diagrams, timing diagrams, reg xfer, . . .

- Optimization Criteria:

Gate Count

[Package Count]

Area
Pin Out

Logic Levels

Fan-in/Fan-out

Delay *Power*
Cost *Design time*


Arithmetic

- **Where we've been:**

- Performance (seconds, cycles, instructions)
- Abstractions:
 - Instruction Set Architecture
 - Assembly Language and Machine Language

- **What's up ahead:**

- Implementing the Architecture

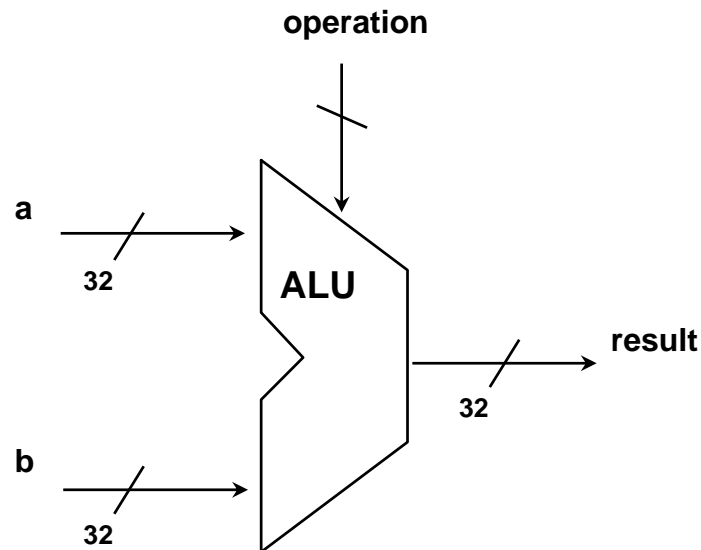

Numbers

- Bits are just bits (no inherent meaning)
⇒ conventions define relationship between bits and numbers
- Binary numbers (base 2)
0000 0001 0010 0011 0100 0101 0110 0111 1000 1001...
decimal: 0 ... $2^n - 1$
- Of course it gets more complicated:
numbers are finite (overflow)
fractions and real numbers
negative numbers
(e.g., no MIPS **subi** instruction; **addi** can add a negative number)
- How do we represent negative numbers?
i.e., which bit patterns will represent which numbers?

Possible Representations

• Signed Magnitude:	One's Complement	Two's Complement
000 = +0	000 = +0	000 = +0
001 = +1	001 = +1	001 = +1
010 = +2	010 = +2	010 = +2
011 = +3	011 = +3	011 = +3
100 = -0	100 = -3	100 = -4
101 = -1	101 = -2	101 = -3
110 = -2	110 = -1	110 = -2
111 = -3	111 = -0	111 = -1

- Issues: balance, number of zeros, ease of operations
- Which one is best? Why?

MIPS

- 32 bit signed numbers (2's Complement):

0000	0000	0000	0000	0000	0000	0000	0000	$_{\text{two}}$	=	0_{ten}	
0000	0000	0000	0000	0000	0000	0000	0001	$_{\text{two}}$	=	$+ 1_{\text{ten}}$	
0000	0000	0000	0000	0000	0000	0000	0010	$_{\text{two}}$	=	$+ 2_{\text{ten}}$	
...											
0111	1111	1111	1111	1111	1111	1111	1110	$_{\text{two}}$	=	$+ 2,147,483,646_{\text{ten}}$	/ <i>maxint</i>
0111	1111	1111	1111	1111	1111	1111	1111	$_{\text{two}}$	=	$+ 2,147,483,647_{\text{ten}}$	
1000	0000	0000	0000	0000	0000	0000	0000	$_{\text{two}}$	=	$- 2,147,483,648_{\text{ten}}$	/ <i>minint</i>
1000	0000	0000	0000	0000	0000	0000	0001	$_{\text{two}}$	=	$- 2,147,483,647_{\text{ten}}$	
1000	0000	0000	0000	0000	0000	0000	0010	$_{\text{two}}$	=	$- 2,147,483,646_{\text{ten}}$	
...											
1111	1111	1111	1111	1111	1111	1111	1101	$_{\text{two}}$	=	$- 3_{\text{ten}}$	
1111	1111	1111	1111	1111	1111	1111	1110	$_{\text{two}}$	=	$- 2_{\text{ten}}$	
1111	1111	1111	1111	1111	1111	1111	1111	$_{\text{two}}$	=	$- 1_{\text{ten}}$	

Two's Complement Representation

- 2's complement representation of negative numbers
 - Bitwise inverse and add 1
 - The MSB is always **1** for negative number => sign bit

• Biggest 4-bit Binary Number: 7

Smallest 4-bit Binary Number: -8

Decimal	Binary	Decimal	Bitwise Inverse	2's Complement
0	0000	0	1111	0000
1	0001	-1	1110	1111
2	0010	-2	1101	1110
3	0011	-3	1100	1101
4	0100	-4	1011	1100
5	0101	-5	1010	1011
6	0110	-6	1001	1010
7	0111	-7	1000	1001
8	1000	-8	0111	1000

“illegal” Positive Number!

Two's Complement Arithmetic

Decimal	Binary
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111

Decimal	2's Complement
0	0000
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001
-8	1000

• Examples: $7 - 6 = 7 + (-6) = 1$

$$\begin{array}{r}
 1 1 1 \\
 0 1 1 \\
 + 1 0 1 \\
 \hline
 0 0 1
 \end{array}$$

$3 - 5 = 3 + (-5) = -2$

$$\begin{array}{r}
 1 1 \\
 0 1 1 \\
 + 1 0 1 \\
 \hline
 1 1 0
 \end{array}$$

Two's Complement Operations


- **Negating a two's complement number: invert all bits and add 1**
 - remember: *negate* and *invert* are quite different!
- **Converting n bit numbers into numbers with more than n bits:**
 - MIPS 16 bit immediate gets converted to 32 bits for arithmetic
 - copy the most significant bit (the sign bit) into the other bits

0010 -> 0000 0010

1010 -> 1111 1010

- "sign extension" (lbu vs. lb)

Functional Specification of the ALU

 

• ALU Control Lines (ALUop)

000

001

010

110

111

Function

And

Or


Add

Subtract

Set-on-less-than

Review: The Multiplexor

 - Selects one of the inputs to be the output, based on a control input




*Note: we call this a 2-input mux
even though it has 3 inputs!*

- Let's build our ALU using a MUX:

Different Implementations

 - Not easy to decide the “best” way to build something
 - Don't want too many inputs to a single gate
 - Don't want to have to go through too many gates
 - for our purposes, ease of comprehension is important
- Let's look at a 1-bit ALU (FA) for addition:




$$c_{out} = a b + a c_{in} + b c_{in}$$
$$sum = a \text{ xor } b \text{ xor } c_{in}$$

- How could we build a 1-bit ALU for add, and, and or?
- How could we build a 32-bit ALU?


A One-bit ALU

 - This 1-bit ALU will perform AND, OR, and ADD



A One-bit Full Adder

 - This is also called a (3, 2) adder
- Half Adder: No CarryIn nor CarryOut
- Truth Table:



3 Inputs			2 Outputs		Comments
A	B	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00$
0	0	1	0	1	$0 + 0 + 1 = 01$
0	1	0	0	1	$0 + 1 + 0 = 01$
0	1	1	1	0	$0 + 1 + 1 = 10$
1	0	0	0	1	$1 + 0 + 0 = 01$
1	0	1	1	0	$1 + 0 + 1 = 10$
1	1	0	1	0	$1 + 1 + 0 = 10$
1	1	1	1	1	$1 + 1 + 1 = 11$

Logic Equation for CarryOut

Inputs			Outputs		Comments
A	B	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00$
0	0	1	0	1	$0 + 0 + 1 = 01$
0	1	0	0	1	$0 + 1 + 0 = 01$
0	1	1	1	0	$0 + 1 + 1 = 10$
1	0	0	0	1	$1 + 0 + 0 = 01$
1	0	1	1	0	$1 + 0 + 1 = 10$
1	1	0	1	0	$1 + 1 + 0 = 10$
1	1	1	1	1	$1 + 1 + 1 = 11$

- $\text{CarryOut} = (!A \& B \& \text{CarryIn}) \mid (A \& !B \& \text{CarryIn}) \mid (A \& B \& !\text{CarryIn}) \mid (A \& B \& \text{CarryIn})$
- $\text{CarryOut} = B \& \text{CarryIn} \mid A \& \text{CarryIn} \mid A \& B$

Logic Equation for Sum

Inputs			Outputs		Comments
A	B	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00$
0	0	1	0	1	$0 + 0 + 1 = 01$
0	1	0	0	1	$0 + 1 + 0 = 01$
0	1	1	1	0	$0 + 1 + 1 = 10$
1	0	0	0	1	$1 + 0 + 0 = 01$
1	0	1	1	0	$1 + 0 + 1 = 10$
1	1	0	1	0	$1 + 1 + 0 = 10$
1	1	1	1	1	$1 + 1 + 1 = 11$

- $$\text{Sum} = (!A \& !B \& \text{CarryIn}) \mid (!A \& B \& !\text{CarryIn}) \mid (A \& !B \& !\text{CarryIn}) \mid (A \& B \& \text{CarryIn})$$


Logic Equation for Sum (continued)

- $\text{Sum} = (!A \& !B \& \text{CarryIn}) \mid (!A \& B \& !\text{CarryIn}) \mid (A \& !B \& !\text{CarryIn}) \mid (A \& B \& \text{CarryIn})$
- $\text{Sum} = A \text{ XOR } B \text{ XOR } \text{CarryIn}$
- Truth Table for XOR:


X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

Logic Diagrams for CarryOut and Sum

- **CarryOut = B & CarryIn | A & CarryIn | A & B**

 


- **Sum = A XOR B XOR CarryIn**

 


A 4-bit ALU



1-bit ALU

 

4-bit ALU

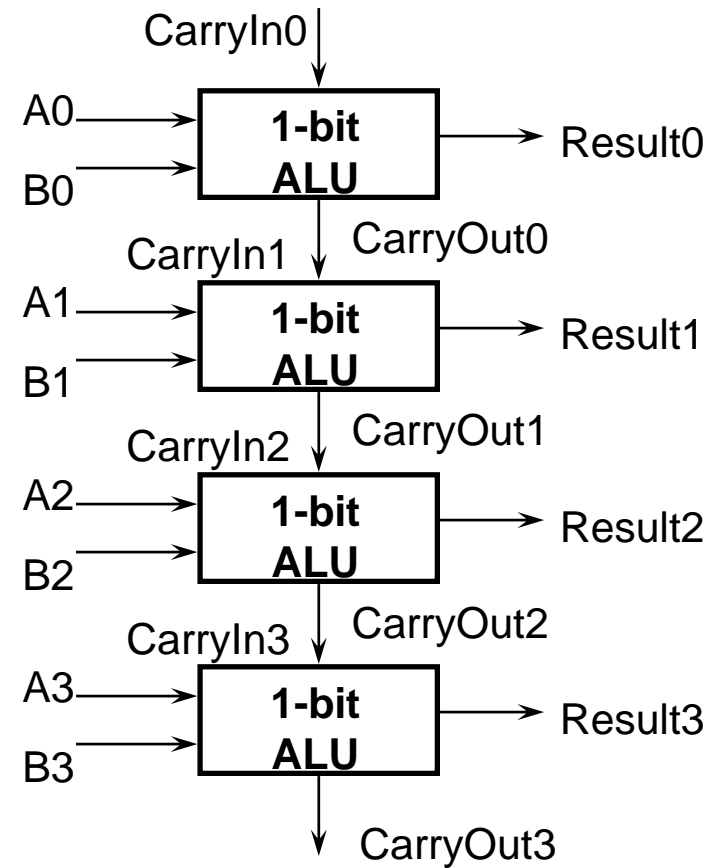


Building a 32-bit ALU

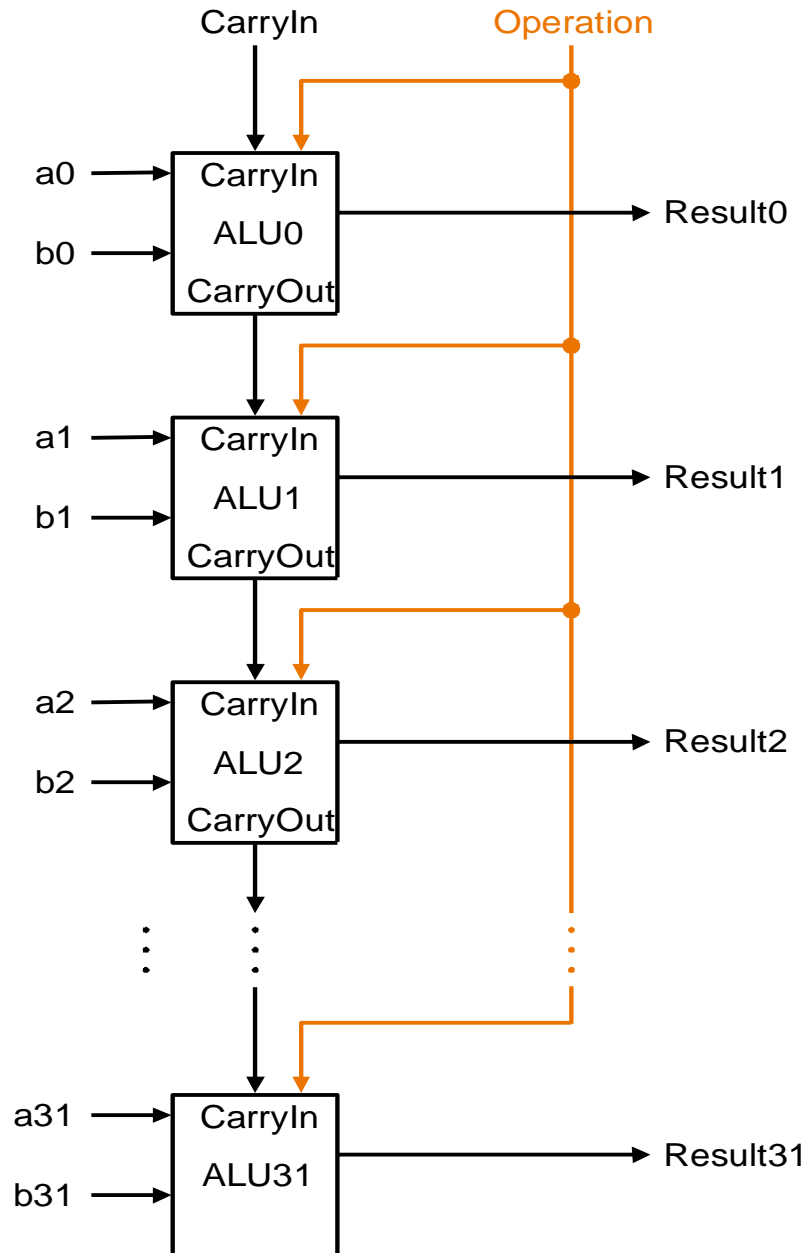 

How About Subtraction?

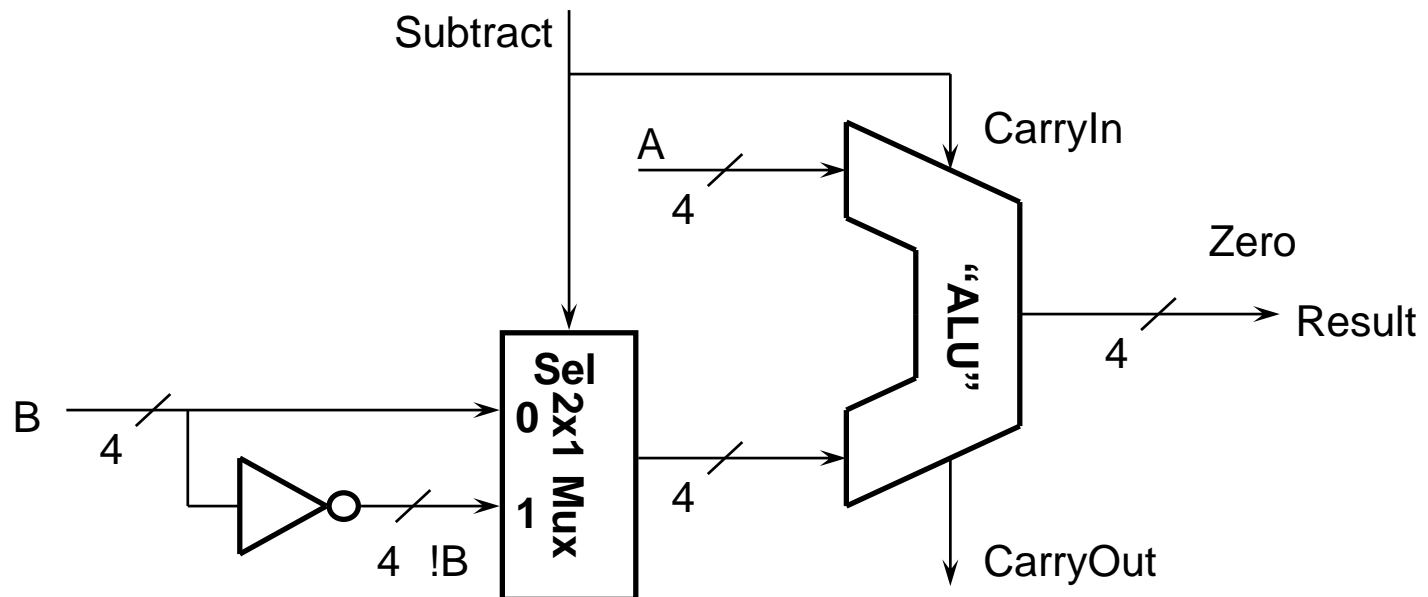- Keep in mind the following:
 - $(A - B)$ is the same as: $A + (-B)$
 - 2's Complement: Take the inverse of every bit and add 1
- Bit-wise inverse of B is !B:
 - $A + !B + 1 = A + (!B + 1) = A + (-B) = A - B$



What about subtraction ($a - b$) ?

- Two's complement approach: just negate b and add.
- How do we negate?
- A very clever solution:

