

Lecture 12



Date: March 1st, 2011

Sao-Jie Chen

Today

- SR latch
- Develop SR master–slave flip-flop
- Clock
- Type of flip-flop clocking:
 - positive-edge, negative-edge, master-slave
- Reading sequential circuits

 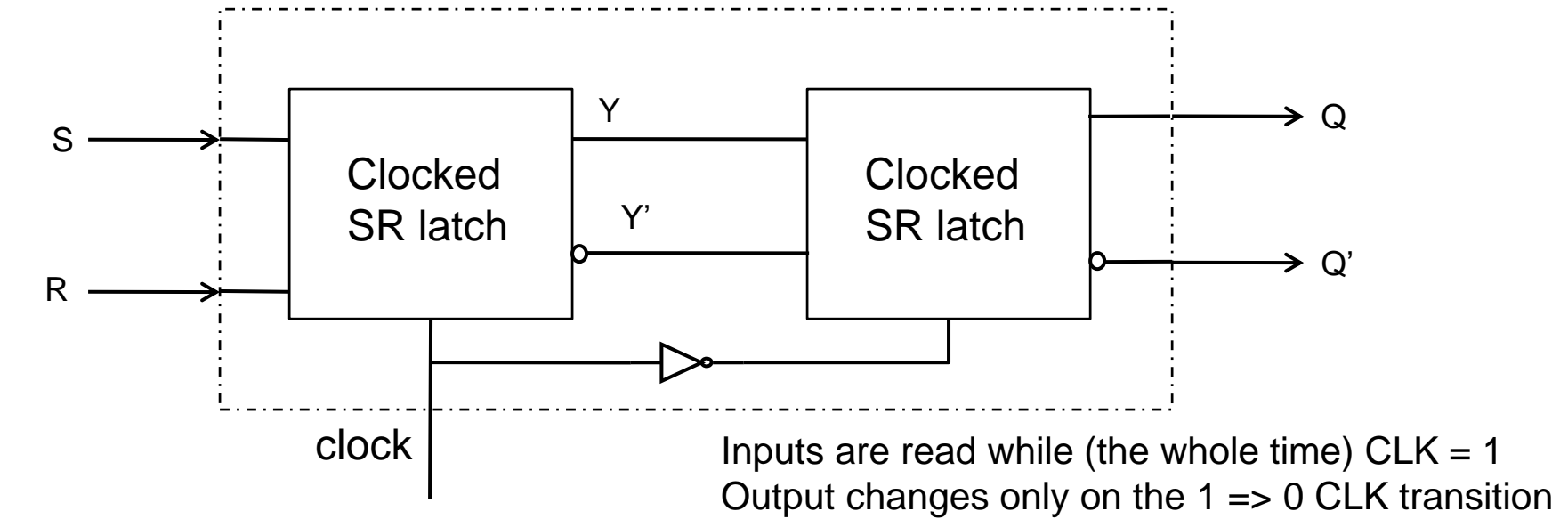Review: a Clocking Solution: Master-Slave



Types of Flip-Flops

D Flip-Flop				
Next-State Table		Excitation Table		
D	Q^+	$Q \ Q^+$	D	
0	0	0 0	0	
1	1	0 1	1	
		1 0	0	
		1 1	1	

T Flip-Flop				
Next-State Table		Excitation Table		
T	Q^+	$Q \ Q^+$	T	
0	Q	0 0	0	
1	Q'	0 1	1	
		1 0	1	
		1 1	0	

SR Flip-Flop				
Next-State Table		Excitation Table		
S R	Q^+	$Q \ Q^+$	S	R
0 0	Q	0 0	0	x
0 1	0	0 1	1	0
1 0	1	1 0	0	1
1 1	?	1 1	x	0

JK Flip-Flop				
Next-State Table		Excitation Table		
J K	Q^+	$Q \ Q^+$	J	K
0 0	Q	0 0	0	x
0 1	0	0 1	1	x
1 0	1	1 0	x	1
1 1	Q'	1 1	x	0

Combinational vs. Sequential Circuits

Combinational:

1. **No** memory
2. Output a function only of current inputs
3. Build using only combinational components (**AND, OR, NOT** gates, etc.)

Sequential:

1. **Has** memory
2. Output a function of current inputs **& previous inputs**
3. Build using only combinational components **& storage elements** (**latches, FF's**)

State of a Sequential Circuit

The state is the binary information stored at any given time.


Synchronous Circuits

All storage elements are **clocked**: their states change simultaneously at fixed intervals, specified by a period input called **clock**.


Clocking Requirements

- Clock period must be long enough for network to stabilize
- Clock pulse must be long enough to provide sufficient switching energy to the flip-flops

Actual case master-slave flip-flop

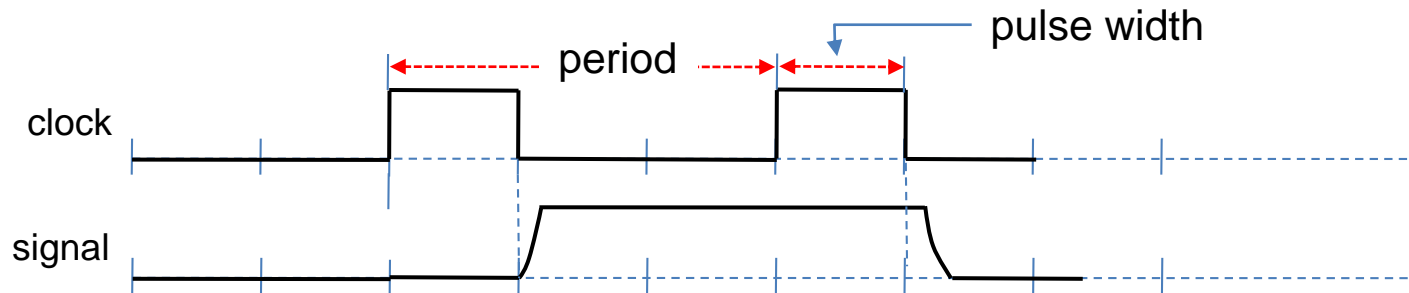


Ideal model (ideal clock)

 


Flip-Flop Clocking (1)

 A **master-slave flip-flop** changes state on the **falling CLK edge**, based on the S and R values while CLK = 1 and immediately prior to 1 \Rightarrow 0 CLK transition




 A **positive-edge-triggered flip-flop** changes state on the rising CLK edge, based on the S and R values immediately prior to 0 \Rightarrow 1 CLK transition




Flip-Flop Clocking (2)

 A *negative-edge-triggered flip-flop* changes state on the falling CLK edge, based on the S and R values immediately prior to 1 \Rightarrow 0 CLK transition




Types of flip-flops


master-slave

 

positive-edge

 


negative-edge

 


Types of Flip-flop Clocking



master-slave

 

positive-edge

 


negative-edge

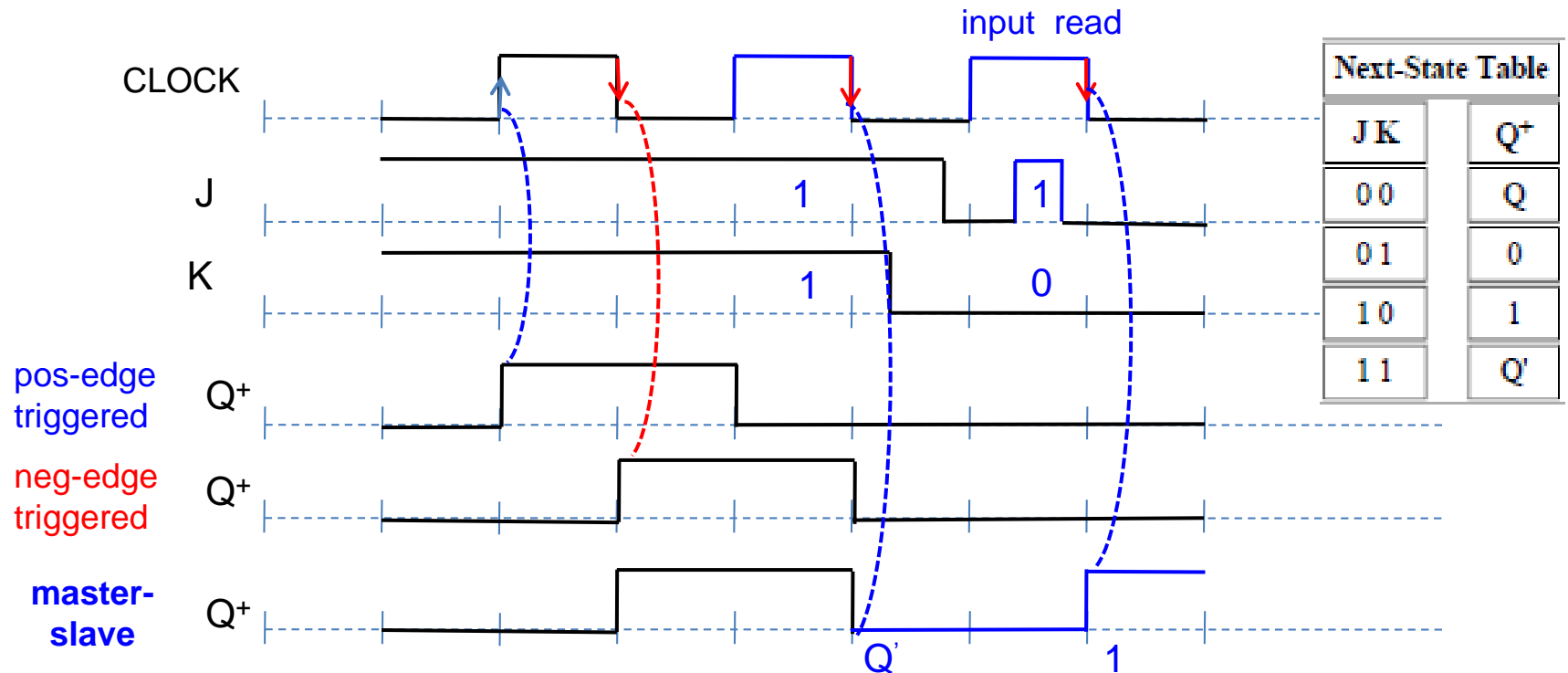 

Assume initially Q = 0


State Variables vs. States

 


- **State** in a sequential circuit is the binary information stored at any given time.
- **When state changes occur?**
 - only at the clock pulse
- **When can output change?**
 - when the state changes
 - or
 - when the inputs change
- **How many states are there?**
 - 1 FF => 1 state var, 2 states: 0, 1
 - 2 FFs => 2 state var's, 4 states: 00, 01, 10, 11
 - 3 FFs => 3 state var's, 8 states: 000, 001, ..., 111

Simple Sequential Circuit Timing Diagram

D Flip-Flops

 


Assume:
 $A = B = C = 0$

 

Sequential Network Analysis Example

D Flip-Flops

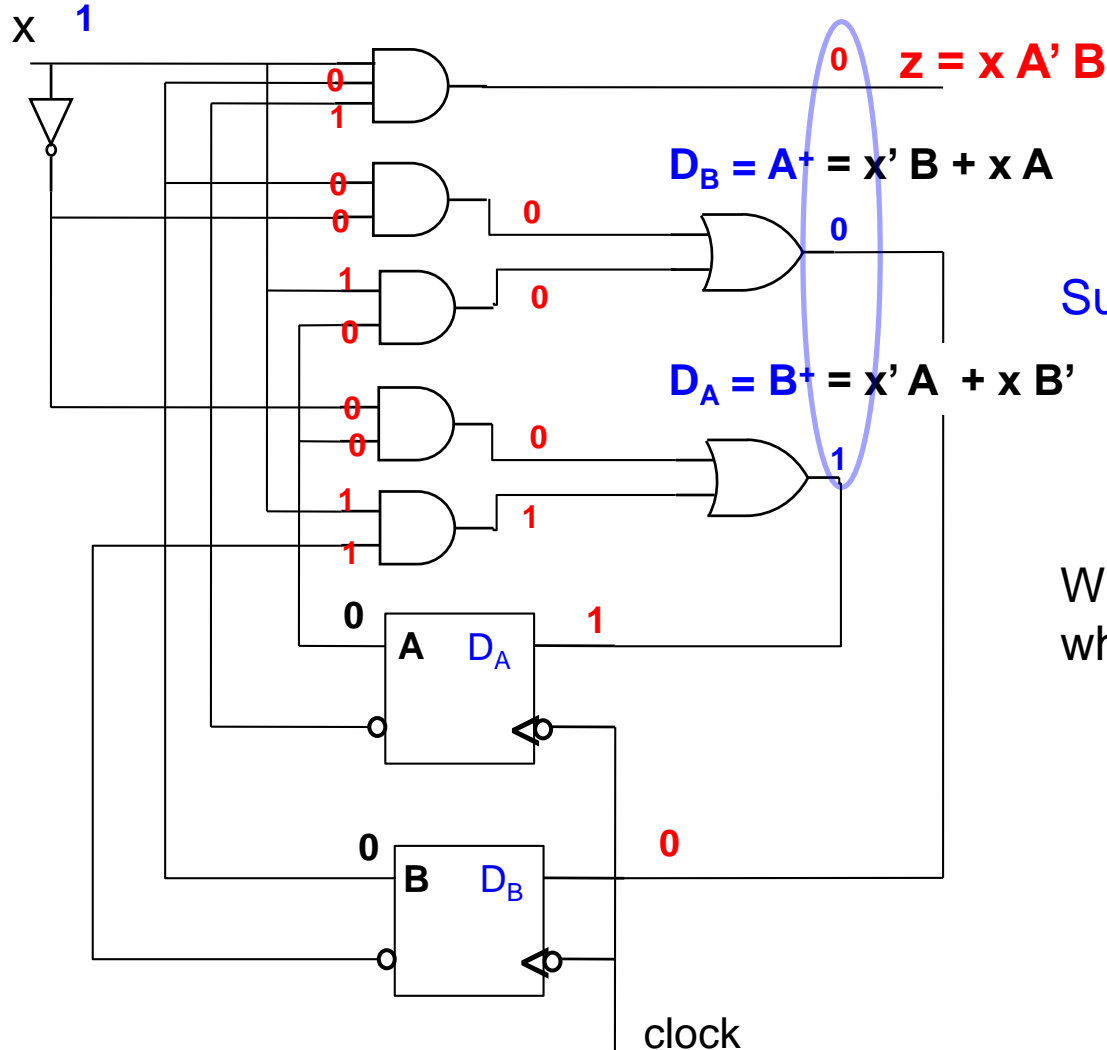

Suppose we are in **state 00** and **x=1**

A	B	x
0	0	1

What is our **current output** and what will be the **next state**?

A ⁺	B ⁺	z
1	0	0

Sequential Network Analysis Example

D Flip Flops (cont.)

Flip-flop inputs:

$$D_A = x' A + x B'$$

$$D_B = x' B + x A$$


Flip-flop outputs:

$$z = x B A'$$

Next state table:

Current state input			FF inputs		Next state		output
A	B	x	D _A	D _B	A ⁺	B ⁺	z
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	1	0	1	0
0	1	1	0	0	0	0	1
1	0	0	1	0	1	0	0
1	0	1	1	1	1	1	0
1	1	0	1	1	1	1	0
1	1	1	0	1	0	1	0

State diagram:

 

States: **AB** or **A⁺B⁺**

Label: **x/z** (input/output)



Sequential Network Analysis Example (cont.)

What does this circuit do?

Examine a timing diagram

Given **input x**, determine **output z** and the sequence of states

Assume initial state is 00

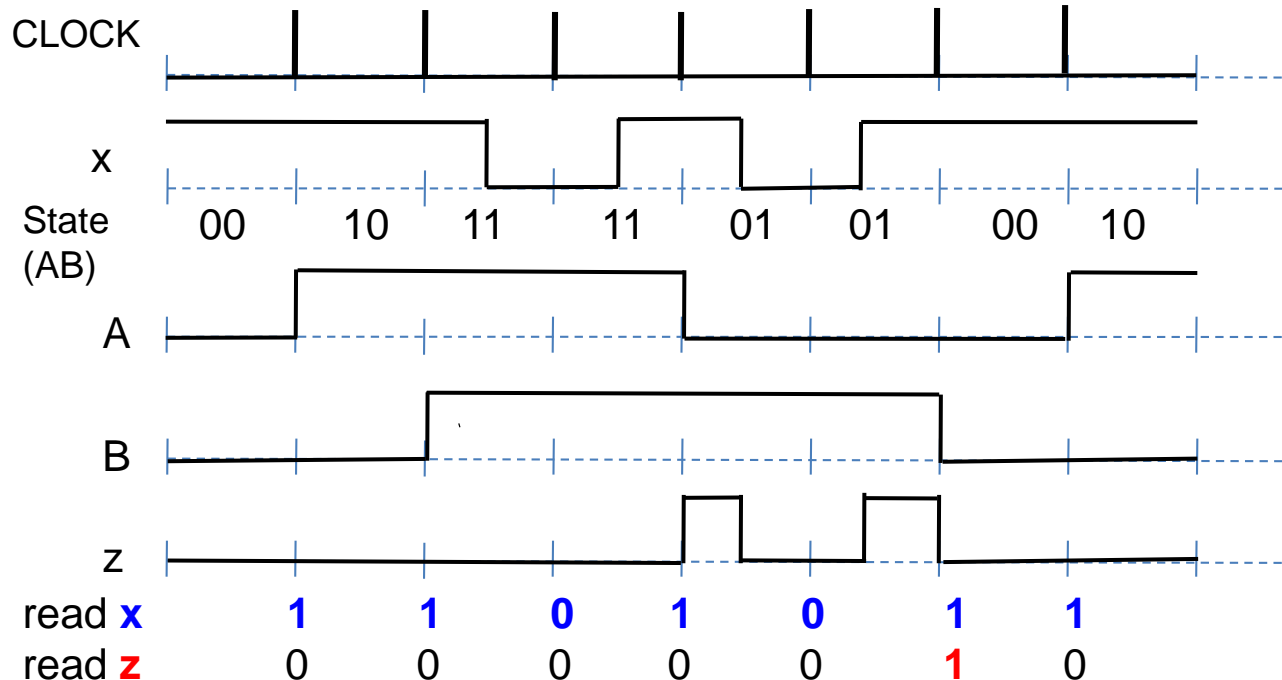 

Meaning of states:

00 start, read 4 1's, 8 1's ...

01 read 11, 7 1's, 11 1's ...


11 read 11, 6 1's, 10 1's, ...

10 read 1, 5 1's, 9 1's, ...

z = 1 when the number of 1's read thus far is $0 \bmod 4$ (and ≥ 4)

Sequential Network Analysis Example

JK Flip-Flops

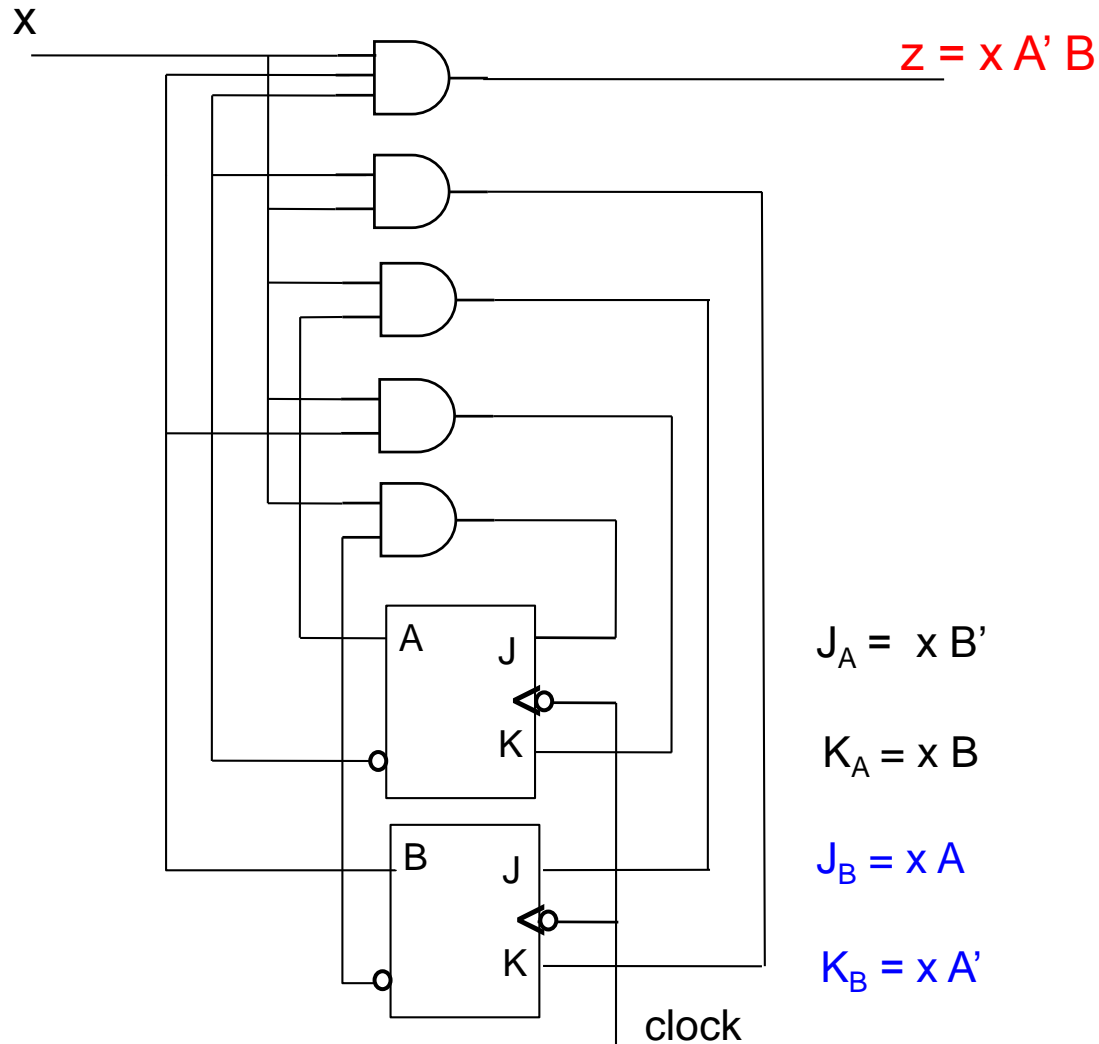

Sequential Network Analysis Example

JK Flip Flops (cont.)

Flip-flop inputs:

$$J_A = x B' \quad J_B = x A$$


$$K_A = x B \quad K_B = x A'$$

Flip-flop outputs:

$$z = x A' B$$

Next state table:

Current state input			FF inputs				Next state		output
A	B	x	J _A	K _A	J _B	K _B	A ⁺	B ⁺	z
0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	1	1	0	0
0	1	0	0	0	0	0	0	1	0
0	1	1	0	1	0	1	0	0	1
1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	1	0	1	1	0
1	1	0	0	0	0	0	1	1	0
1	1	1	0	1	1	0	0	1	0

 

Does the same thing
as our previous example:

**The state diagram
would be identical !**