


Computer Architecture

Ch. 5-3: Designing a Multiple Cycle Processor


Spring, 2005

Sao-Jie Chen (csj@cc.ee.ntu.edu.tw)


Recap: Instruction Fetch Unit

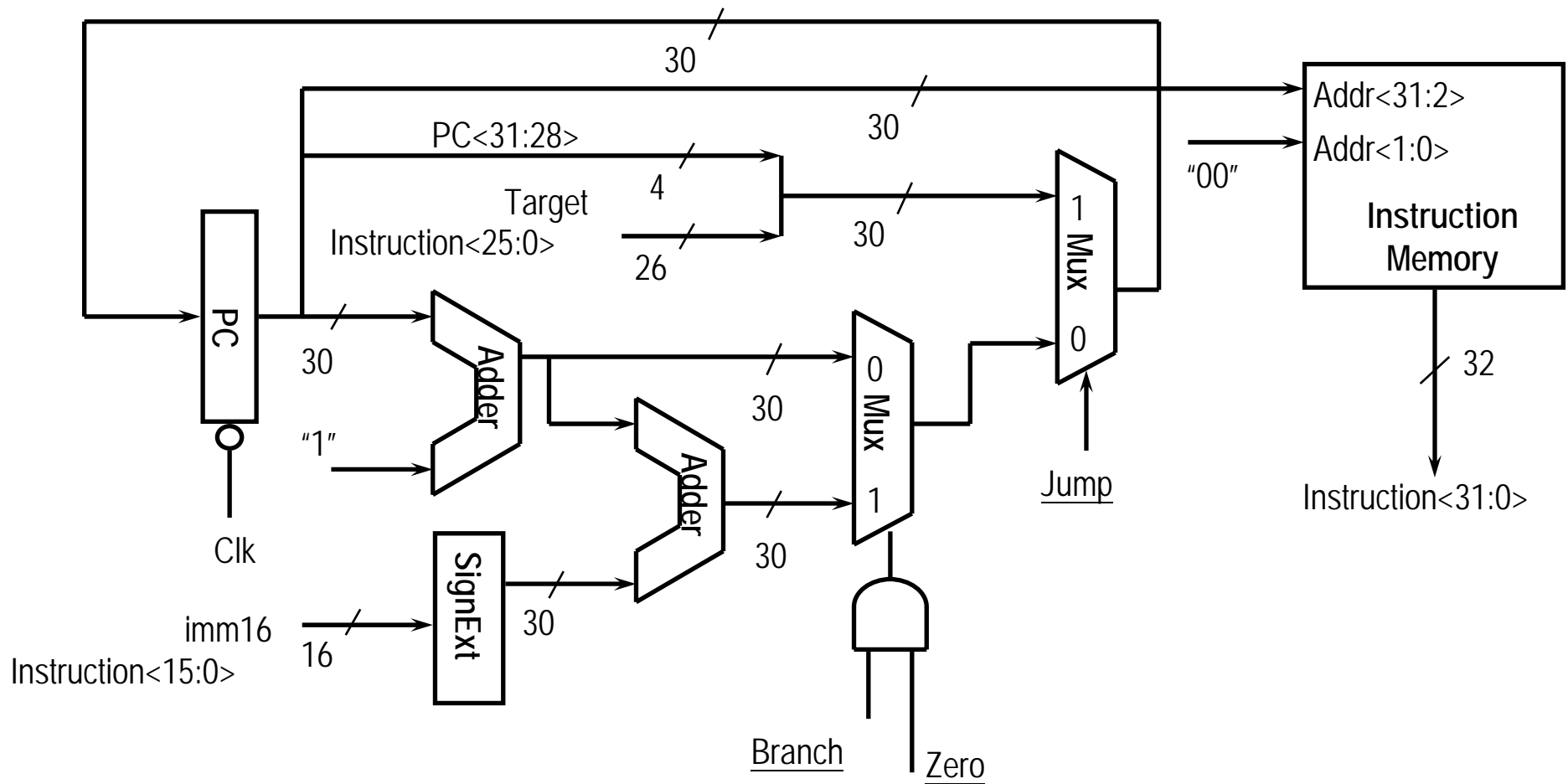

Recap: A Single Cycle Processor

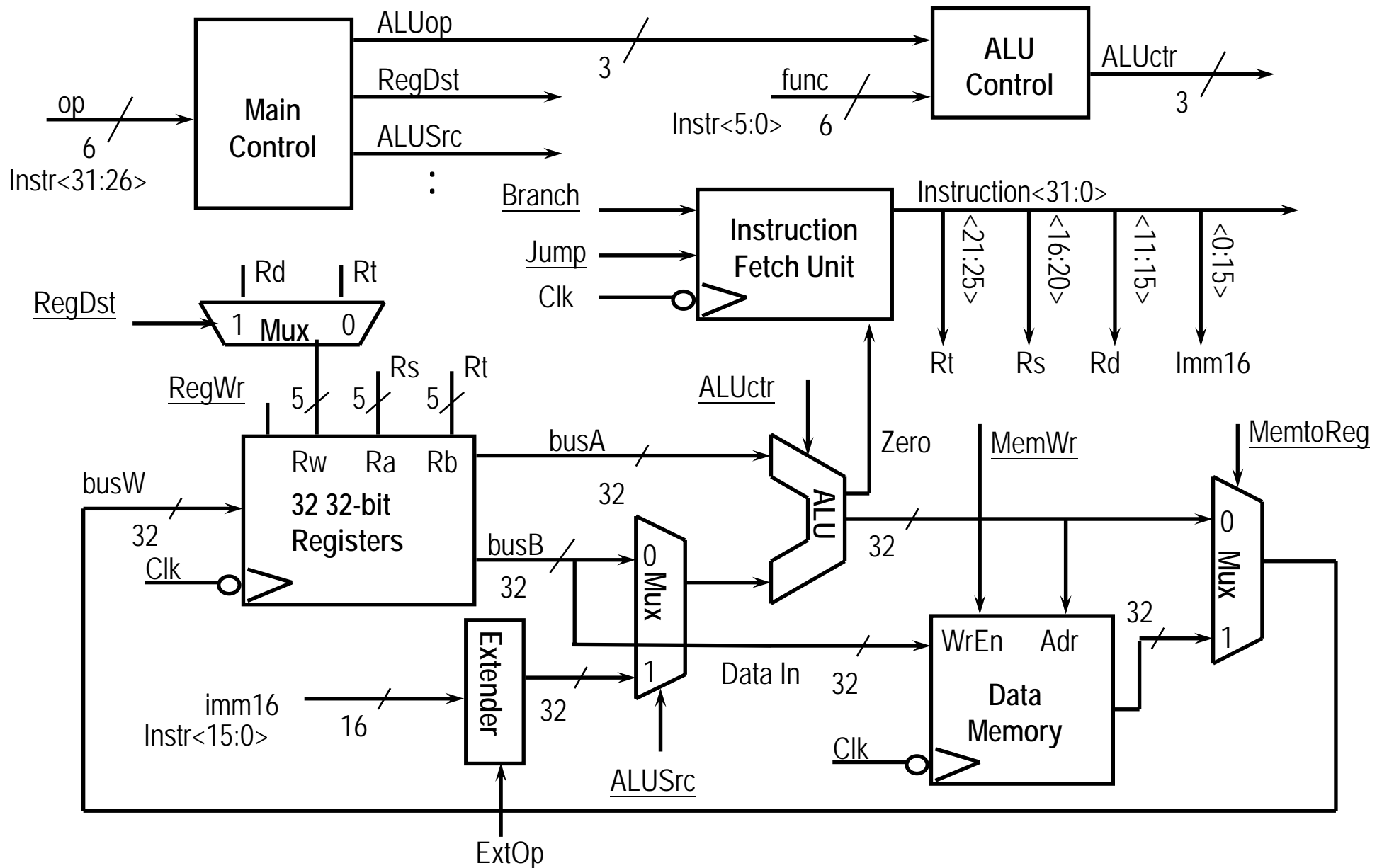

Recap: The Main Control

 

Drawbacks of this Single Cycle Processor

- Long cycle time:
 - Cycle time must be long enough for the load instruction:
 - ⇒ PC's Clock -to-Q +
 - ⇒ Instruction Memory Access Time +
 - ⇒ Register File Access Time +
 - ⇒ ALU Delay (address calculation) +
 - ⇒ Data Memory Access Time +
 - ⇒ Register File Setup Time +
 - ⇒ Clock Skew
- Cycle time is much longer than needed for all other instructions.
Examples:
 - R-type instructions do not require data memory access
 - Jump does not require ALU operation nor data memory access

Overview of a Multiple Cycle Implementation


- The root of the single cycle processor's problems:
 - The cycle time has to be long enough for the slowest instruction
- **Solution:**
 - Break the instruction into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
 - ⇒ **Cycle time:** time it takes to execute the longest step
 - ⇒ Keep all the steps to have similar length
 - This is the essence of the multiple cycle processor
- The advantages of the multiple cycle processor:
 - Cycle time is much shorter
 - Different instructions take different number of cycles to complete
 - ⇒ Load takes **five** cycles
 - ⇒ Jump only takes **three** cycles
 - Allows a functional unit to be used more than once per instruction

Multicycle Approach


- We will be reusing functional units
 - ALU used to compute address and to increment PC
 - Memory used for instruction and data
- Our control signals will not be determined solely by instruction
 - e.g., what should the ALU do for a *subtract* instruction?
- We'll use a finite state machine for control

Multicycle Approach

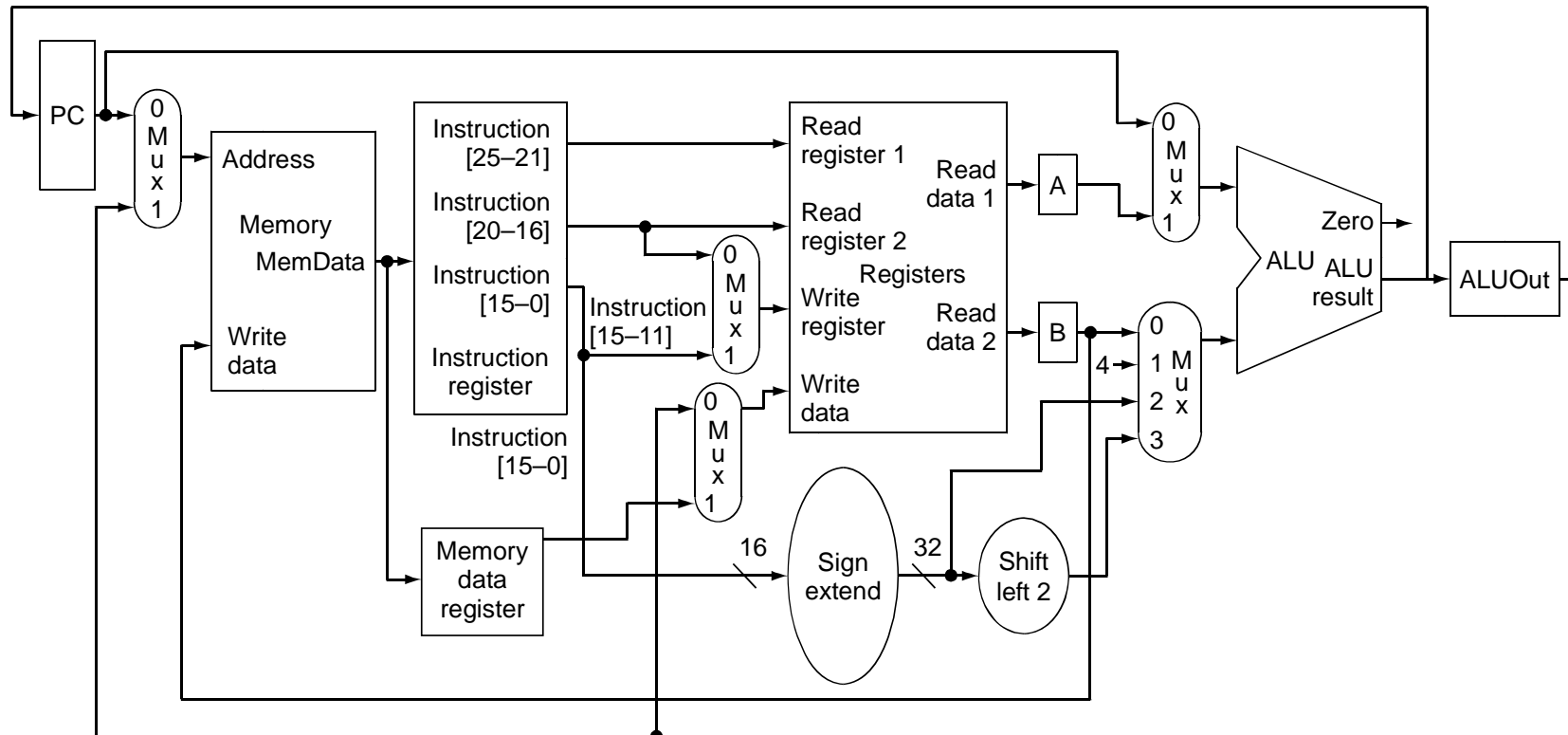- Break up the instructions into steps, each step takes a cycle
 - balance the amount of work to be done
 - restrict each cycle to use only one major functional unit
- At the end of a cycle
 - store values for use in later cycles (easiest thing to do)
 - introduce additional *internal* registers




The Five Steps of a Load Instruction

 

Register File & Memory Write Timing: Ideal vs. Reality


- In previous lectures, register file and memory are simplified:

 - Write happens at the clock tick
- Address (Adr), input data (Din), and write enable (WrEn) must be stable one **set-up** time before the clock tick



- In real life:

 
- Neither register file nor ideal memory has the clock input
- The write path is a combinational logic delay path:
 - ⇒ WrEn goes to 1 and Din (Data In) settles down
 - ⇒ Memory write access delay
 - ⇒ Din is written into mem[address]
- Important: **Address and Data must be stable BEFORE Write Enable goes to 1**



Race Condition Between Address and Write Enable


- This **real** (no clock input) register file may not work reliably in the single cycle processor because:

 - We cannot guarantee Rw will be stable BEFORE $RegWr = 1$
- There is a **race** between Rw (address) and $RegWr$ (write enable)



- The **real** (no clock input) memory may not work reliably in the single cycle processor because:

 - We cannot guarantee Address will be stable BEFORE $WrEn = 1$
- There is a **race** between Adr and $WrEn$




How to Avoid this Race Condition?

- **Solution for the multiple cycle implementation:**
 - **Make sure Address is stable by the end of Cycle N**
 - **Assert Write Enable signal ONE cycle later at Cycle (N + 1)**
 - **We have to make sure that address cannot change until Write Enable is disasserted**

Dual-Port Ideal Memory

- **Dual Port Ideal Memory**
 - Independent Read (**RAdr**, **Dout**) and Write (**WrAdr**, **Din**) ports
 - Read and write (to different location) can occur at the same cycle
- **Read Port is a combinational path:**
 - Read Address (**RAdr**) Valid -->
 - Memory Read Access Delay -->
 - Data Out (**Dout**) Valid
- **Write Port is also a combinational path:**
 - MemWrite **MemWr** = 1 -->
 - Memory Write Access Delay -->
 - Data In (**Din**) is written into location [**WrAdr**]

 

Instructions from ISA perspective

- Consider each instruction from perspective of ISA.
- Example:
 - The add instruction changes a register.
 - Register specified by bits 15:11 of instruction.
 - Instruction specified by the PC.
 - New value is the sum (“**op**”) of two registers.
 - Registers specified by bits 25:21 and 20:16 of the instruction

`Reg[Memory[PC][15:11]] <= Reg[Memory[PC][25:21]] op Reg[Memory[PC][20:16]]`

- In order to accomplish this we must break up the instruction.
(kind of like introducing variables when programming)

Breaking down an instruction

- **ISA definition of arithmetic:**

$\text{Reg}[\text{Memory}[\text{PC}][15:11]] \leq \text{Reg}[\text{Memory}[\text{PC}][25:21]] \text{ op } \text{Reg}[\text{Memory}[\text{PC}][20:16]]$

- **Could break down to:**

- $\text{IR} \leq \text{Memory}[\text{PC}]$
- $\text{A} \leq \text{Reg}[\text{IR}[25:21]]$
- $\text{B} \leq \text{Reg}[\text{IR}[20:16]]$
- $\text{ALUOut} \leq \text{A op B}$
- $\text{Reg}[\text{IR}[20:16]] \leq \text{ALUOut}$

- **We forgot an important part of the definition of arithmetic!**

- $\text{PC} \leq \text{PC} + 4$

Idea behind multicycle approach

- We define each instruction from the ISA perspective (do this!)
- Break it down into steps following our rule that data flows through at most one major functional unit (e.g., balance work across steps)
- Introduce new registers as needed (e.g, **A**, **B**, **ALUOut**, **MDR**, etc.)
- Finally try and pack as much work into each step
(avoid unnecessary cycles)
while also trying to share steps where possible
(minimizes control, helps to simplify solution)
- Result: Our book's multicycle Implementation!

Five Execution Steps

- **Instruction Fetch**
- **Instruction Decode and Register Fetch**
- **Execution, Memory Address Computation, or Branch Completion**
- **Memory Access or R-type instruction completion**
- **Write-back step**

INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!

Step 1: Instruction Fetch

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR <= Memory[PC];  
PC <= PC + 4;
```



Can we figure out the values of the control signals?

What is the advantage of updating the PC now?

1. Instruction Fetch Cycle: In the Beginning

- Every cycle begins right **AFTER** the clock tick:


- **mem[PC]** **PC<31:0> + 4**

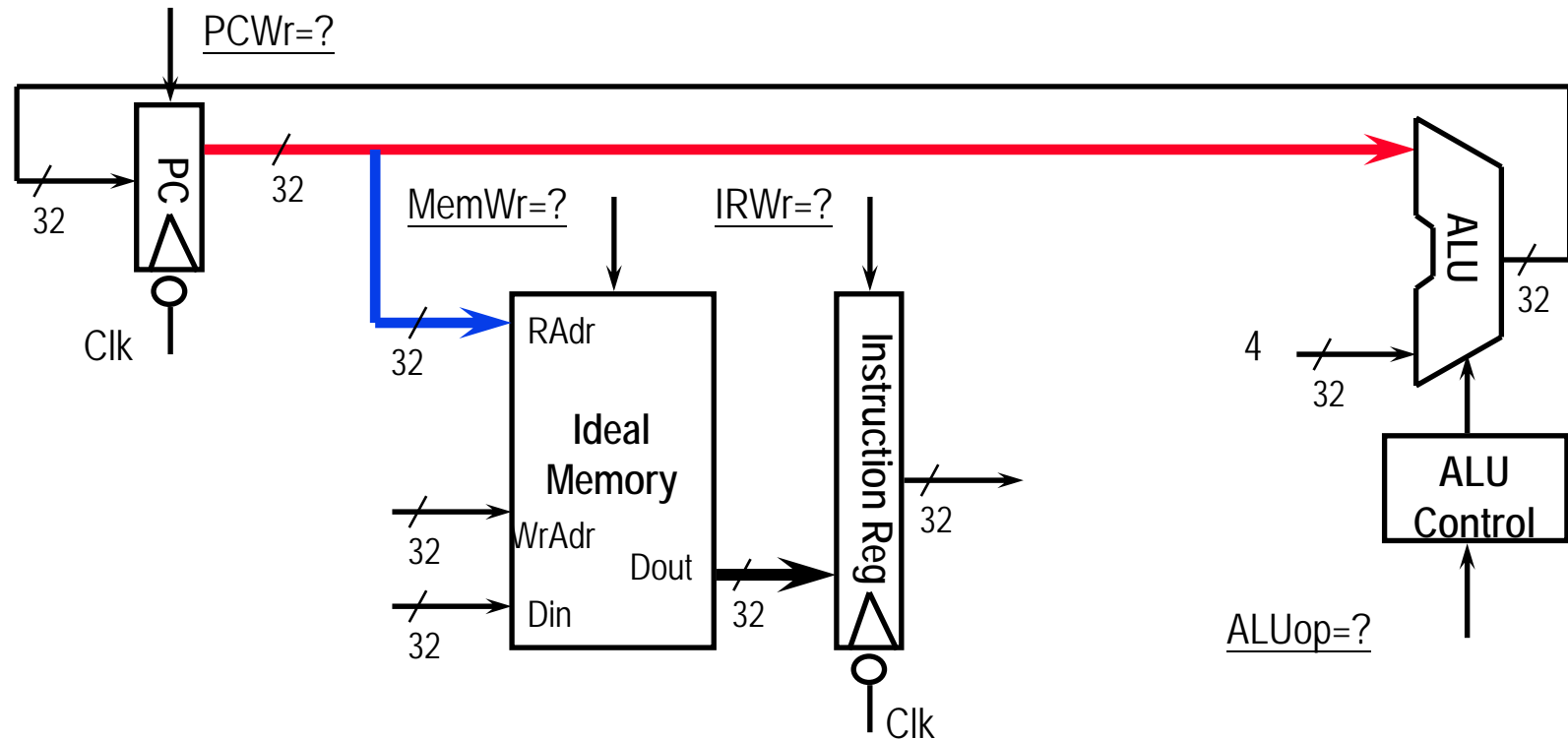 

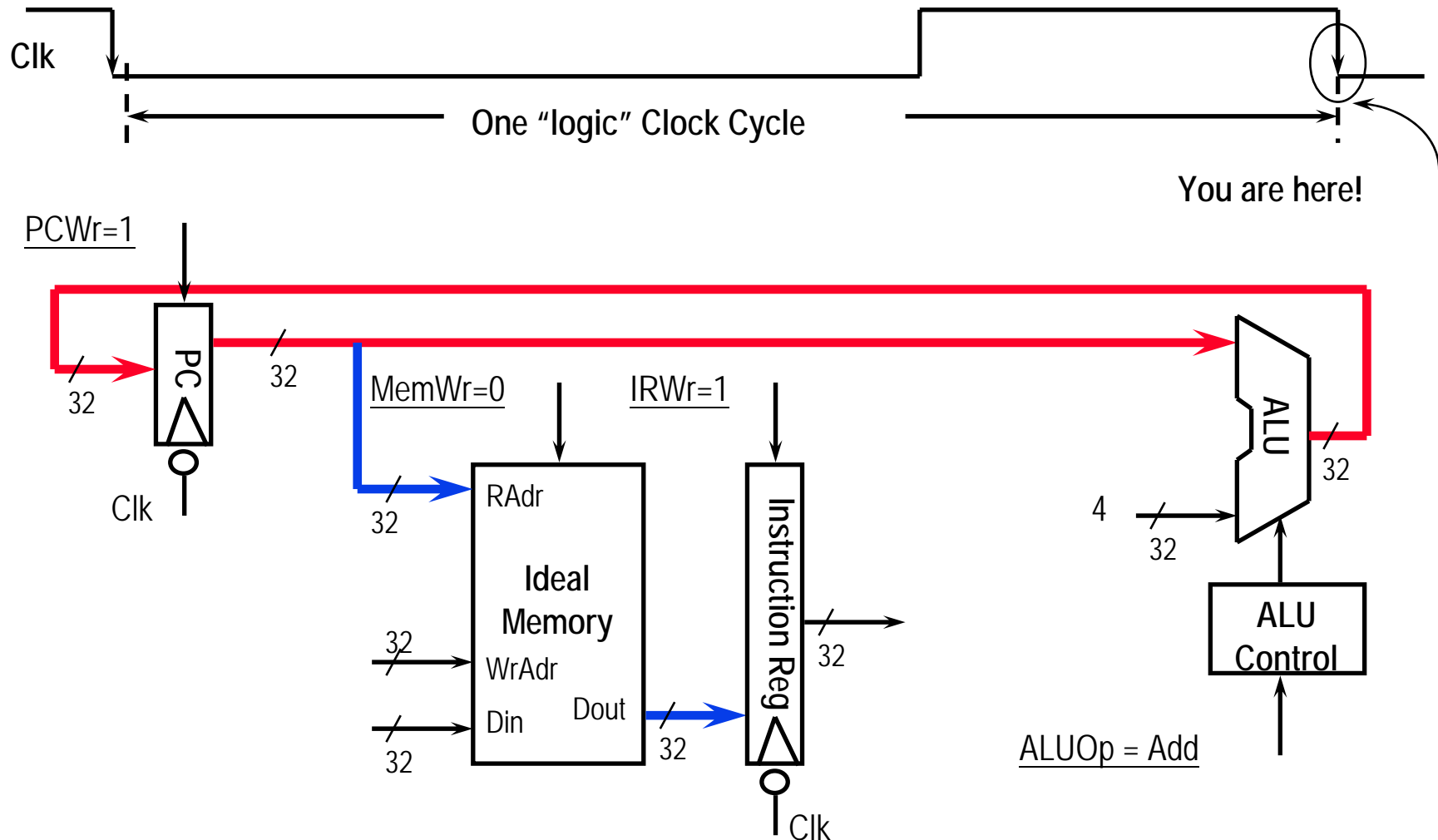
1. Instruction Fetch Cycle: The End

- Every cycle ends AT the next clock tick (storage element updates):

- $IR \leftarrow \text{mem}[PC]$ $PC_{<31:0>} \leftarrow PC_{<31:0>} + 4$



Instruction Fetch Cycle: Overall Picture

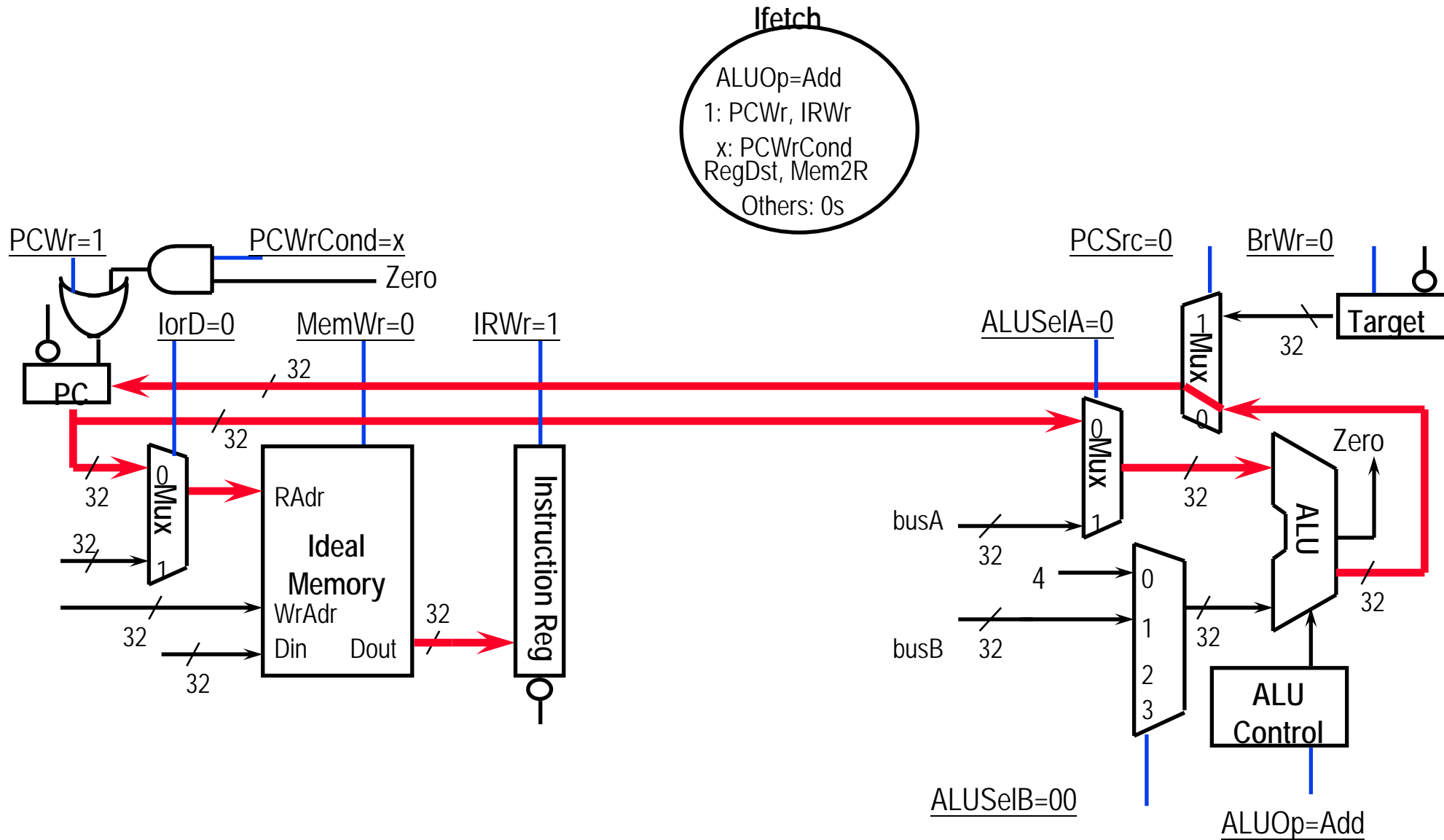

Step 2: Instruction Decode and Register Fetch

- Read registers **rs** and **rt** in case we need them
- Compute the branch address in case the instruction is a branch
- RTL:

A <= Reg[IR[25:21]];

B <= Reg[IR[20:16]];


ALUOut <= PC + (sign-extend(IR[15:0]) << 2);

- We aren't setting any control lines based on the instruction type
(we are busy "decoding" it in our control logic)

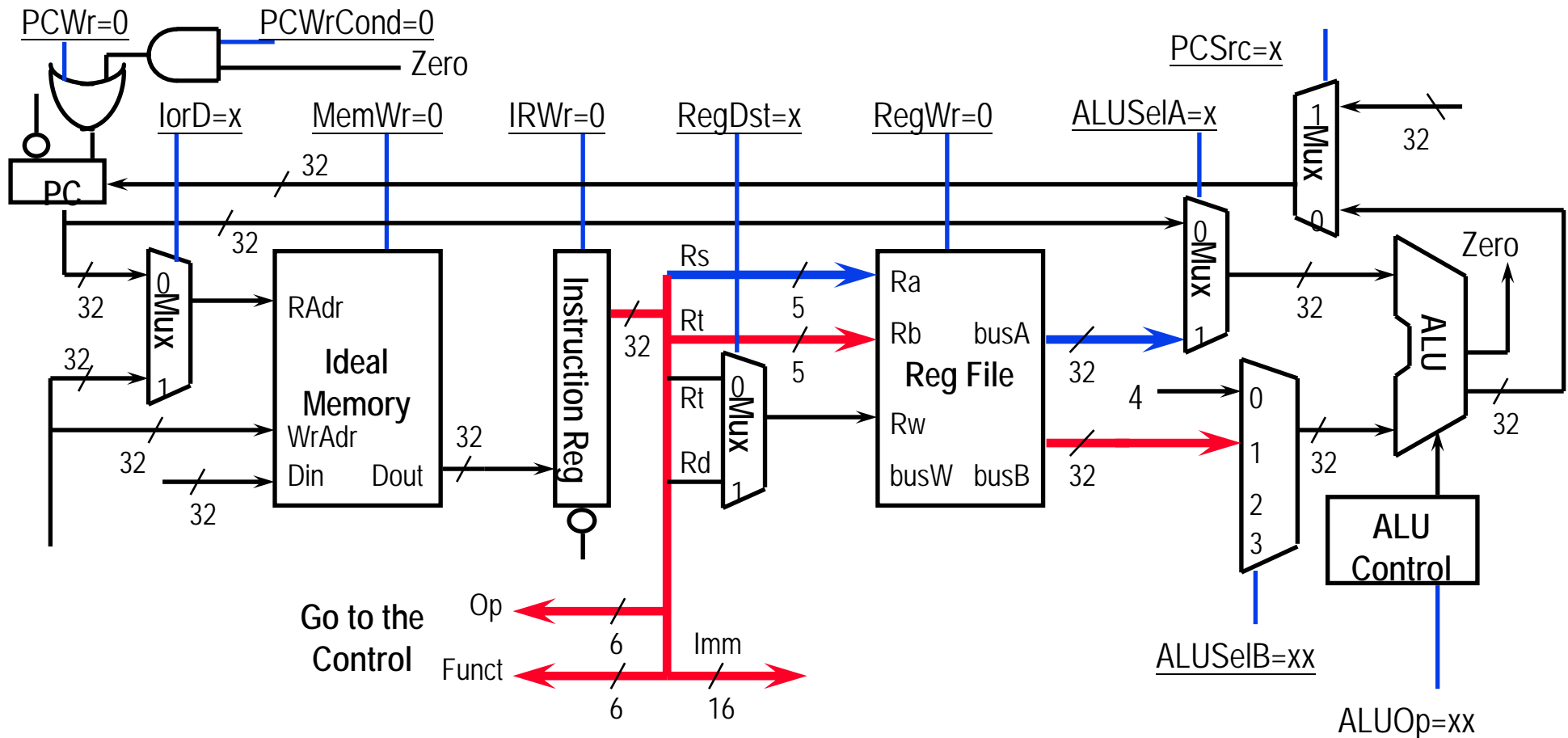2. Register Fetch / Instruction Decode

• $\text{busA} \leftarrow \text{RegFile}[\text{rs}]$; $\text{busB} \leftarrow \text{RegFile}[\text{rt}]$;

ALU is not being used: $\text{ALUctr} \leftarrow \text{xx}$




2. Register Fetch / Instruction Decode (Continued)

• $\text{busA} \leftarrow \text{Reg}[\text{rs}] ; \text{busB} \leftarrow \text{Reg}[\text{rt}] ;$

$\text{Target} \leftarrow \text{PC} + \text{SignExt}(\text{Imm16}) * 4$

Rfetch/Decode

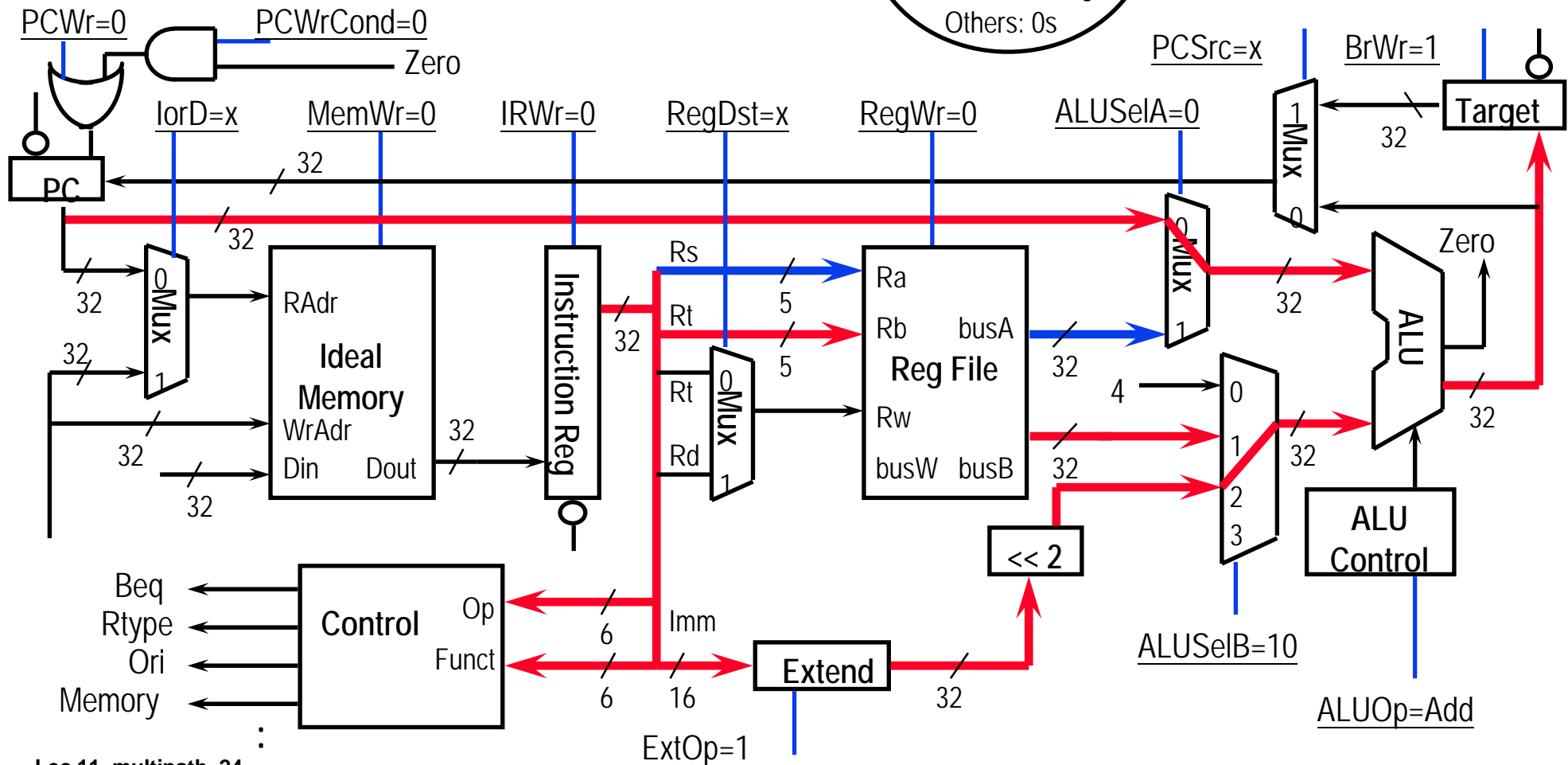ALUOp=Add
1: BrWr, ExtOp
ALUSelB=10
x: RegDst, PCSrc
lorD, MemtoReg
Others: 0s



Step 3: (instruction dependent)

ALU is performing one of three functions, based on instruction type

- **Memory Reference:**

$ALUOut \leq A + \text{sign-extend}(IR[15:0]);$

- **R-type:**

$ALUOut \leq A \text{ op } B;$

- **Branch:**

$\text{if } (A == B) \text{ PC} \leq ALUOut;$

- **Jump (see Lec. 10-18)**


$\text{PC} \leq \text{PC}[31:28] \parallel (IR[25:0] \ll 2);$

3. Branch Completion

- if (busA == busB)
 PC <- Target


BrComplete

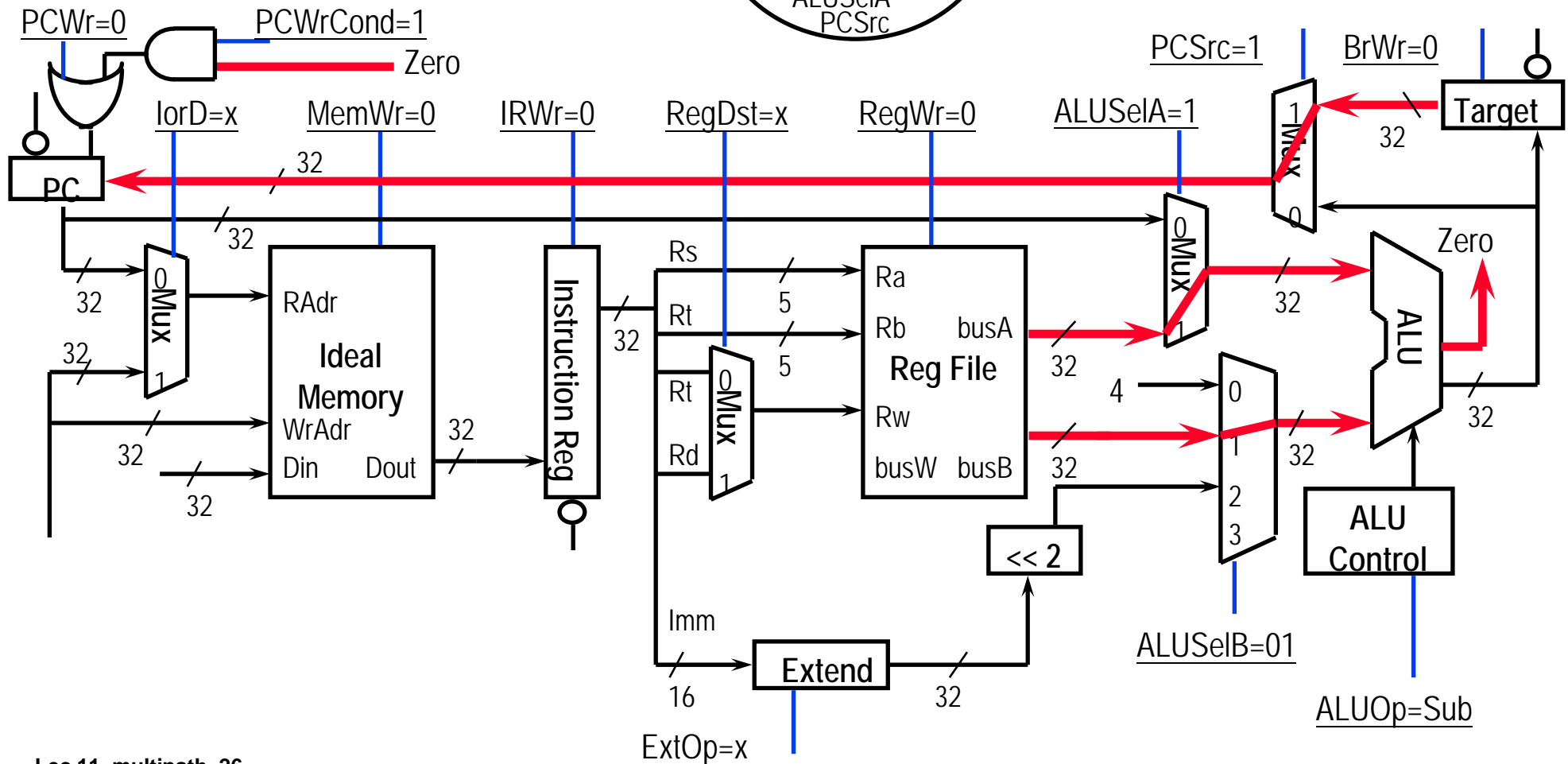ALUOp=Sub
ALUSelB=01
x: lorD, Mem2Reg
RegDst, ExtOp
1: PCWrCond
ALUSelA
PCSrc




Instruction Decode: We have a R-type!

- Next Cycle: **R-type** Execution

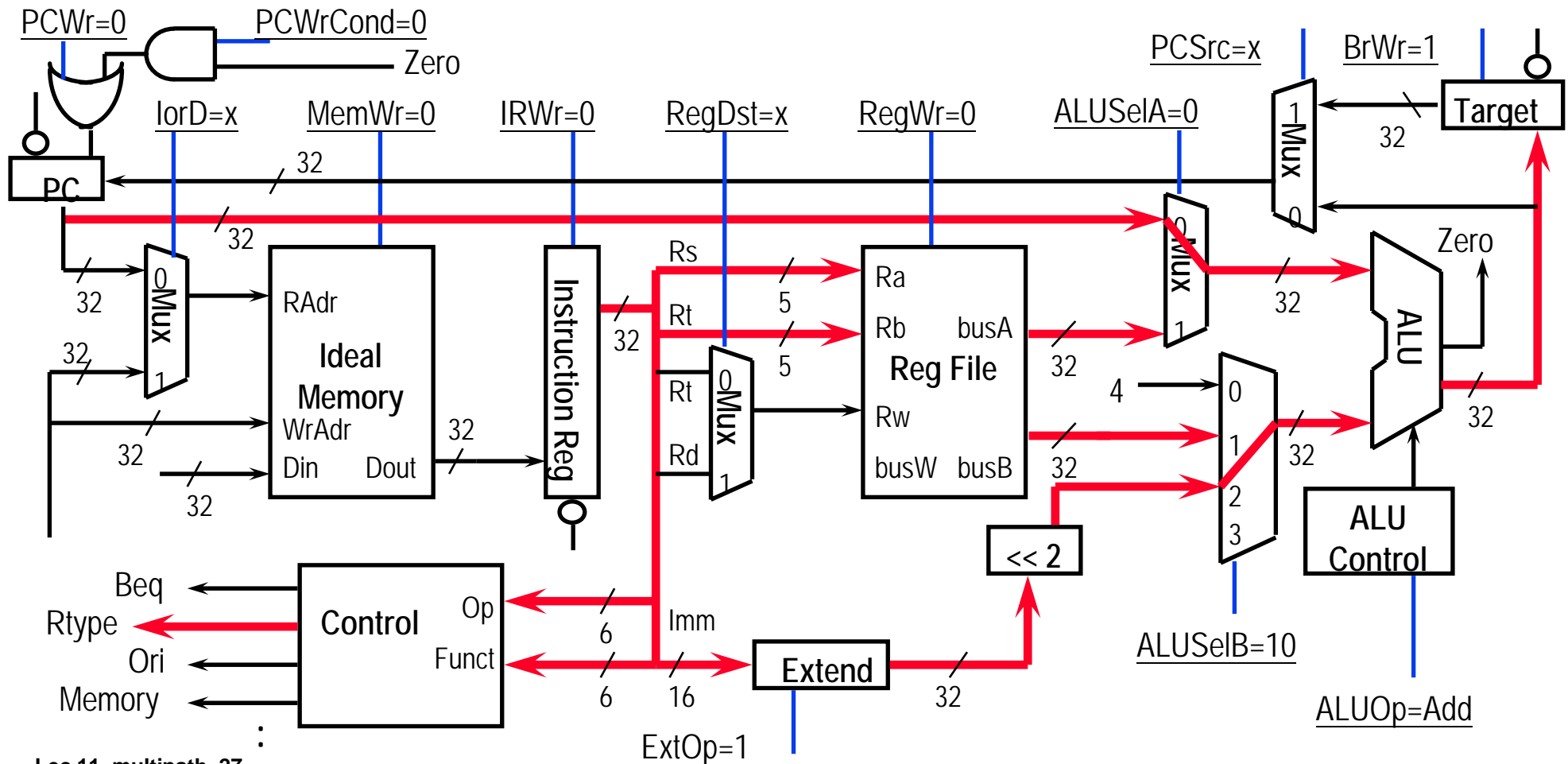

3. R-type Execution

- **ALU Output <- busA op busB**

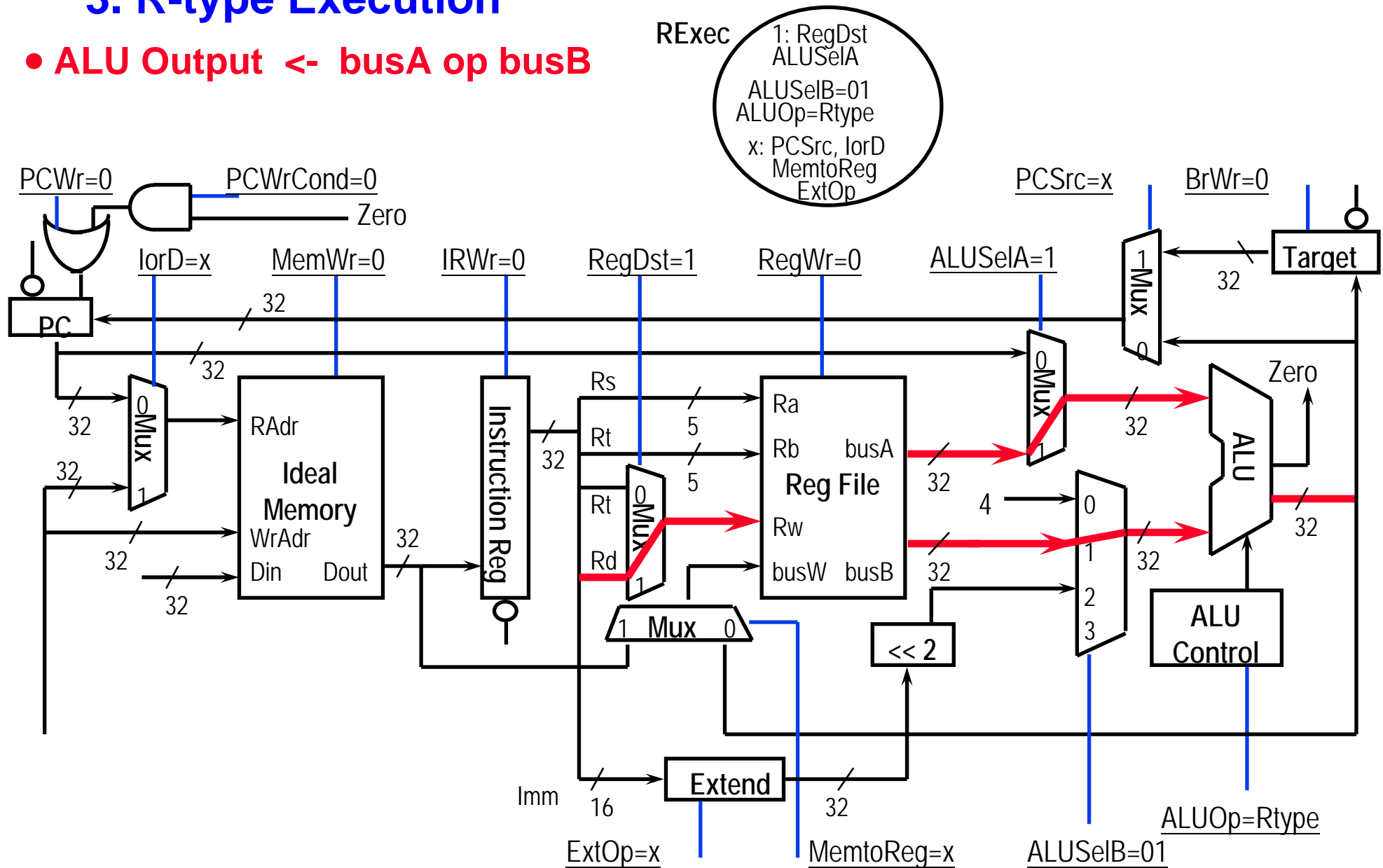

Step 4: R-type or memory-access

- Loads and stores access memory

MDR \leq Memory[ALUOut];
or
Memory[ALUOut] \leq B;


- R-type instructions finish

Reg[IR[15:11]] \leq ALUOut;

The write actually takes place at the end of the cycle on the edge


4. R-type Completion

- $R[rd] \leftarrow \text{ALU Output}$

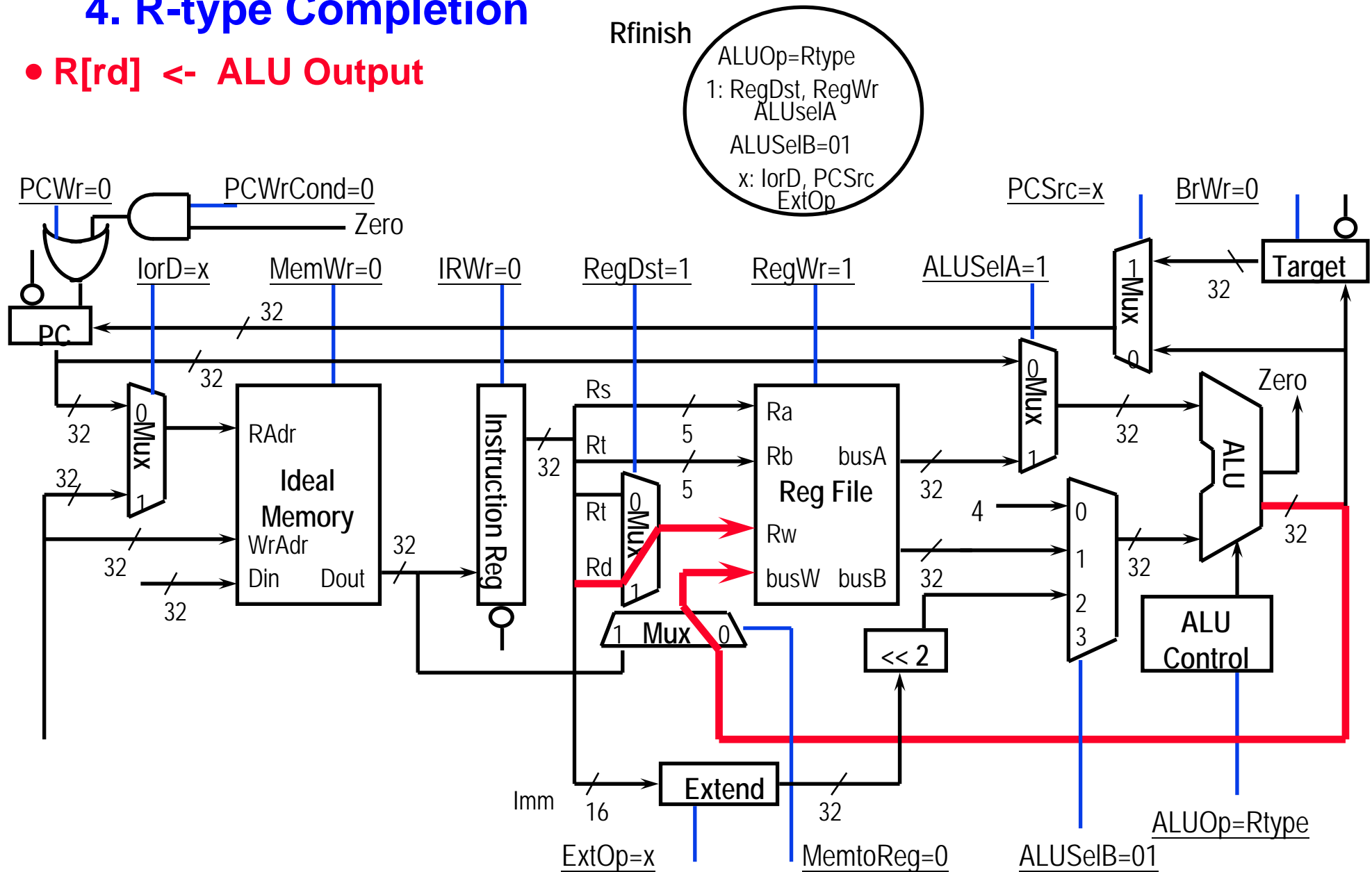

A Multiple Cycle Delay Path

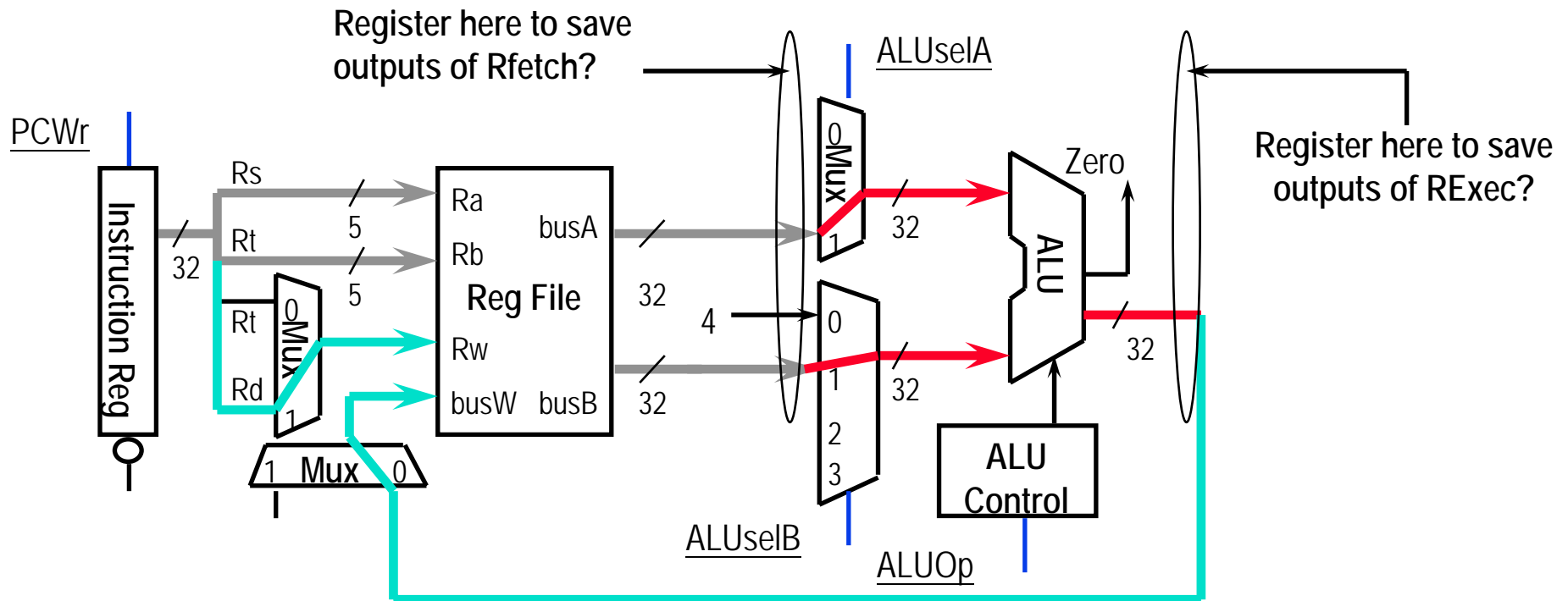- There is no register to save the results between:
 - Register Fetch: $\text{busA} \leftarrow \text{Reg}[\text{rs}] ; \text{busB} \leftarrow \text{Reg}[\text{rt}]$
 - R-type Execution: $\text{ALU output} \leftarrow \text{busA op busB}$
 - R-type Completion: $\text{Reg}[\text{rd}] \leftarrow \text{ALU output}$




A Multiple Cycle Delay Path (Continued)

- Register is NOT needed to save the outputs of Register Fetch:
 - IRWr = 0: busA and busB will not change after Register Fetch
- Register is NOT needed to save the outputs of R-type Execution:
 - busA and busB will not change after Register Fetch
 - Control signals ALUSelA, ALUSelB, and ALUOp will not change after R-type Execution
 - Consequently ALU output will not change after R-type Execution
- In theory, you need a register to hold a signal value if:
 - Cond.(1) The signal is computed in one clock cycle and used in another.
 - Cond.(2) AND the inputs to the functional block that computes this signal can change before the signal is written into a state element.
- You can save a register if Cond.(1) is true BUT Cond.(2) is false:
 - But in practice, this will introduce a multiple cycle delay path:
 - ⇒ A logic delay path that takes multiple cycles to propagate from one storage element to the next storage element

Pros and Cons of a Multiple Cycle Delay Path

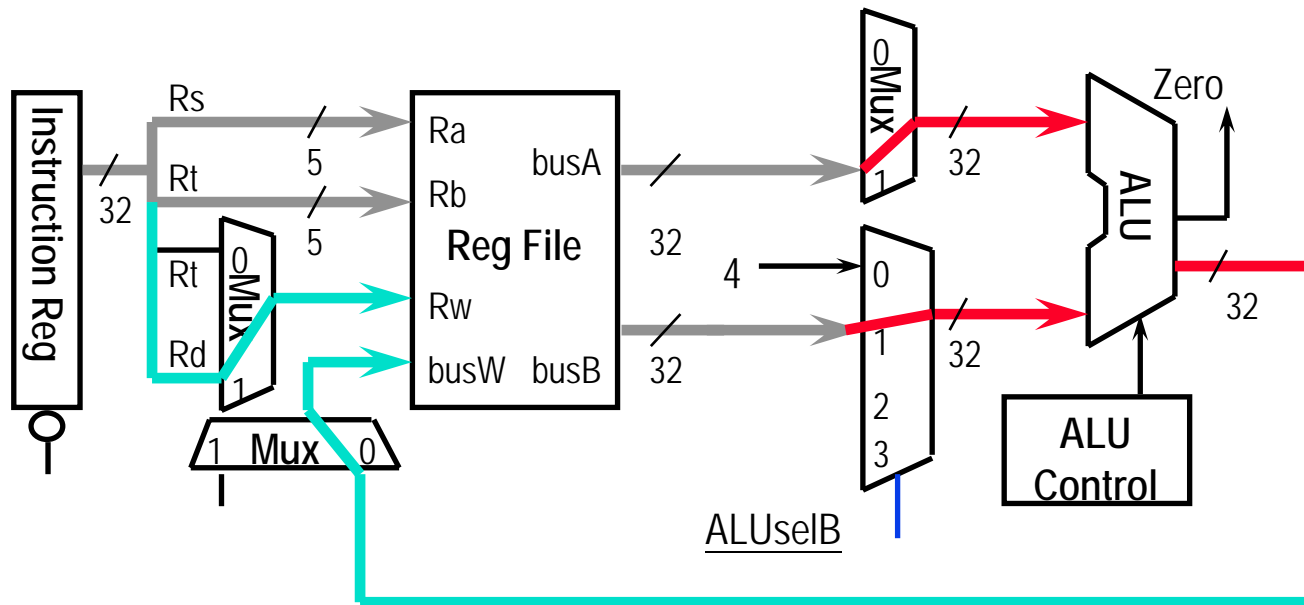
- A 3-cycle path example:
 - IR (storage) -> Reg File Read -> ALU -> Reg File Write (storage)
- Advantages:
 - Register savings
 - We can share time among cycles:
 - ⇒ If ALU takes longer than one cycle, still “a OK” as long as the entire path takes less than 3 cycles to finish



Pros and Cons of a Multiple Cycle Delay Path (Continued)


- **Disadvantage:**

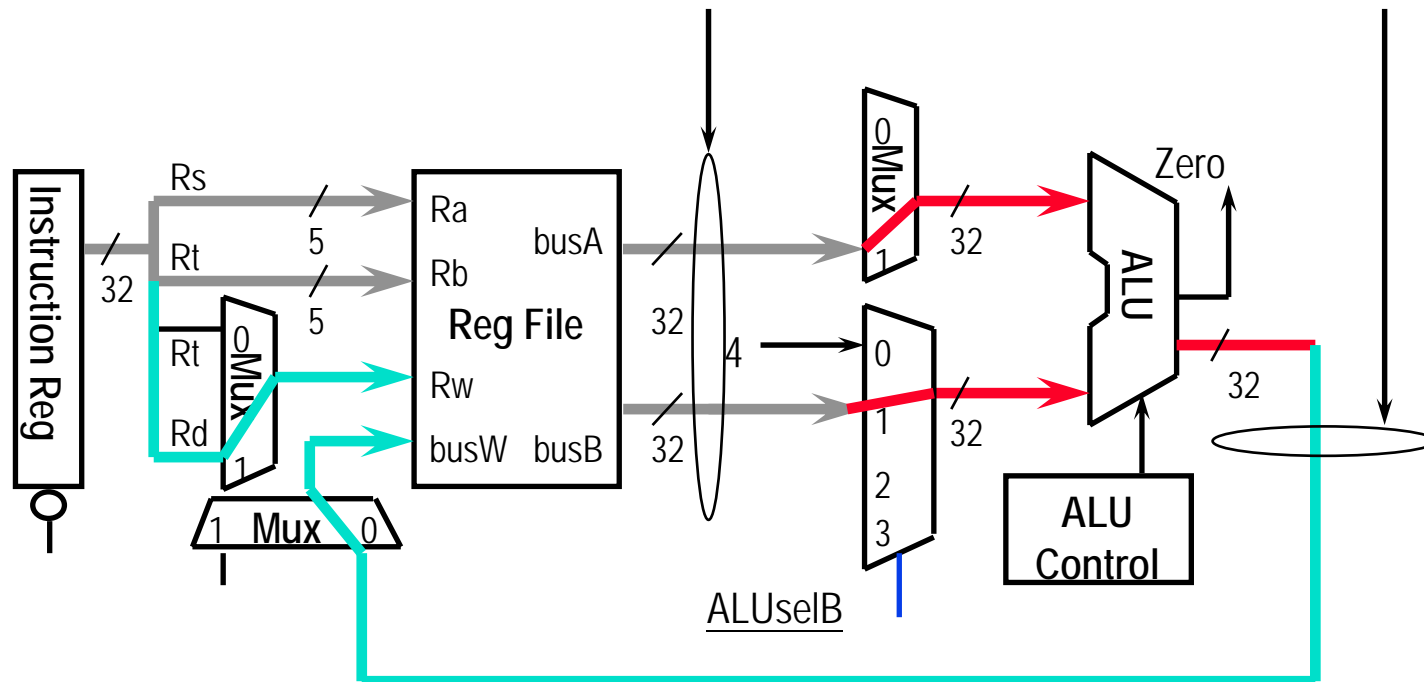- Static timing analyzer, which **ONLY** looks at delay between two storage elements, will report this as a timing violation
- You have to ignore the static timing analyzer's warnings
- But you may end up ignoring real timing violations
- I always TRY to put in registers between cycles to avoid **MCDP**



Instruction Decode: We have an Ori!

- Next Cycle: **Ori** Execution

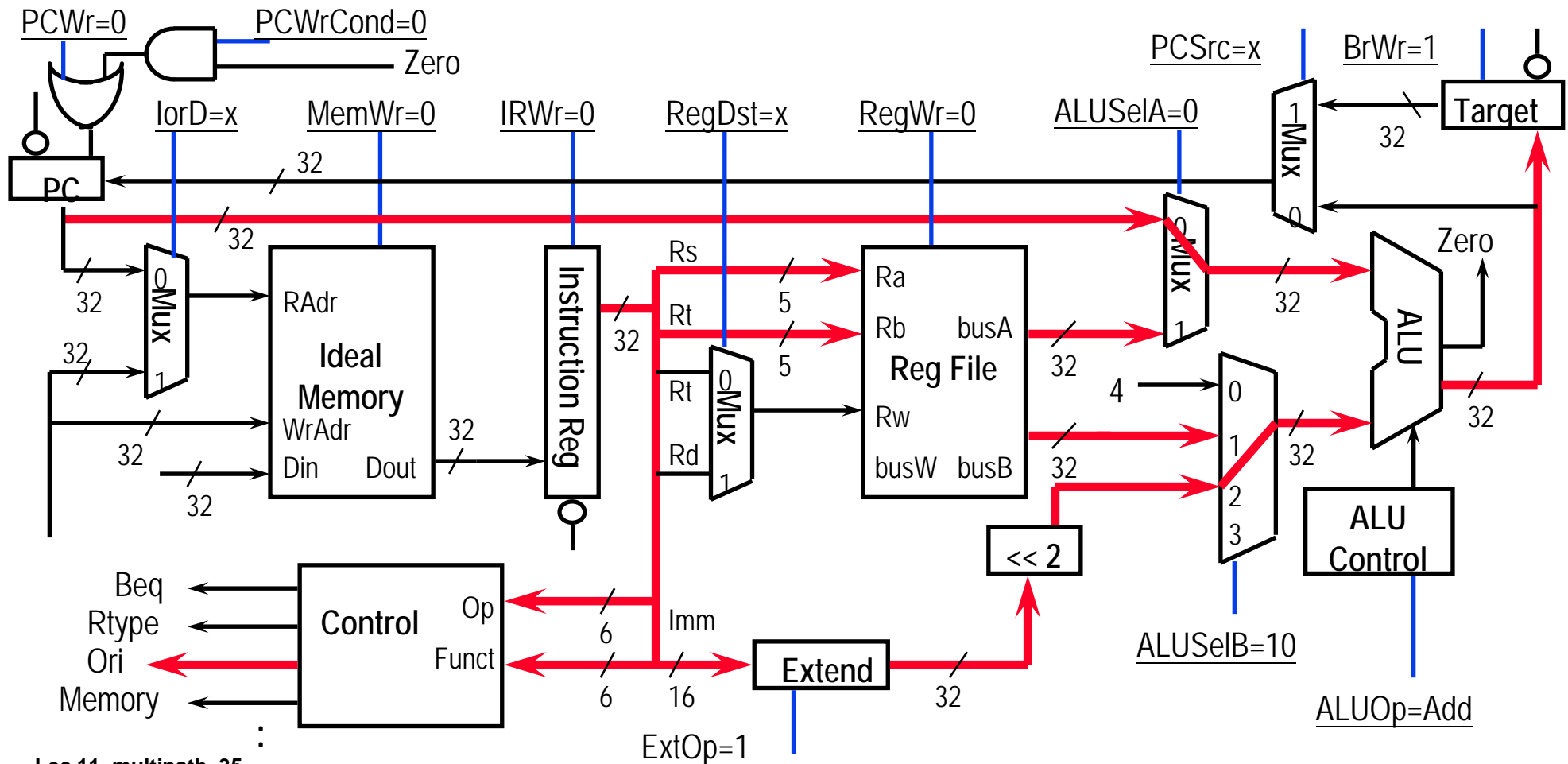


Ori Execution (Step 3)

- ALU output <- busA or ZeroExt(imm16)


OriExec

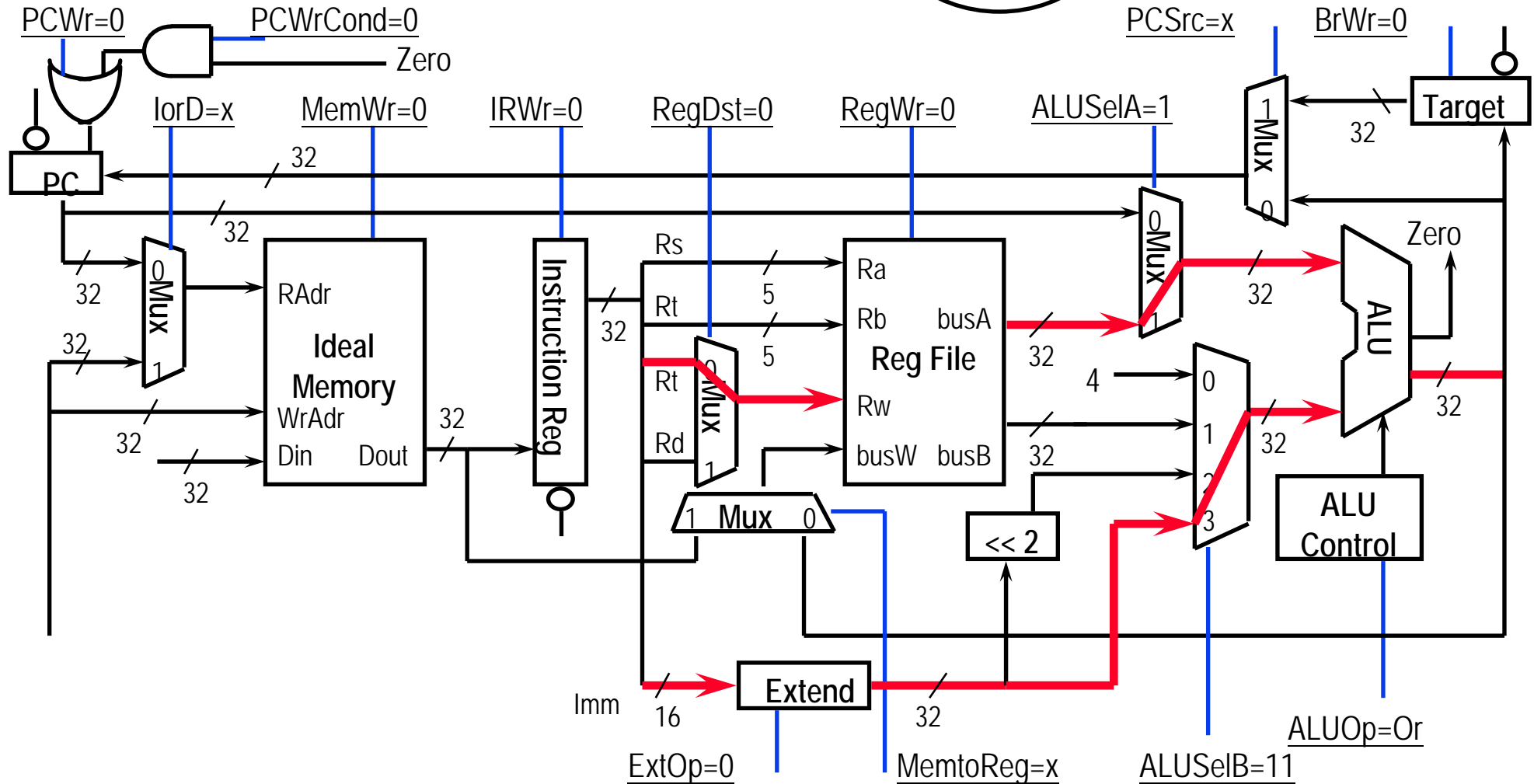ALUOp=Or
1: ALUSelA
ALUSelB=11
x: MemtoReg
forD, PCSrc




Ori Completion (Step 4)

- **Reg[rt] <- ALU output**

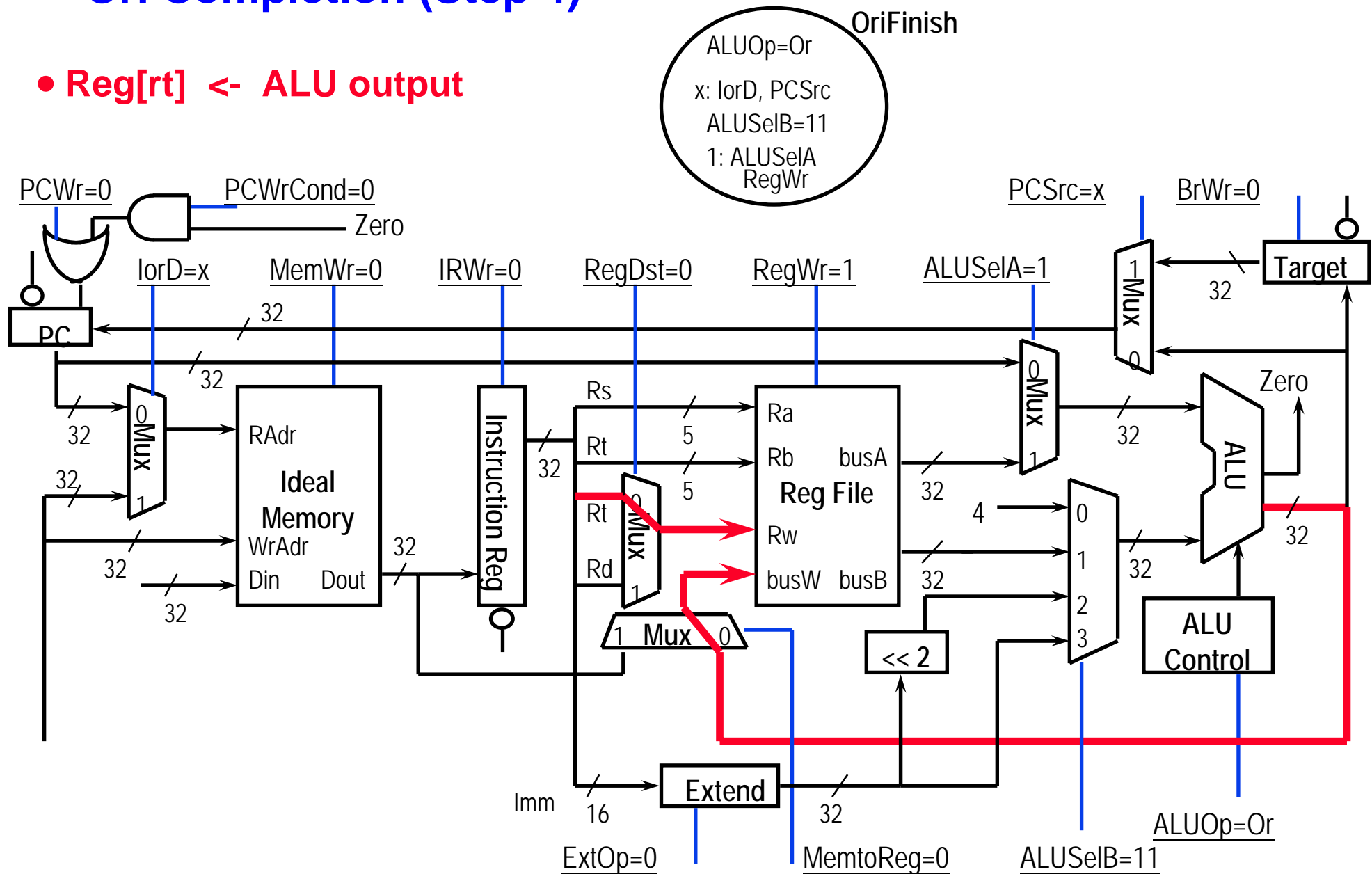


Instruction Decode: We have a Memory Access!

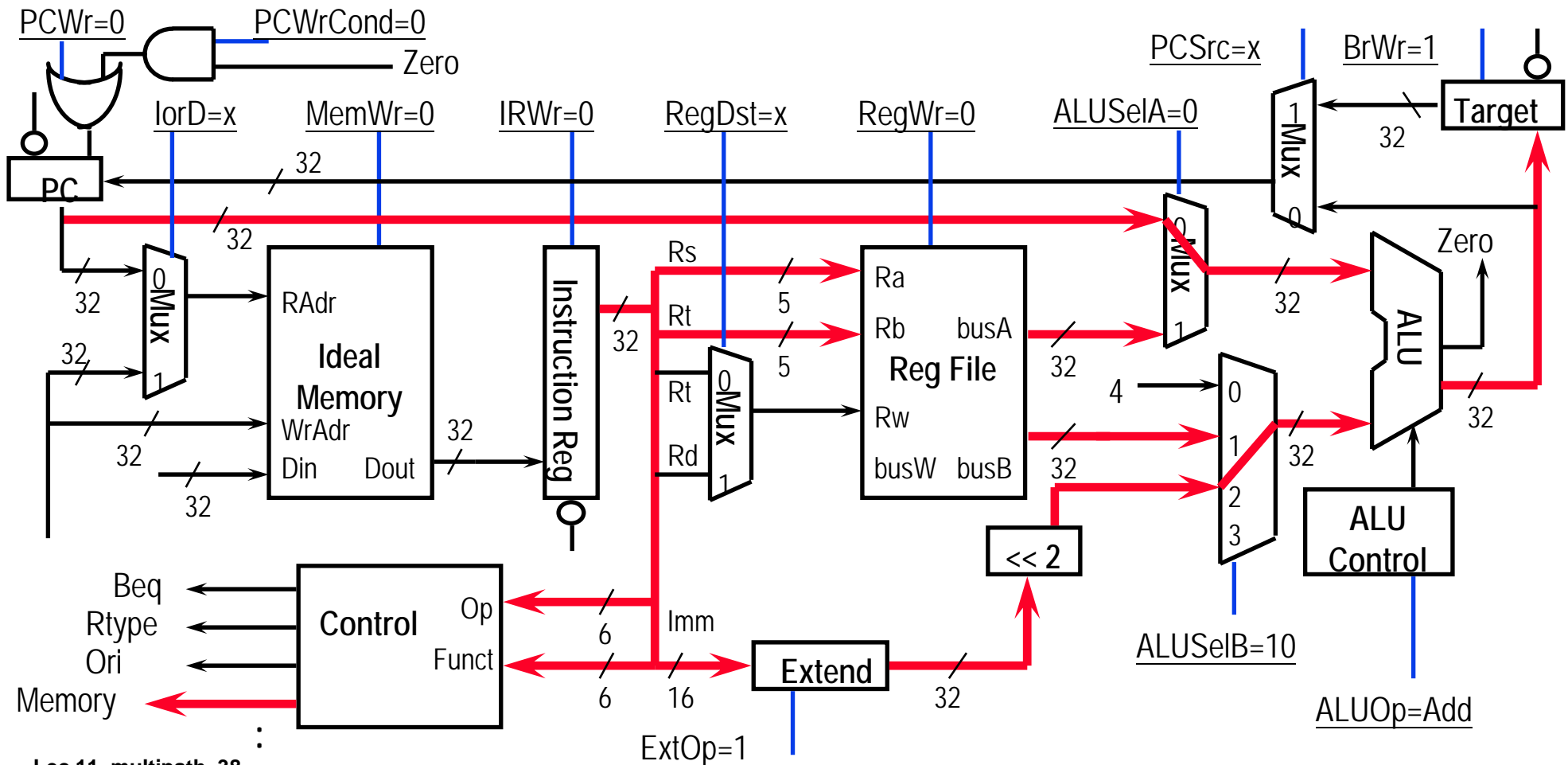- Next Cycle: **Memory Address Calculation**




Memory Address Calculation (Step 3)

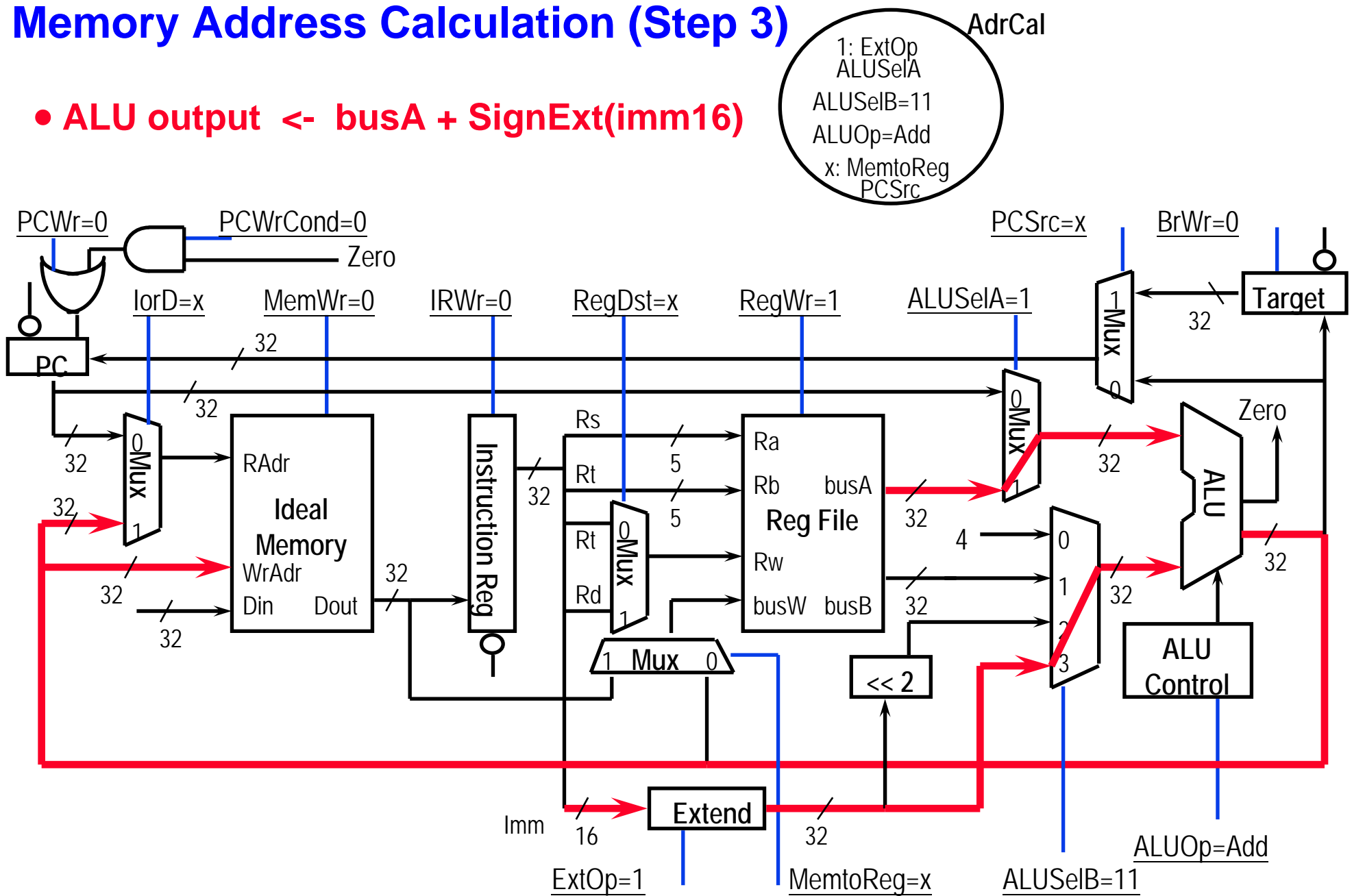- **ALU output** <- busA + SignExt(imm16)



Memory Access for Store (Step 4)


- **mem[ALU output] <- busB**

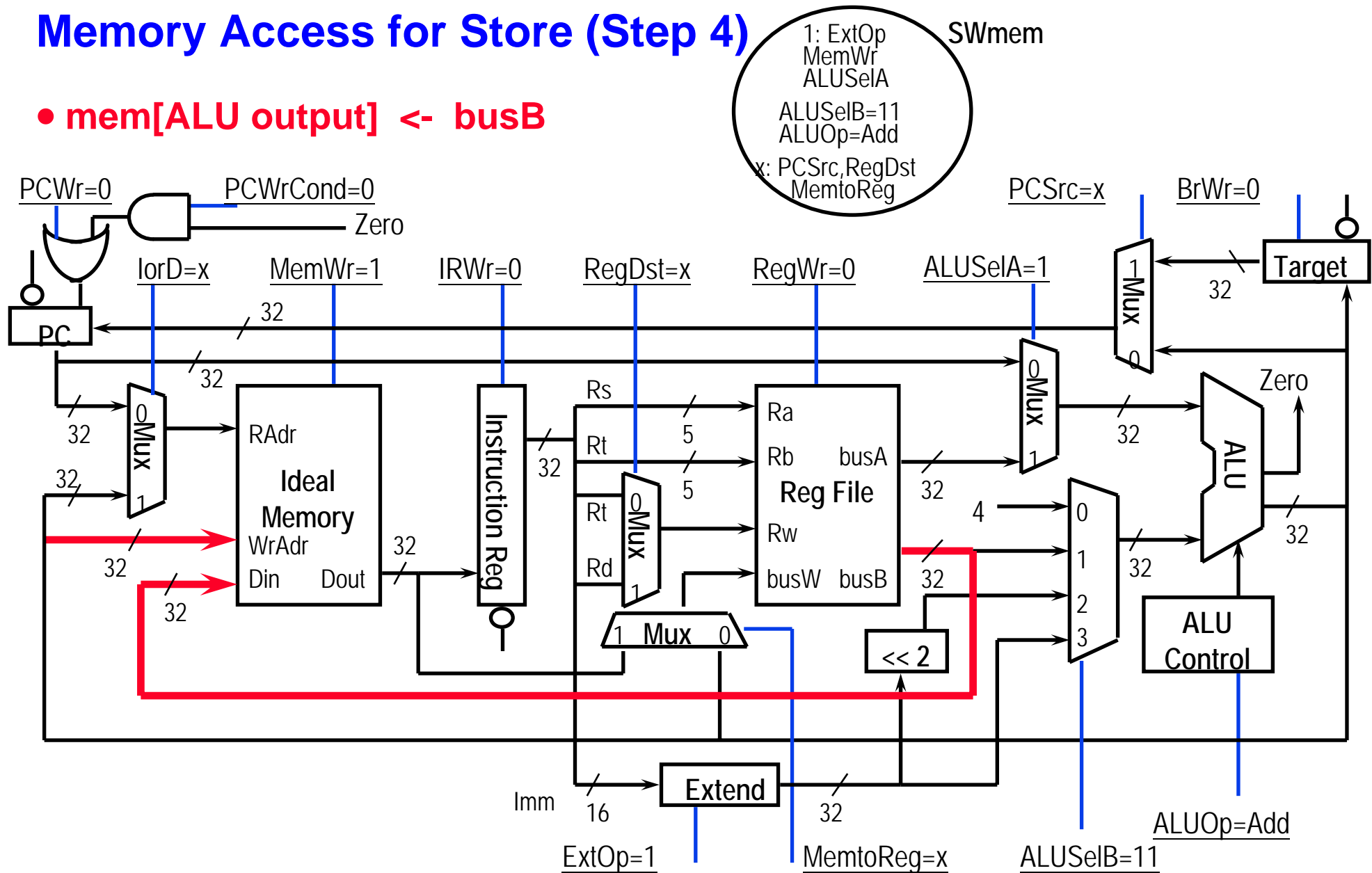

Memory Access for Load (Step 4)

• **Mem Dout** <- mem[ALU output]

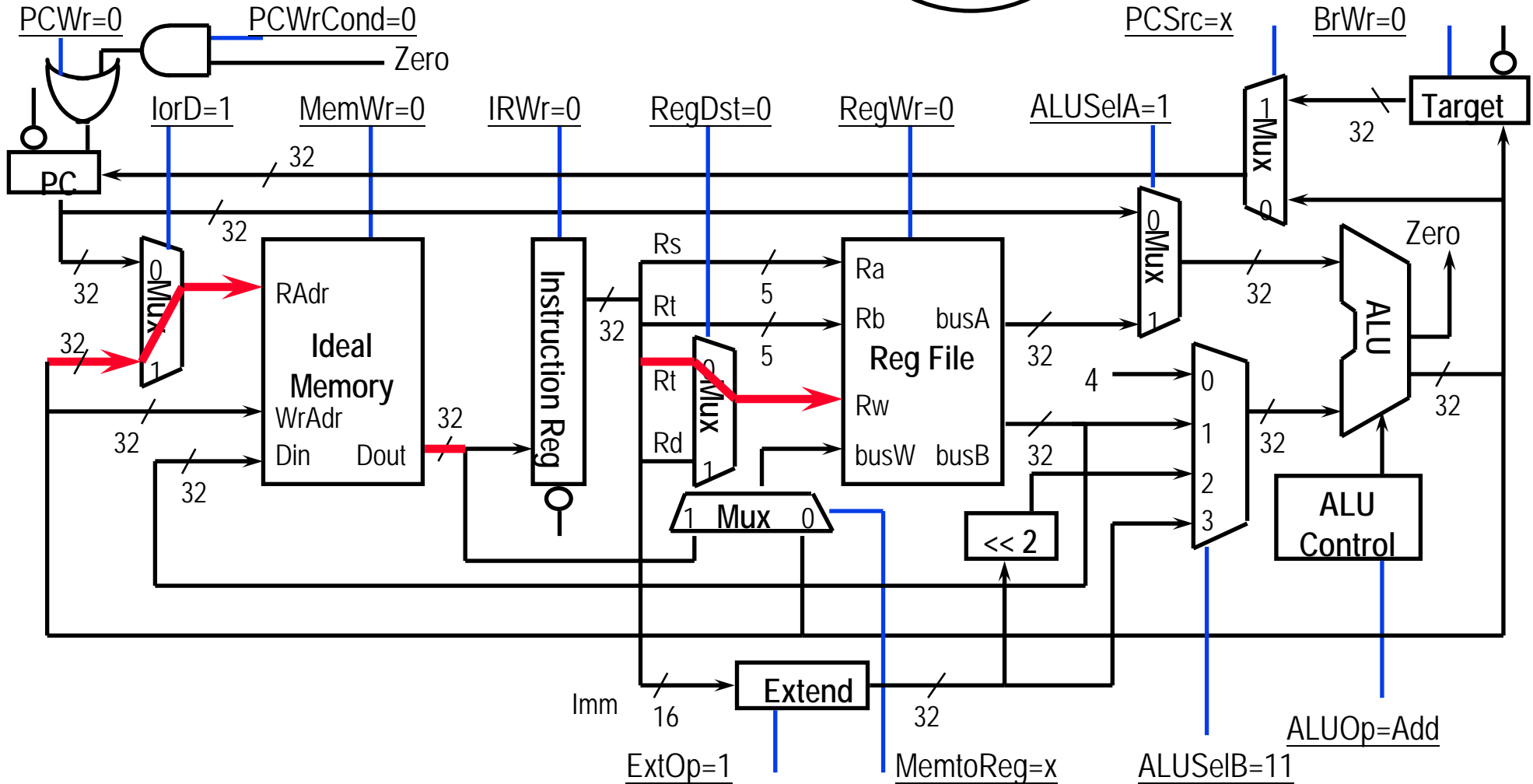1: ExtOp
ALUSelA, lorD
ALUSelB=11
ALUOp=Add
x: MemtoReg
PCSrc




Step 5: Write-back for Load

- $\text{Reg}[\text{IR}[20:16]] \leftarrow \text{MDR};$


Which instruction needs this?

Write Back for Load (Step 5)

- **Reg[rt] <- Mem Dout**

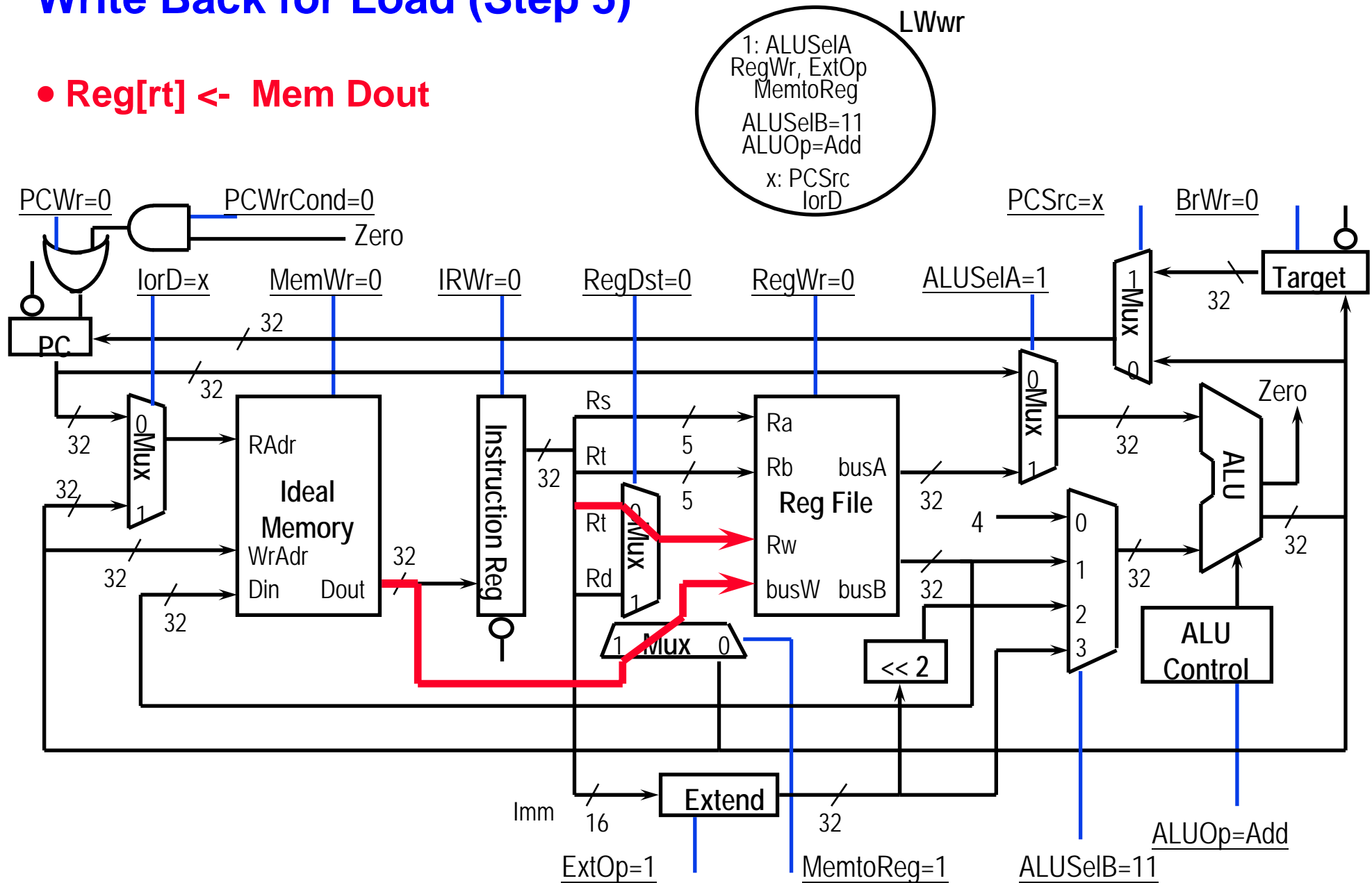

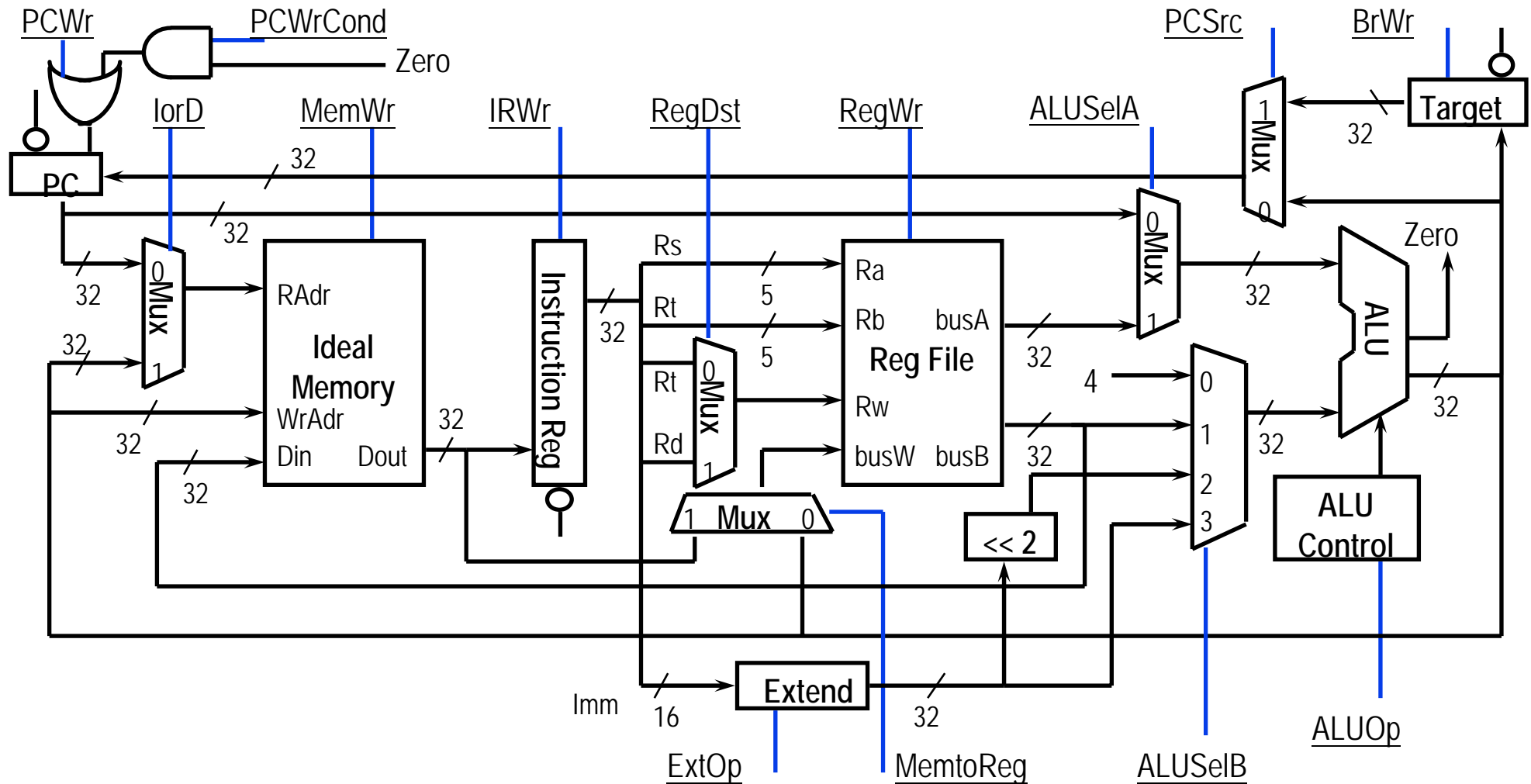Putting it all together: Multiple Cycle Datapath




Summary:

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	IR \leftarrow Memory[PC]			
	PC \leftarrow PC + 4			
Instruction decode/ register fetch	A \leftarrow Reg [IR[25:21]]			
	B \leftarrow Reg [IR[20:16]]			
	ALUOut \leftarrow PC + (sign-extend (IR[15:0]) \ll 2)			
Execution, address computation, branch/ jump completion	ALUOut \leftarrow A op B	ALUOut \leftarrow A + sign-extend (IR[15:0])	if (A == B) then PC \leftarrow ALUOut	PC \leftarrow {PC [31:28], (IR[25:0] \ll 2'b00)}
Memory access or R-type completion	Reg [IR[15:11]] \leftarrow ALUOut	Load: MDR \leftarrow Memory[ALUOut] or Store: Memory [ALUOut] \leftarrow B		
Memory read completion		Load: Reg[IR[20:16]] \leftarrow MDR		


Implementing the Control

- **Value of control signals is dependent upon:**
 - what instruction is being executed
 - which step is being performed
- **Use the information we've accumulated to specify a finite state machine (FSM)**
 - specify the finite state machine graphically, or
 - use microprogramming
- **Implementation can be derived from specification**


Graphical Specification of FSM

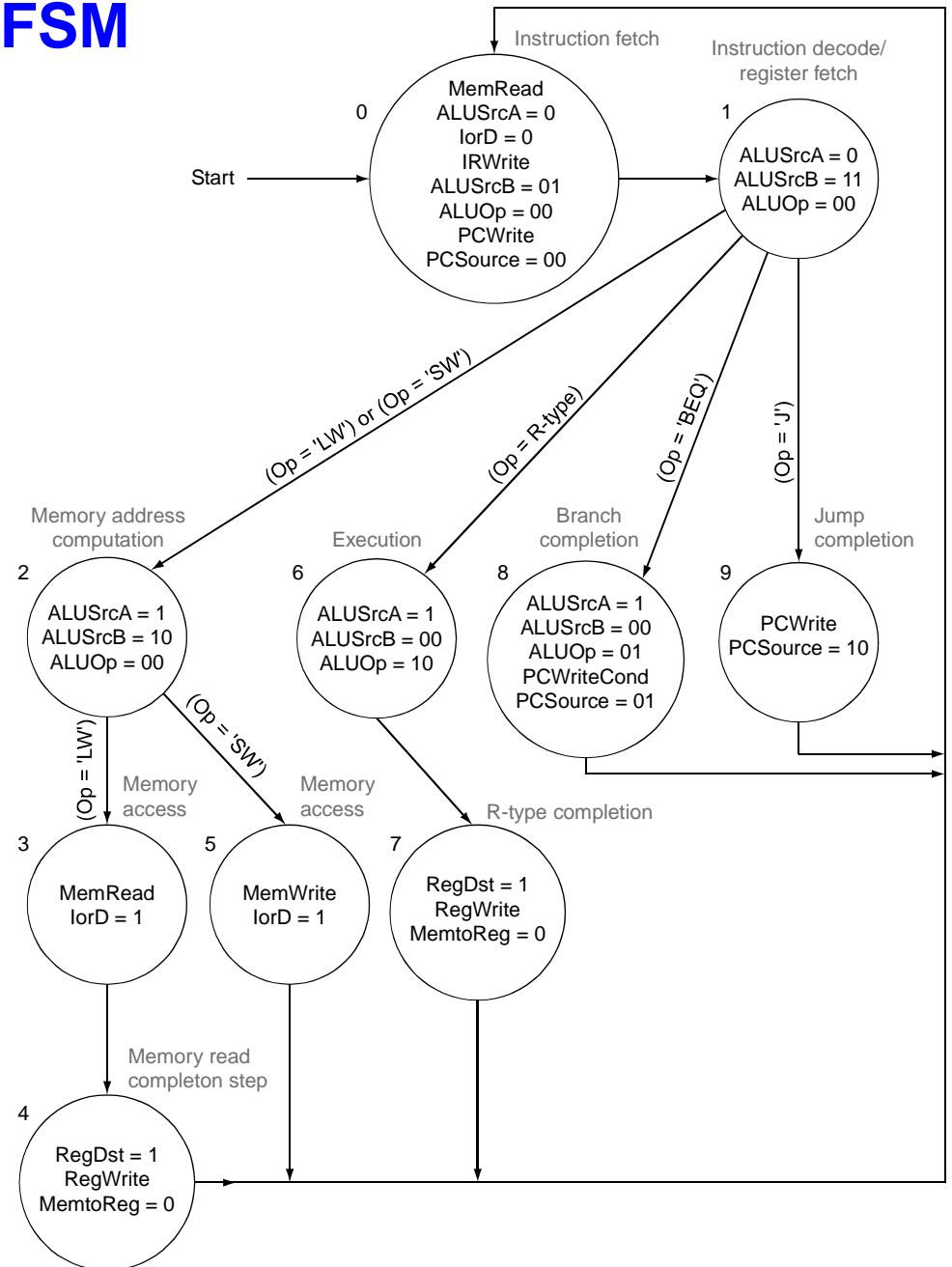

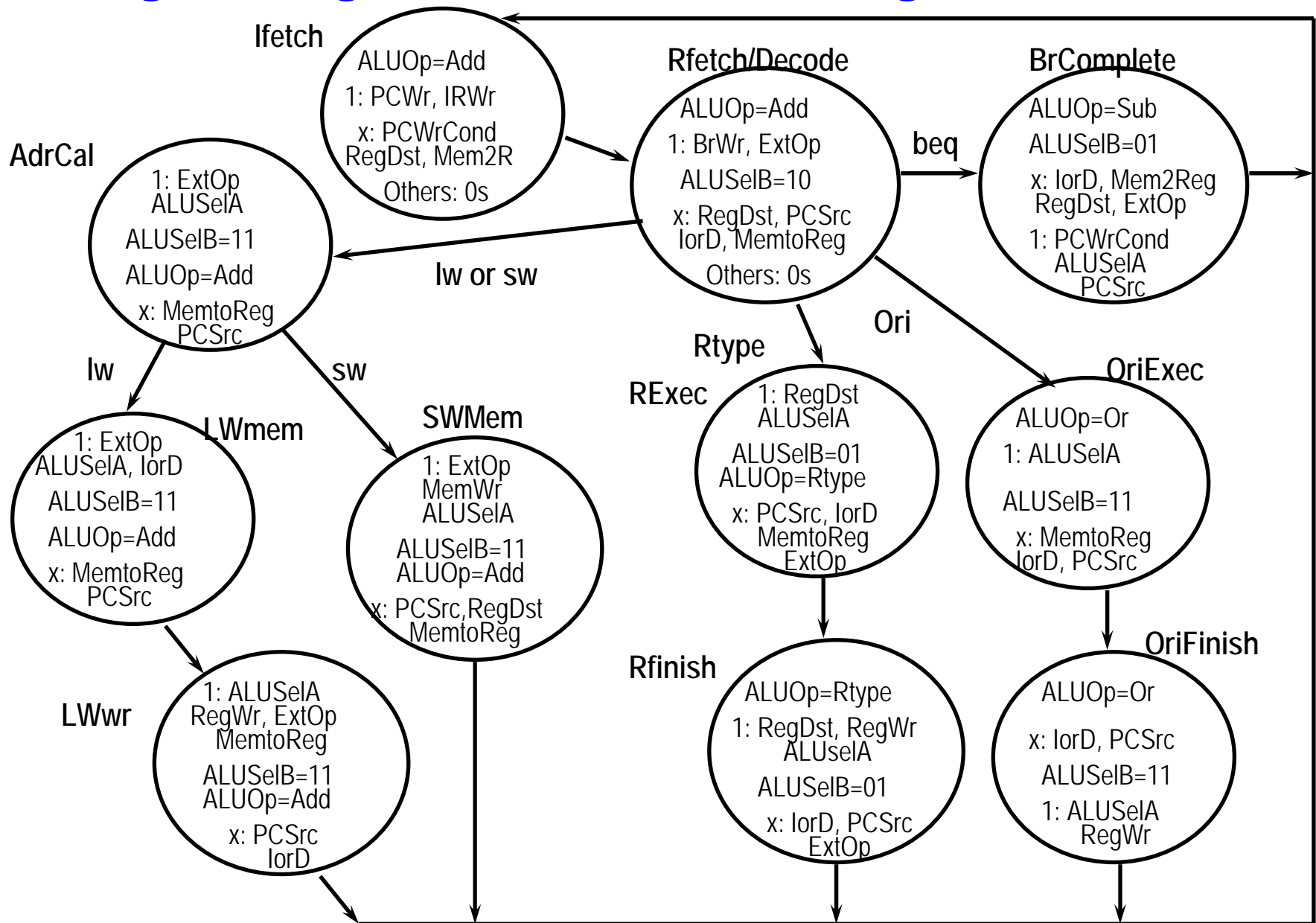Putting it all together: Control State Diagram



The Final Control Path and Data Path

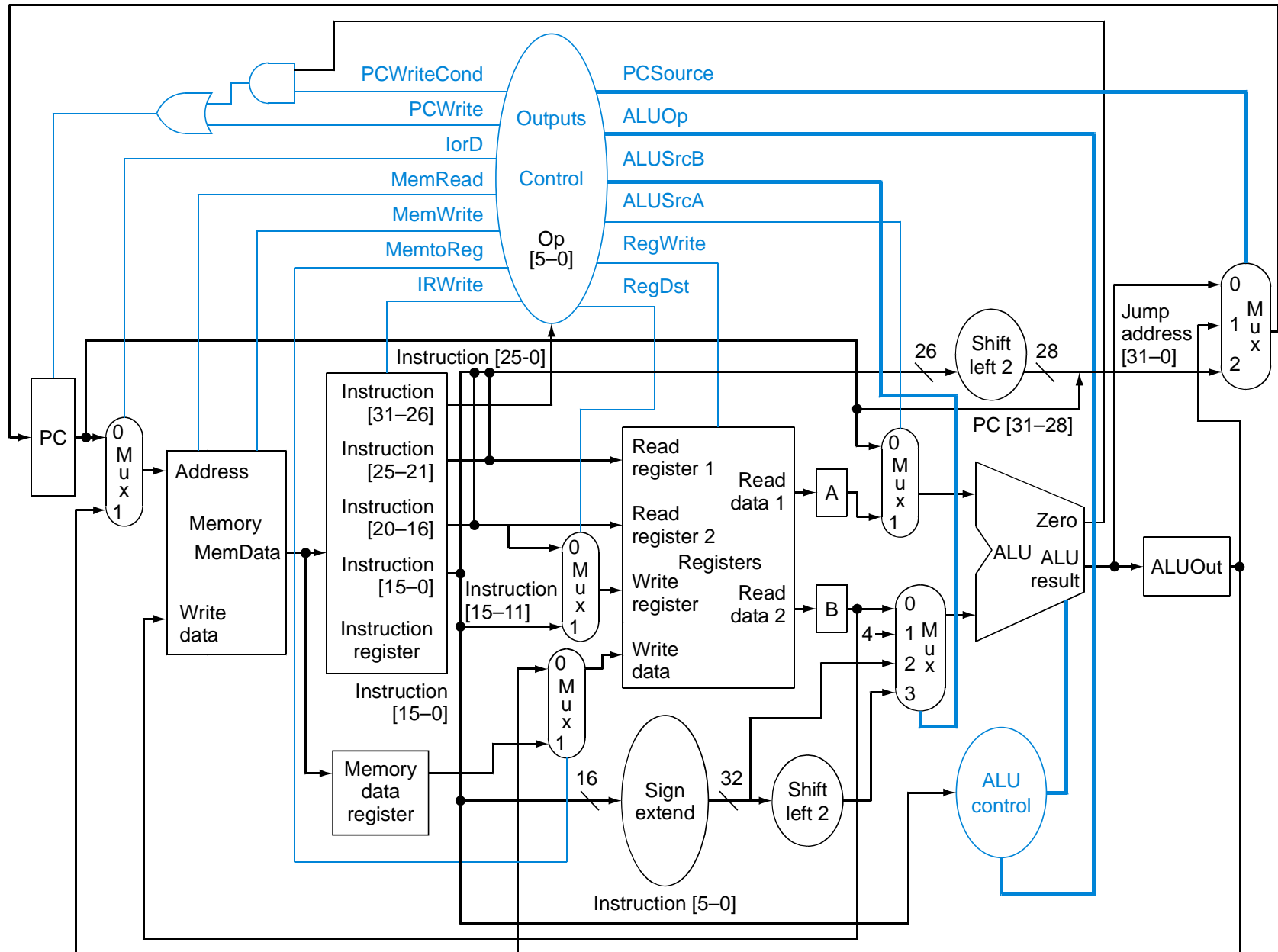

Summary

- **Disadvantages of the Single Cycle Processor**
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- **Multiple Cycle Processor:**
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- **Do NOT confuse Multiple Cycle Processor with Multiple Cycle Delay Path**
 - Multiple Cycle Processor executes each instruction in multiple clock cycles
 - Multiple Cycle Delay Path: a combinational logic path between two storage elements that takes more than one clock cycle to complete
- **It is possible (desirable) to build a MC Processor without MCDP:**
 - Use a register to save a signal's value whenever a signal is generated in one clock cycle and used in another cycle later

Where to get more information?

- **Next two lectures:**
 - **Multiple Cycle Controller: Appendix C of your text book.**
 - **Microprogramming: Section 5.7 (in CD) of your text book.**
- **D. Patterson, “Microprogramming,” *Scientific America*, March 1983.**
- **D. Patterson and D. Ditzel, “The Case for the Reduced Instruction Set Computer,” *Computer Architecture News* 8, 6 (October 15, 1980)**