

Computer Architecture


Ch. 5-2: Designing Single Cycle Control

Spring, 2005

Sao-Jie Chen (csj@cc.ee.ntu.edu.tw)

Recap: The MIPS Instruction Formats

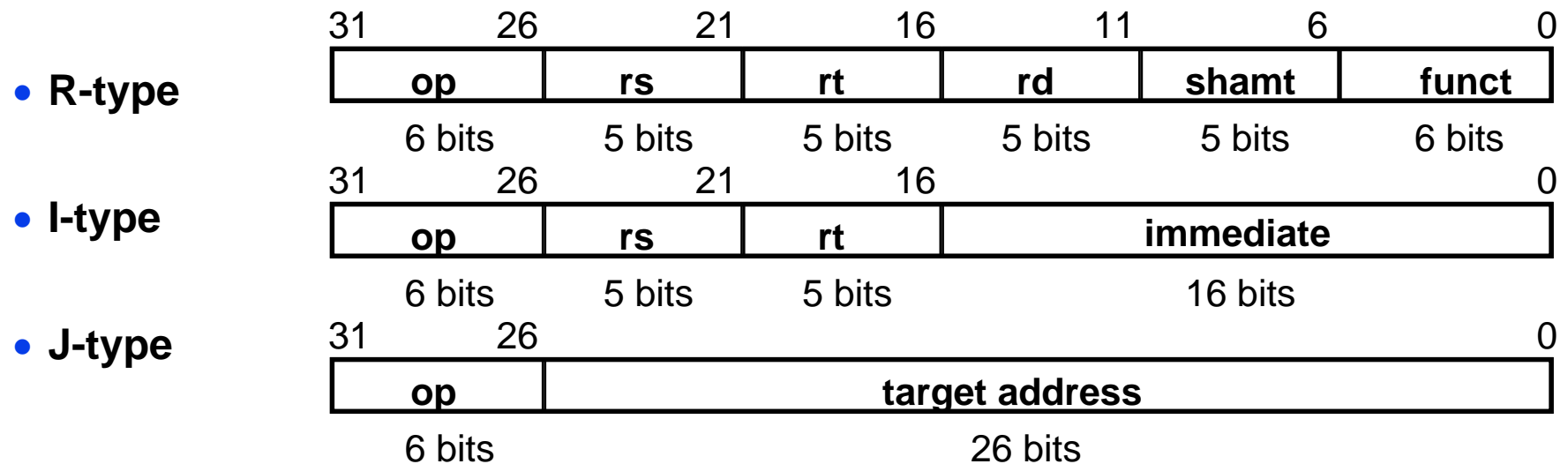- All MIPS instructions are 32 bits long. The three instruction formats:




- The different fields are:
 - op: operation of the instruction
 - rs, rt, rd: the source and destination registers specifier
 - shamt: shift amount
 - funct: selects the variant of the operation in the “op” field
 - address / immediate: address offset or immediate value
 - target address: target address of the jump instruction

Recap: The MIPS Subset


- **ADD and subtract**

- add rd, rs, rt
- sub rd, rs, rt

 

- **OR Imm:**

- ori rt, rs, imm16

 

- **LOAD and STORE**


- lw rt, rs, imm16
- sw rt, rs, imm16

- **BRANCH:**

- beq rs, rt, imm16


- **JUMP:**

- j target

 


Recap: A Single Cycle Datapath

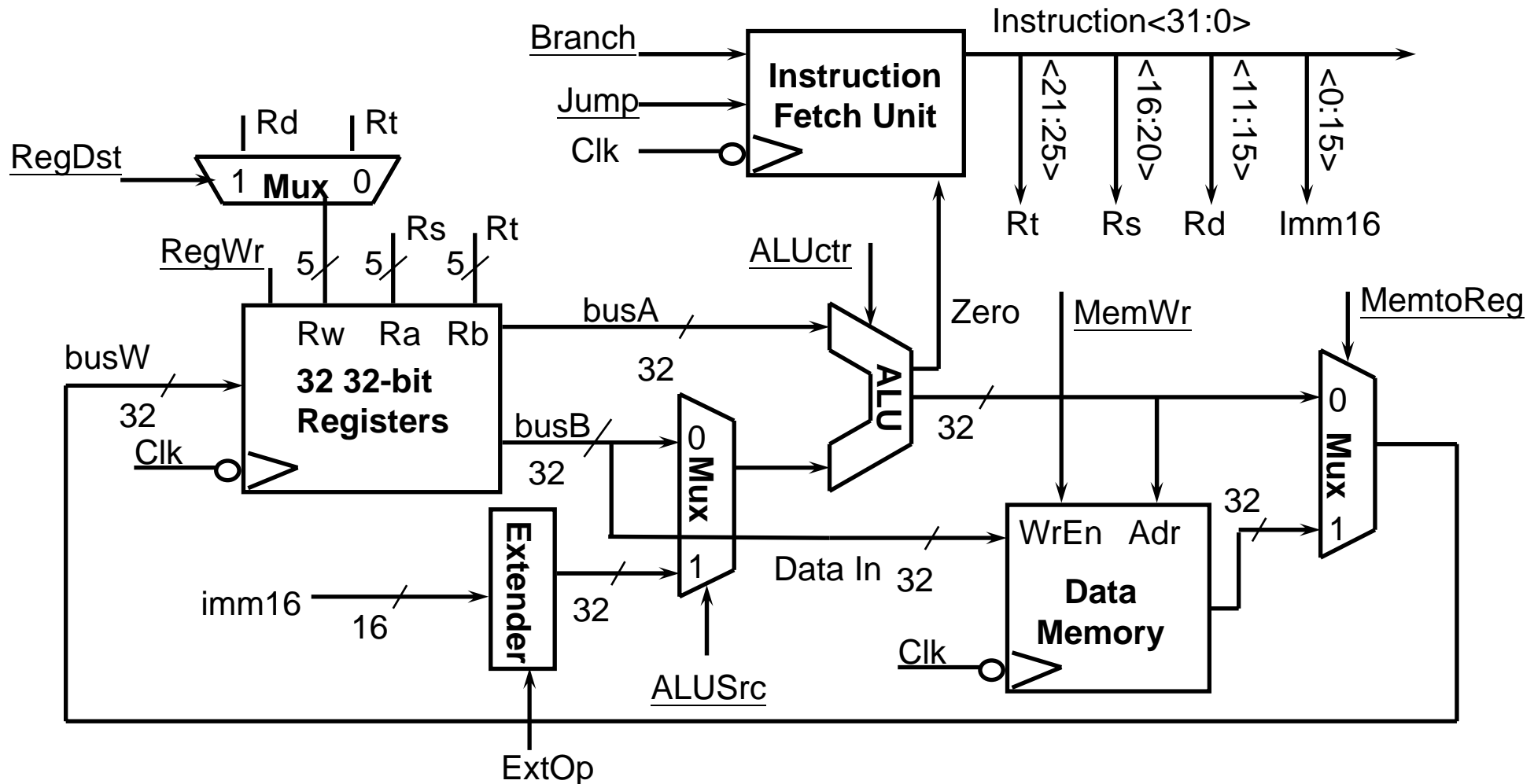- We have everything except control signals (underline)
 - Today's lecture will show you how to generate the control signals



The Big Picture: Where are We Now?

 - The Five Classic Components of a Computer



- Today's Topic: Designing the **Control** for the Single Cycle Datapath

Control

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction
- Example:

add \$8, \$17, \$18

Instruction Format:

000000	10001	10010	01000	00000	100000
op	rs	rt	rd	shamt	funct

- ALU's operation based on instruction type and function code

Control

- e.g., what should the ALU do with this instruction
- Example: **lw \$1, 100(\$2)**

35	2	1	100
-----------	----------	----------	------------


op	rs	rt	16 bit offset
-----------	-----------	-----------	----------------------

- ALU control input

0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

- Why is the code for subtract **0110** and not **0011**?

RTL: The ADD Instruction

 

- **add rd, rs, rt**

- mem[PC]

Fetch the instruction from memory

- $R[rd] \leftarrow R[rs] + R[rt]$


The actual operation

- $PC \leftarrow PC + 4$


Calculate the next instruction's address

Instruction Fetch Unit at the Beginning of Add / Subtract

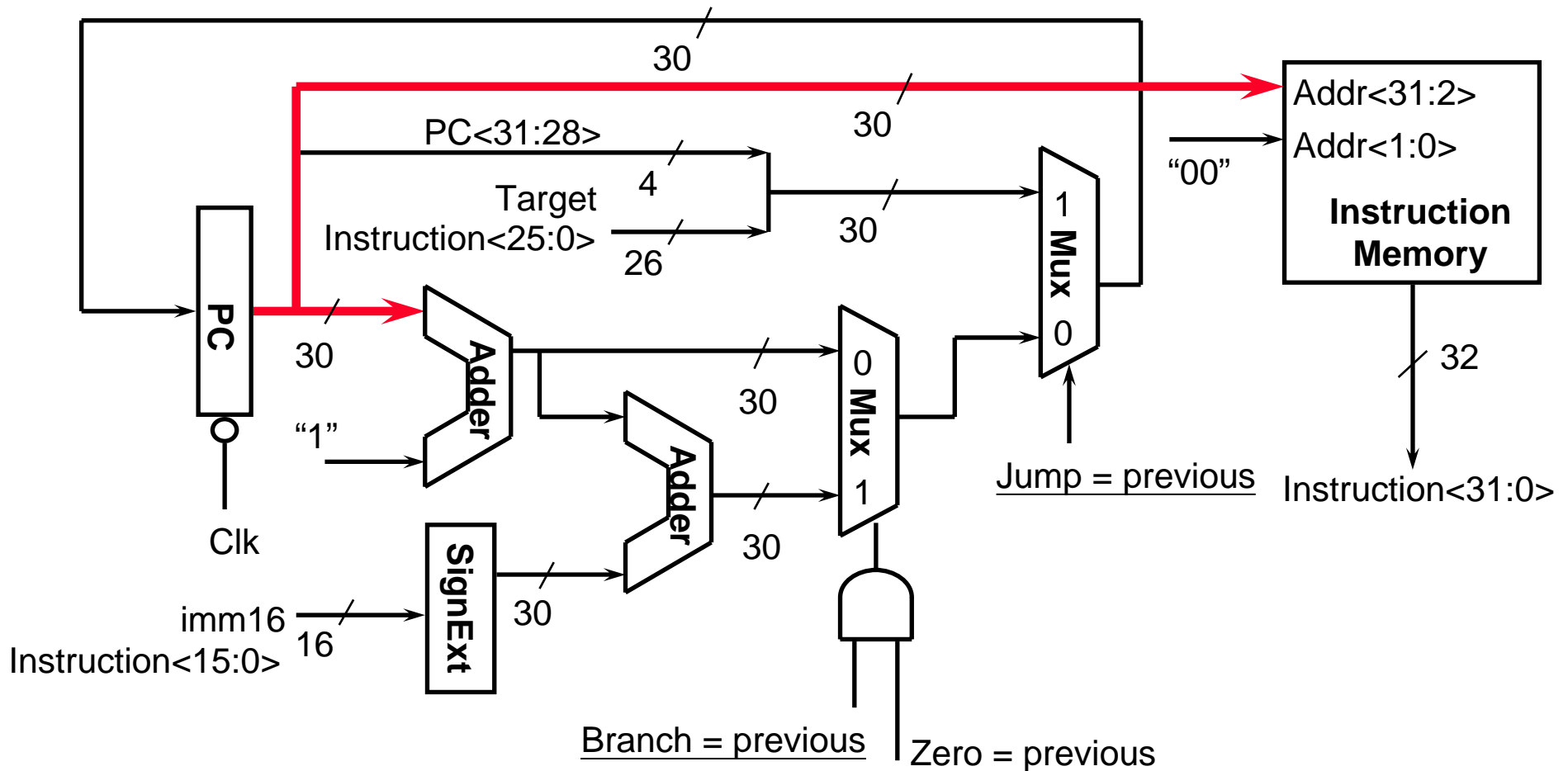
- Fetch the instruction from Instruction memory: **Instruction** \leftarrow **mem[PC]**
- This is the same for all instructions



 The Single Cycle Datapath during Add and Subtract




• $R[rd] \leftarrow R[rs] + / - R[rt]$

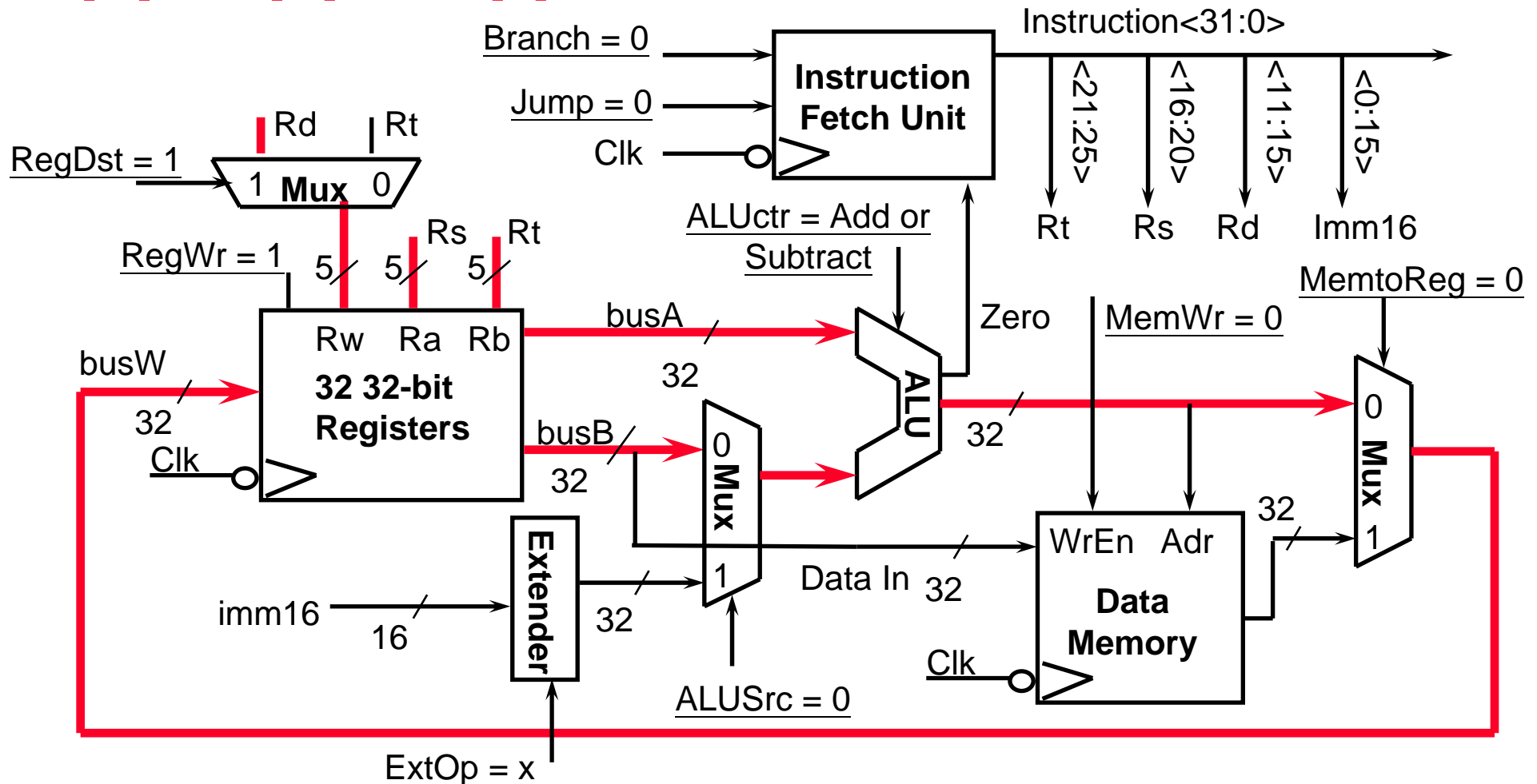


Instruction Fetch Unit at the End of Add and Subtract

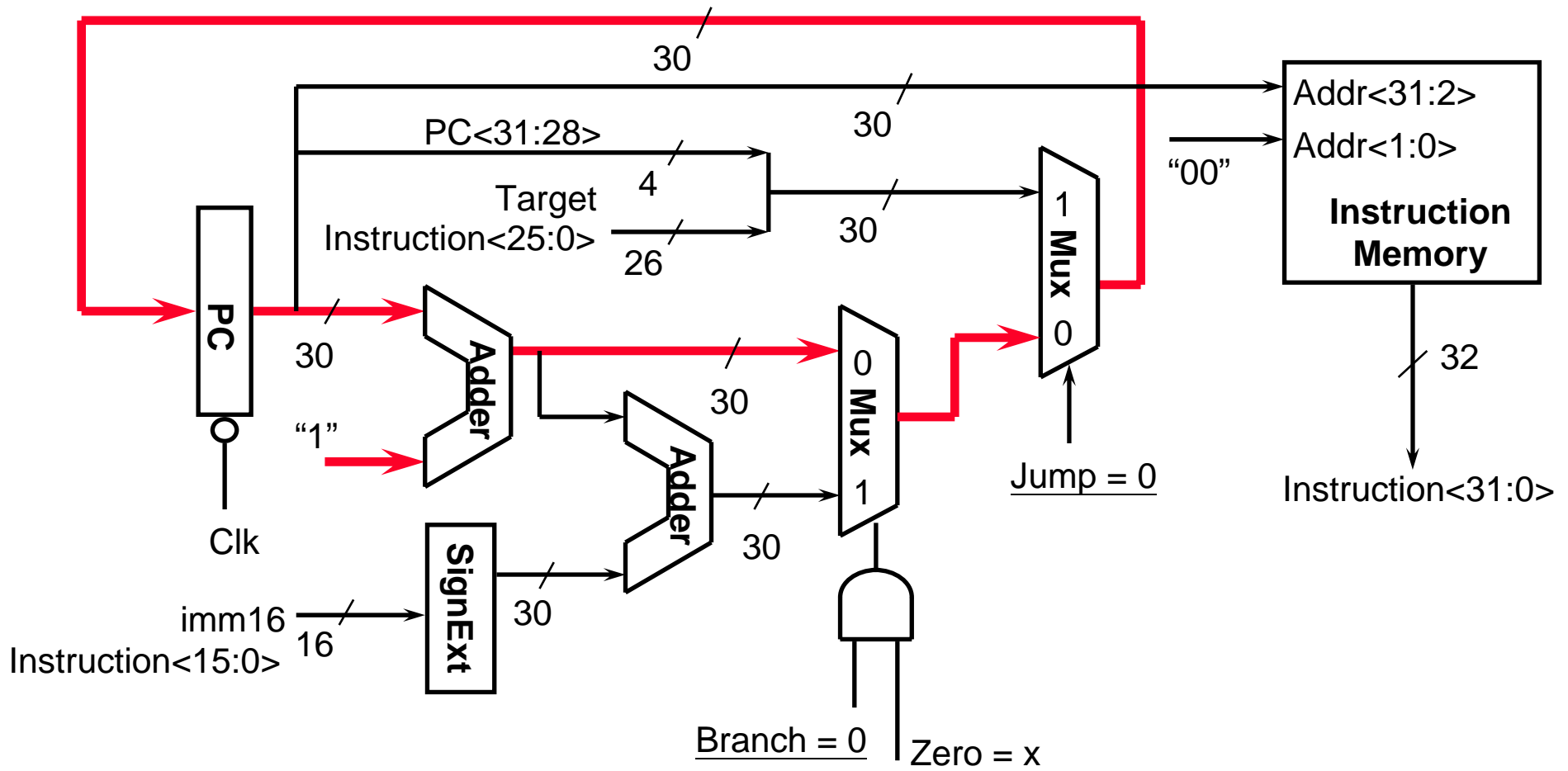
- **PC \leftarrow PC + 4**
 - This is the same for all instructions except: Branch and Jump



 
The Single Cycle Datapath during Or Immediate



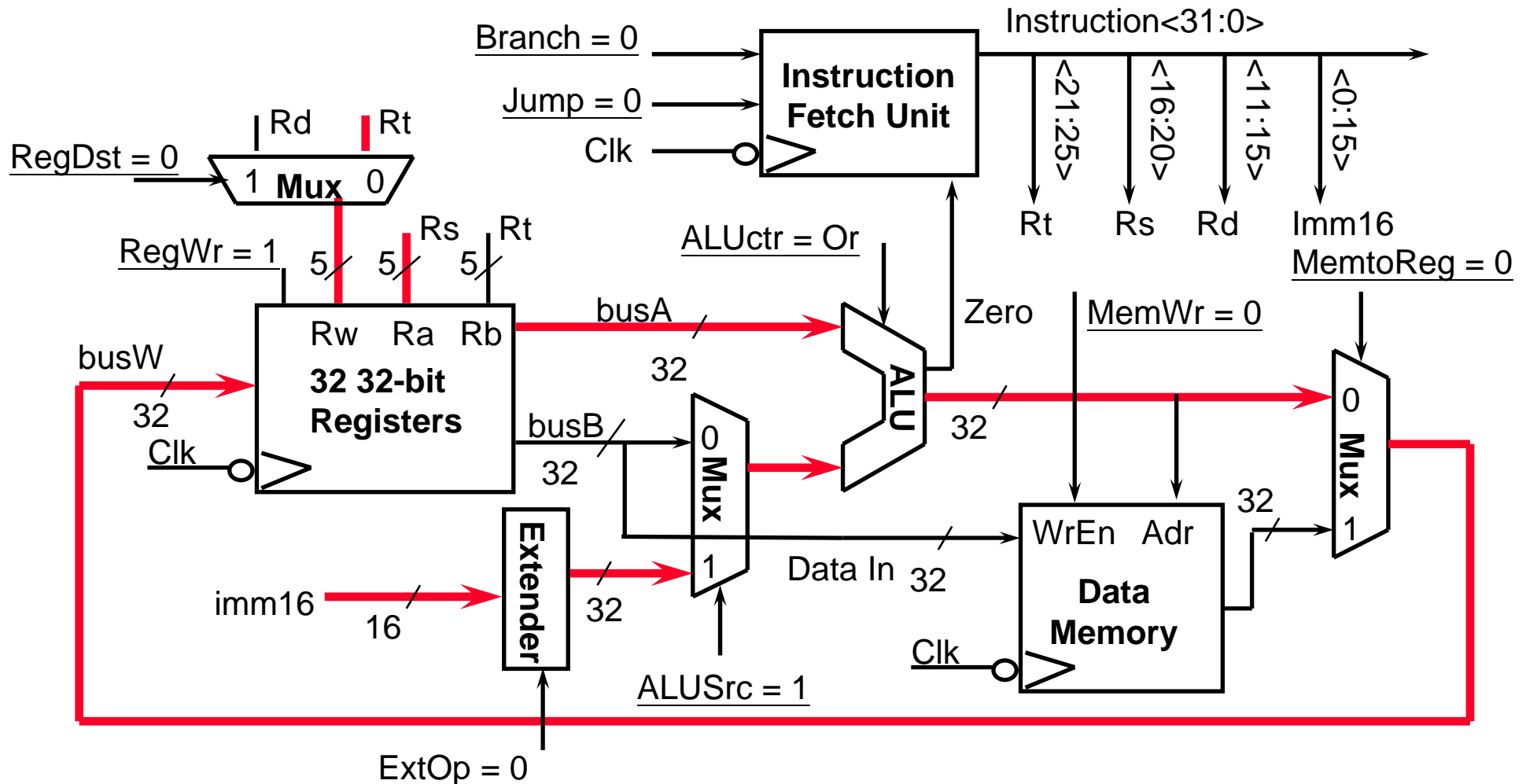
- $R[rt] \leftarrow R[rs] \text{ or } \text{ZeroExt}(\text{imm16})$




The Single Cycle Datapath during Load

 

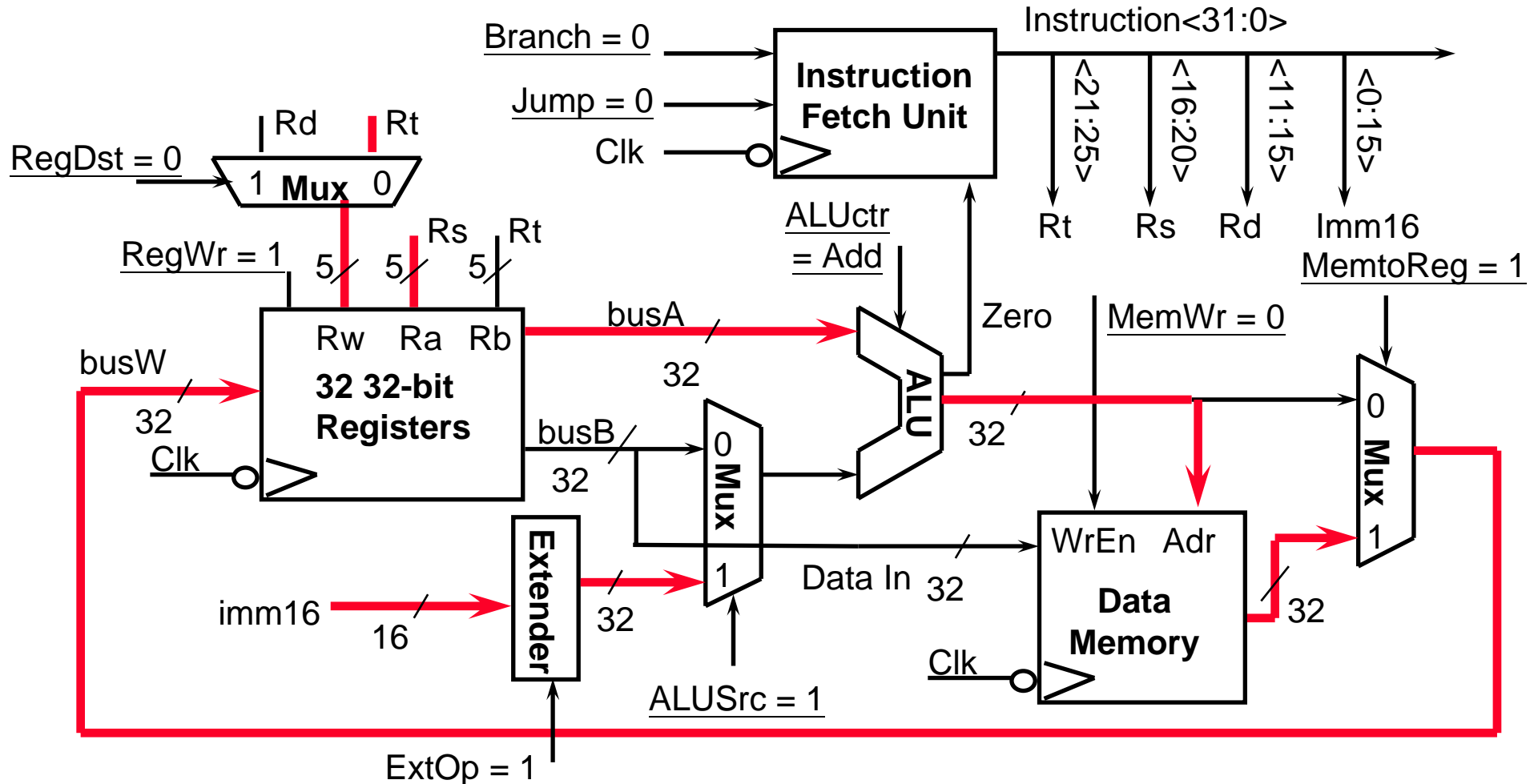
- $R[rt] \leftarrow \text{Data Memory}[R[rs] + \text{SignExt}(\text{imm16})]$




The Single Cycle Datapath during Store

 

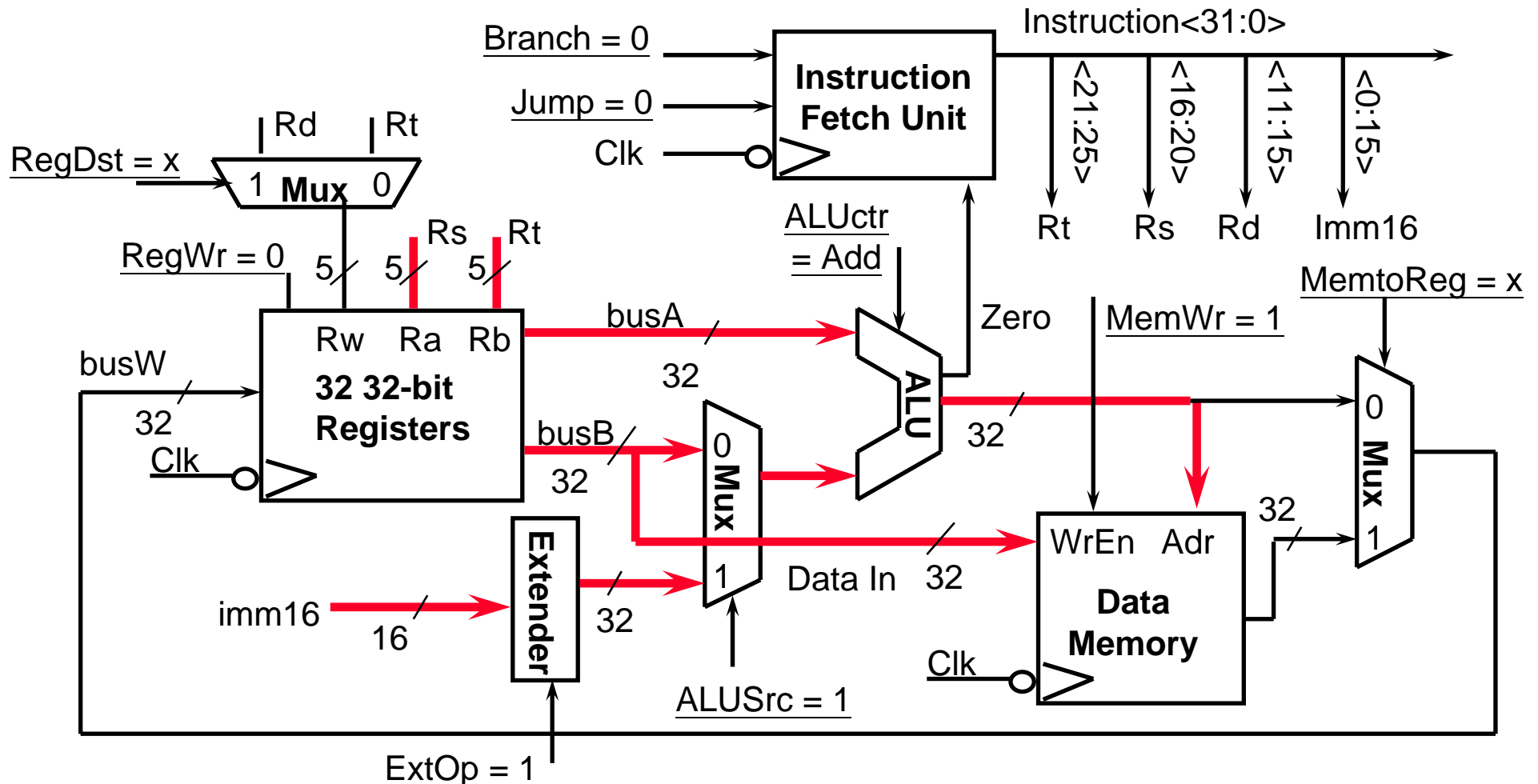
- **Data Memory [R[rs] + SignExt(imm16)] <- R[rt]**




The Single Cycle Datapath during Branch

 

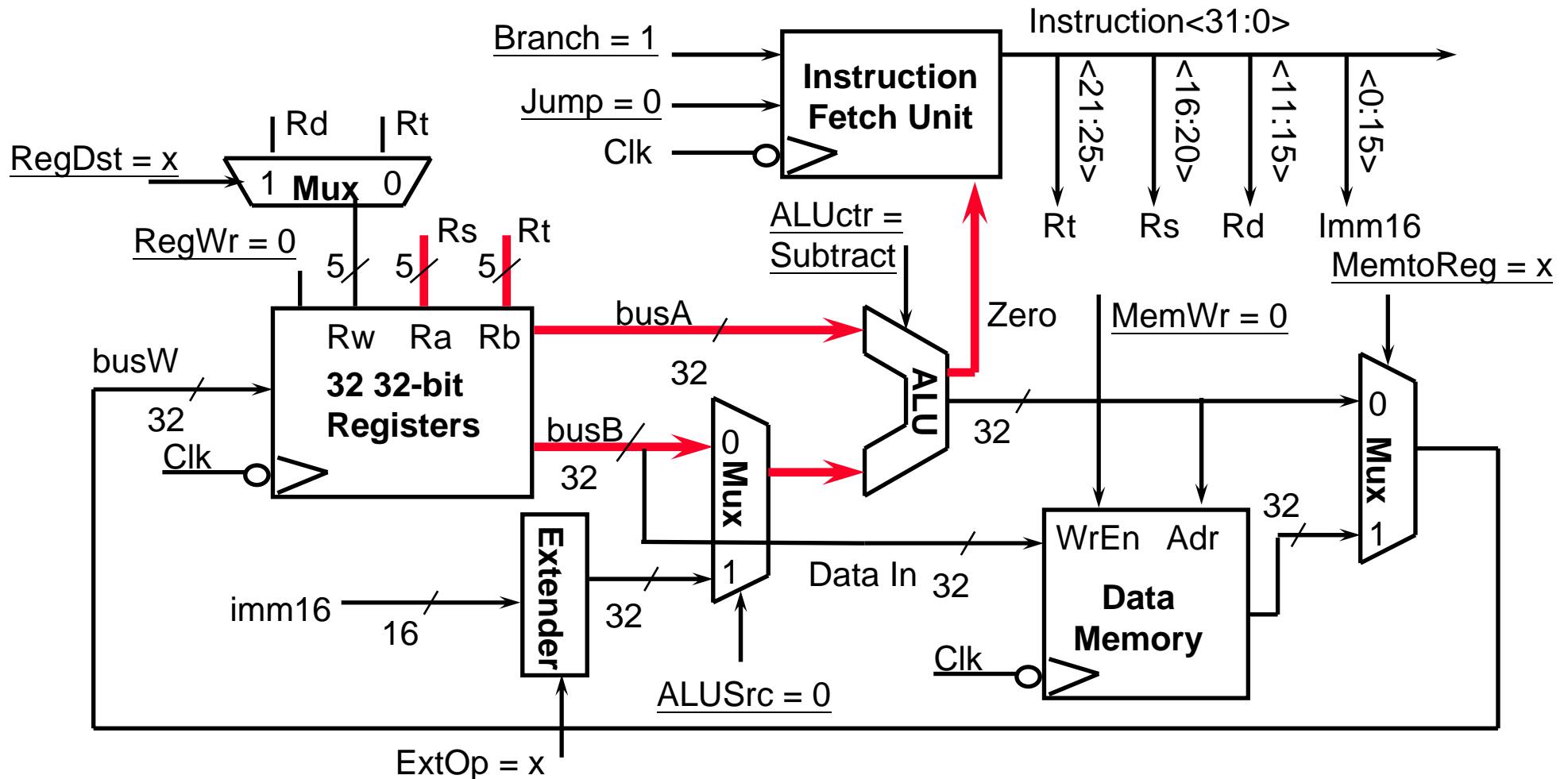
- if (R[rs] - R[rt] == 0) then Zero <- 1; else Zero <- 0



 Instruction Fetch Unit at the End of Branch



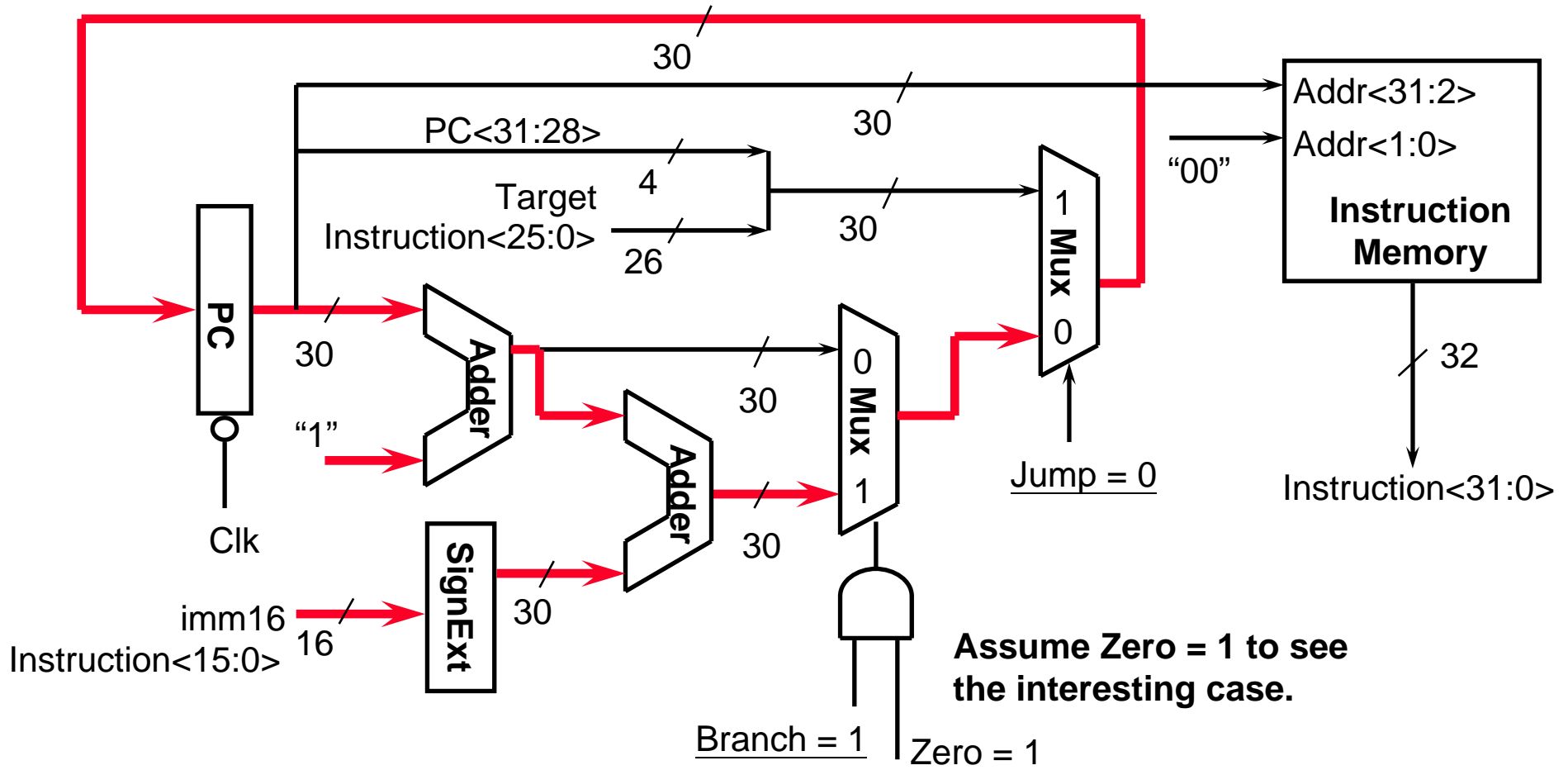
- if (Zero == 1) then $PC = PC + 4 + \text{SignExt}(\text{imm16}) * 4$; else $PC = PC + 4$



The Single Cycle Datapath during Jump



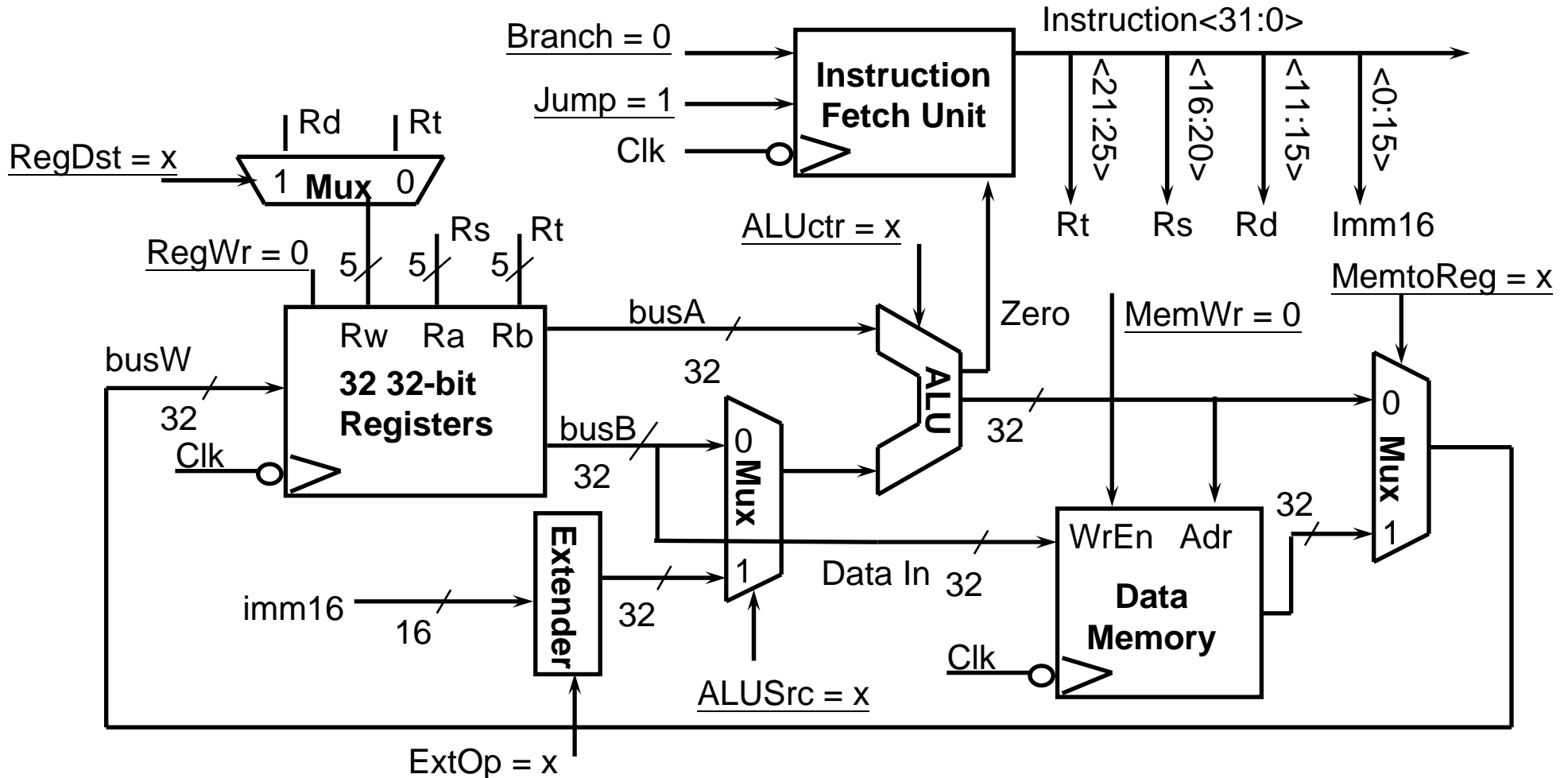
- **Nothing to do!** Make sure control signals are set correctly!



Instruction Fetch Unit at the End of Jump



- `PC <- PC<31:28> concat target<25:0>`

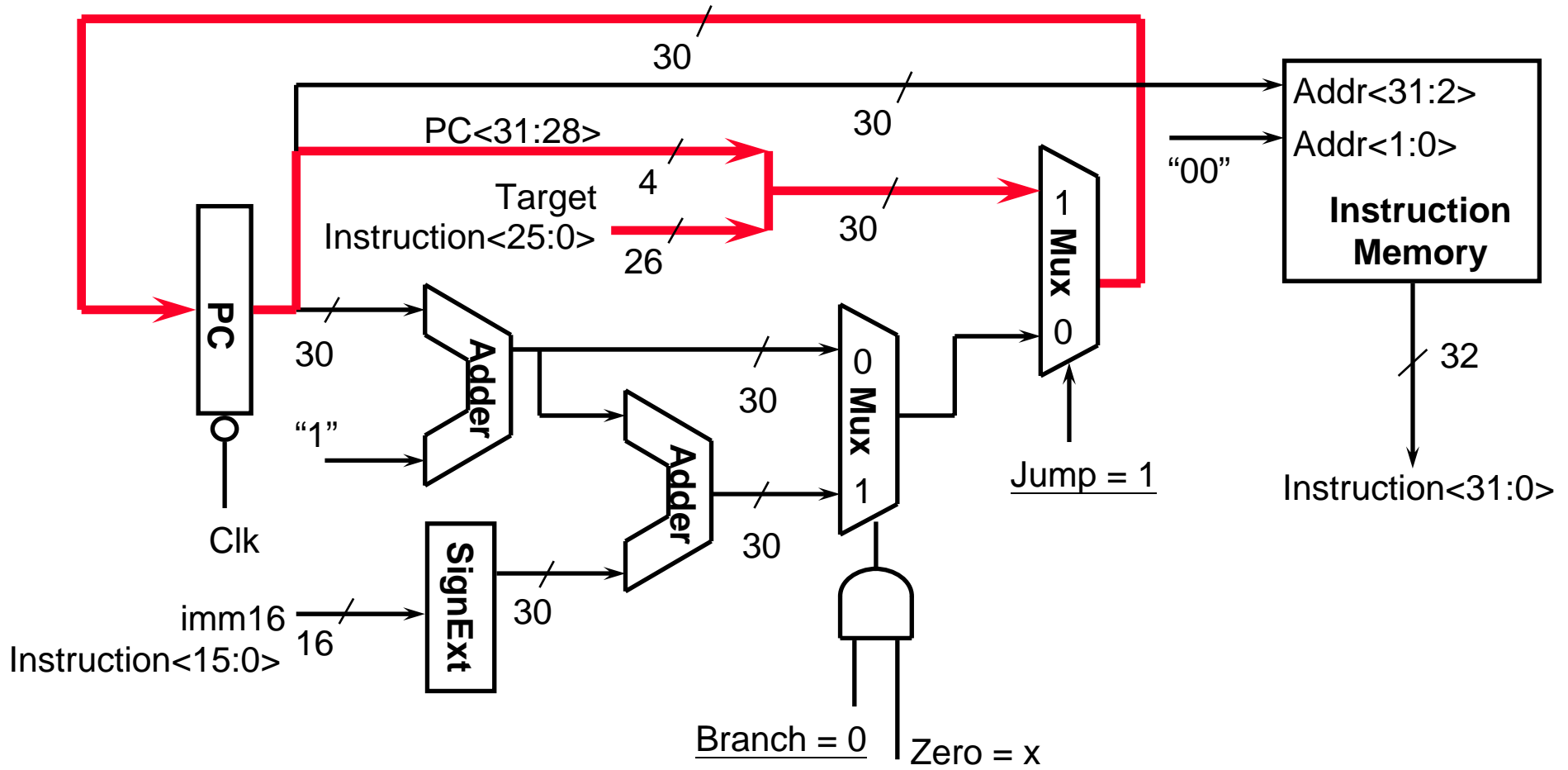

A Summary of the Control Signals


See Appendix B

	func	10 0000	10 0010	We Don't Care :-)				
	op	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
		add	sub	ori	lw	sw	beq	jump
RegDst		1	1	0	0	x	x	x
ALUSrc		0	0	1	1	1	0	x
MemtoReg		0	0	0	1	x	x	x
RegWrite		1	1	1	1	0	0	0
MemWrite		0	0	0	0	1	0	0
Branch		0	0	0	0	0	1	0
Jump		0	0	0	0	0	0	1
ExtOp		x	x	0	1	1	x	x
ALUctr<2:0>		Add	Subtract	Or	Add	Add	Subtract	xxx


	31	26	21	16	11	6	0						
R-type	op		rs		rt		rd		shamt		funct		add, sub
I-type	op		rs		rt		immediate						ori, lw, sw, beq
J-type	op		target address										jump

The Concept of Local Decoding

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUOp<N:0>	"R-type"	Or	Add	Add	Subtract	xxx

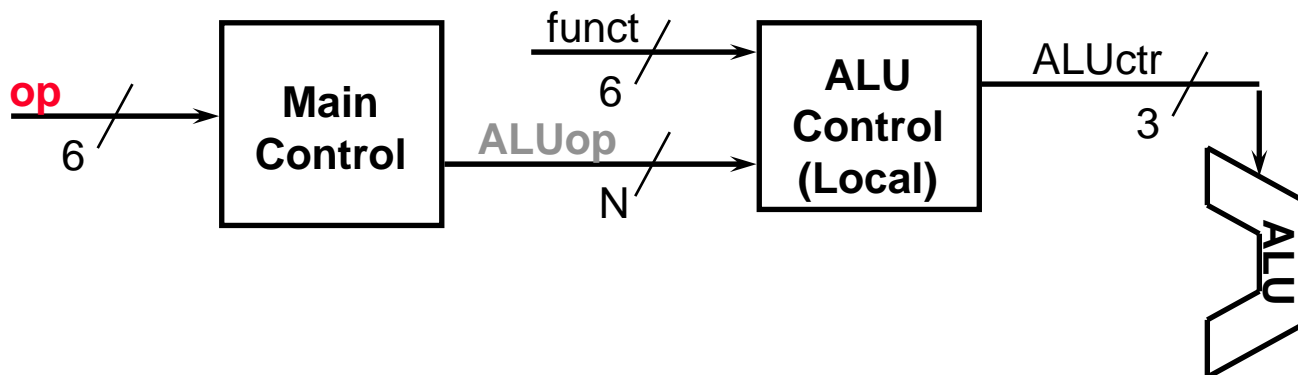


The Encoding of ALUop

 


- In this exercise, ALUop has to be 2 bits wide to represent:
 - (1) “R-type” instructions
 - “I-type” instructions that require the ALU to perform:
 - ⇒ (2) Or, (3) Add, and (4) Subtract
- To implement the full MIPS ISA, **ALUop** has to be **3 bits** to represent:
 - (1) “R-type” instructions
 - “I-type” instructions that require the ALU to perform:
 - ⇒ (2) Or, (3) Add, (4) Subtract, and (5) And (Example: andi)

	R-type	ori	lw	sw	beq	jump
ALUop (Symbolic)	“R-type”	Or	Add	Add	Subtract	xxx
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

The Decoding of the “Funct” Field

 


	R-type	ori	lw	sw	beq	jump
ALUOp (Symbolic)	“R-type”	Or	Add	Add	Subtract	xxx
ALUOp<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

 

funct<5:0>	Instruction Operation
10 0000	add
10 0010	subtract
10 0100	and
10 0101	or
10 1010	set-on-less-than

Recall ALU Homework (also P. 353 text):

 

ALUctr<2:0>	ALU Operation
000	And
001	Or
010	Add
110	Subtract
111	Set-on-less-than

The Truth Table for ALUctr

ALUOp (Symbolic)	R-type	ori	lw	sw	beq
	"R-type"	Or	Add	Add	Subtract
ALUOp<2:0>	1 00	0 10	0 00	0 00	0 01

funct<3:0>	Instruction Op.
0000	add
0010	subtract
0100	and
0101	or
1010	set-on-less-than

ALUOp			funct				ALU Operation	ALUctr		
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>		bit<2>	bit<1>	bit<0>
0	0	0	x	x	x	x	Add	0	1	0
0	x	1	x	x	x	x	Subtract	1	1	0
0	1	x	x	x	x	x	Or	0	0	1
1	x	x	0	0	0	0	Add	0	1	0
1	x	x	0	0	1	0	Subtract	1	1	0
1	x	x	0	1	0	0	And	0	0	0
1	x	x	0	1	0	1	Or	0	0	1
1	x	x	1	0	1	0	Set on <	1	1	1

Control

- Must describe hardware to compute 3-bit ALU control input
 - given instruction type
 - 00 = lw, sw
 - 01 = beq,
 - 11 = arithmetic
 - function code for arithmetic
- > **ALUOp**
computed from instruction type
- Describe it using a truth table (can turn into gates):

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

The Logic Equation for ALUctr<2>

ALUop			funct				ALUctr<2>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	x	1	x	x	x	x	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

This makes funct<3> a don't care

- $ALUctr<2> = !ALUop<2> \& ALUop<0> +$
 $ALUop<2> \& !funct<2> \& funct<1> \& !funct<0>$

The Logic Equation for ALUctr<1>

ALUop			funct				ALUctr<1>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	0	0	x	x	x	x	1
0	x	1	x	x	x	x	1
1	x	x	0	0	0	0	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

- $$\text{ALUctr}<1> = \neg \text{ALUop}<2> \ \& \ \neg \text{ALUop}<1> +$$


$$\text{ALUop}<2> \ \& \ \neg \text{funct}<2> \ \& \ \neg \text{funct}<0>$$

The Logic Equation for ALUctr<0>

ALUop			funct				ALUctr<0>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	1	x	x	x	x	x	1
1	x	x	0	1	0	1	1
1	x	x	1	0	1	0	1


- $ALUctr<0> = !ALUop<2> \& ALUop<1>$
 $+ ALUop<2> \& !funct<3> \& funct<2> \& !funct<1> \& funct<0>$
 $+ ALUop<2> \& funct<3> \& !funct<2> \& funct<1> \& !funct<0>$

The ALU Control Block

 


- $ALUctr<2> = !ALUop<2> \& ALUop<0> +$
 $ALUop<2> \& !funct<2> \& funct<1> \& !funct<0>$
- $ALUctr<1> = !ALUop<2> \& !ALUop<1> +$
 $ALUop<2> \& !funct<2> \& !funct<0>$
- $ALUctr<0> = !ALUop<2> \& ALUop<1>$
 $+ ALUop<2> \& !funct<3> \& funct<2> \& !funct<1> \& funct<0>$
 $+ ALUop<2> \& funct<3> \& !funct<2> \& funct<1> \& !funct<0>$

The “Truth Table” for the Main Control

 

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUop (Symbolic)	“R-type”	Or	Add	Add	Subtract	xxx
ALUop <2>	1	0	0	0	0	x
ALUop <1>	0	1	0	0	0	x
ALUop <0>	0	0	0	0	1	x

Control

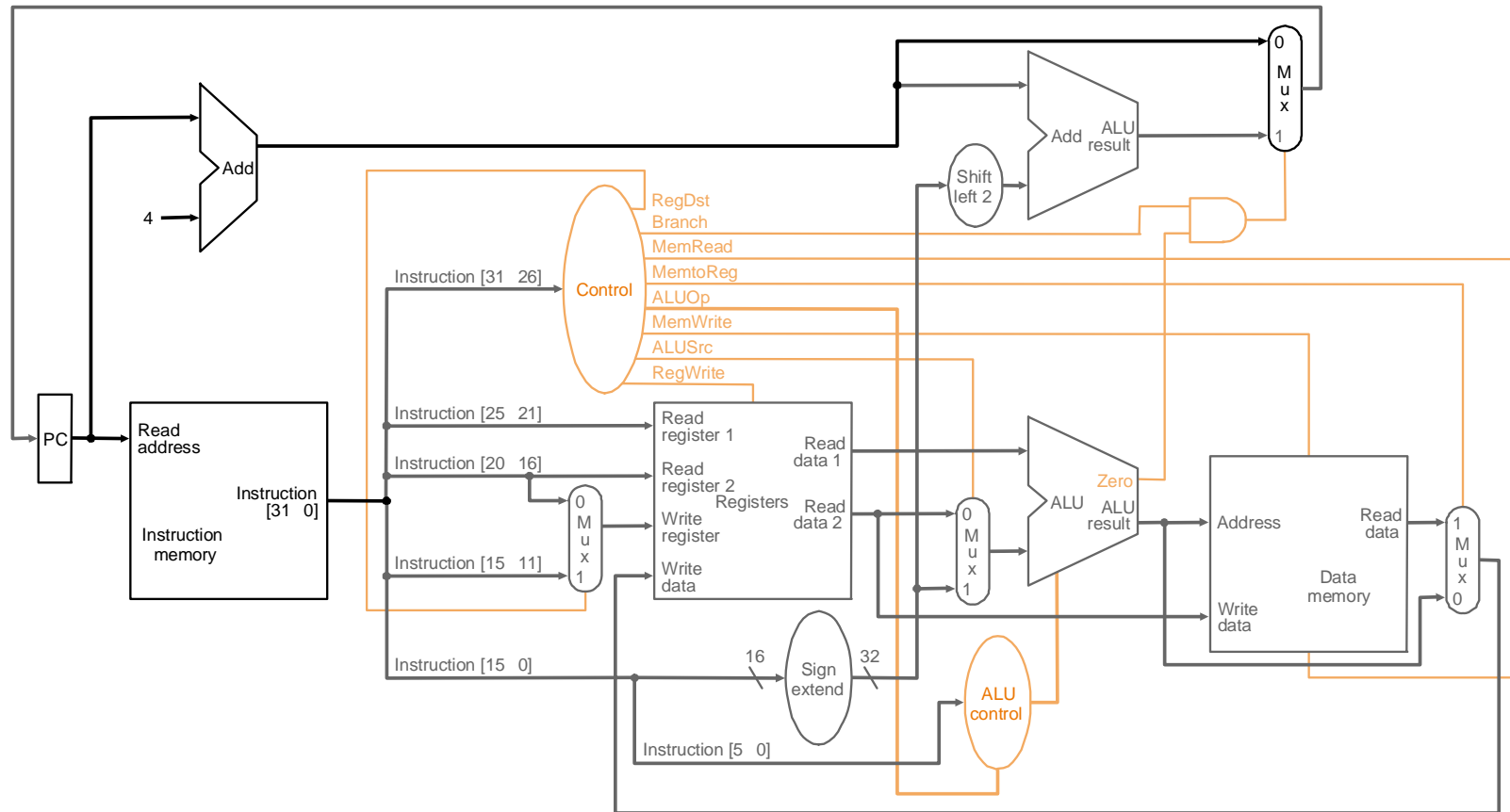

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

The “Truth Table” for RegWrite


op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegWrite	1	1	1	x	x	x

- **RegWrite = R-type + ori + lw**


= !op<5> & !op<4> & !op<3> & !op<2> & !op<1> & !op<0> (R-type)

+ !op<5> & !op<4> & op<3> & op<2> & !op<1> & op<0> (ori)

 + op<5> & !op<4> & !op<3> & !op<2> & op<1> & op<0> (lw)




PLA Implementation of the Main Control

 

Building Control Path from True Table


Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Inputs

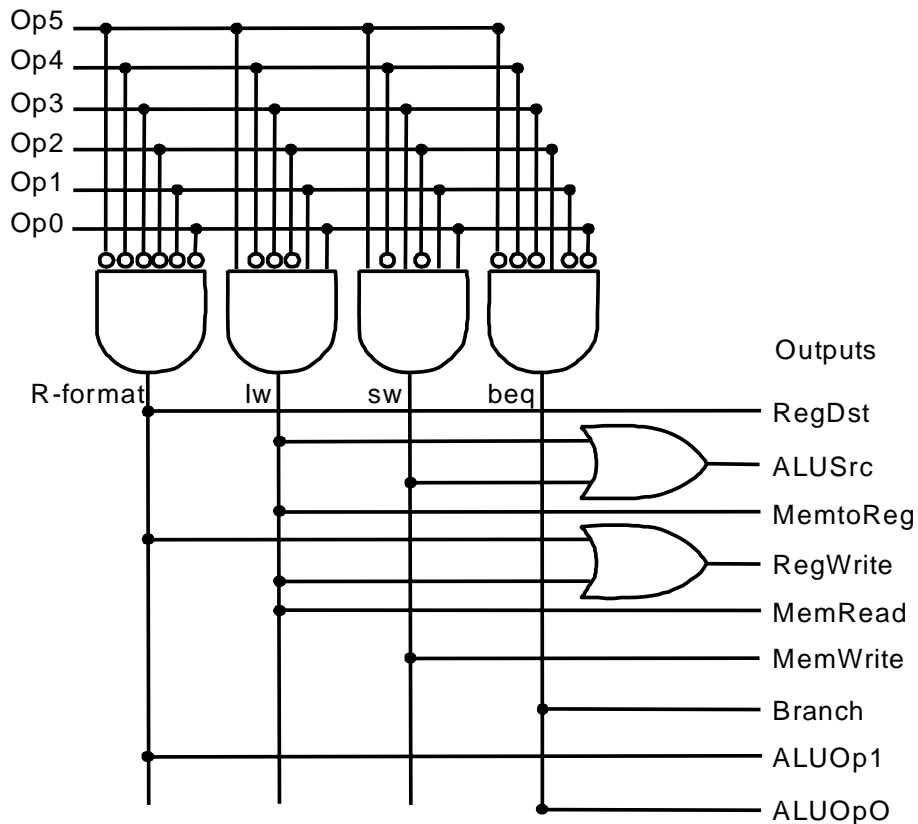


Building Control Path from True Table

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

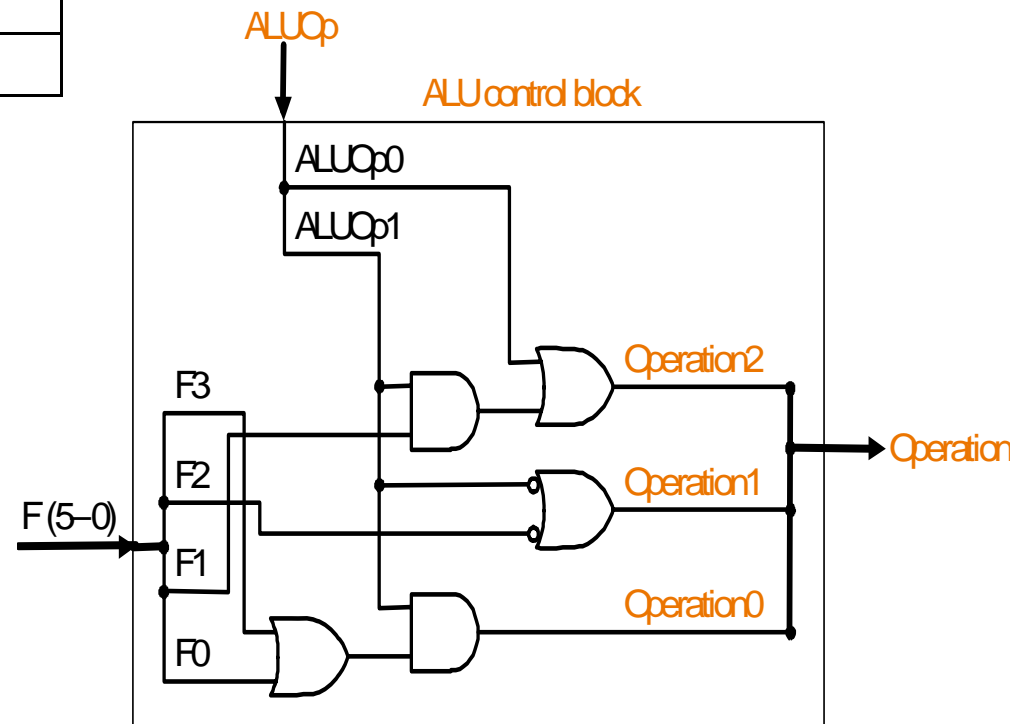


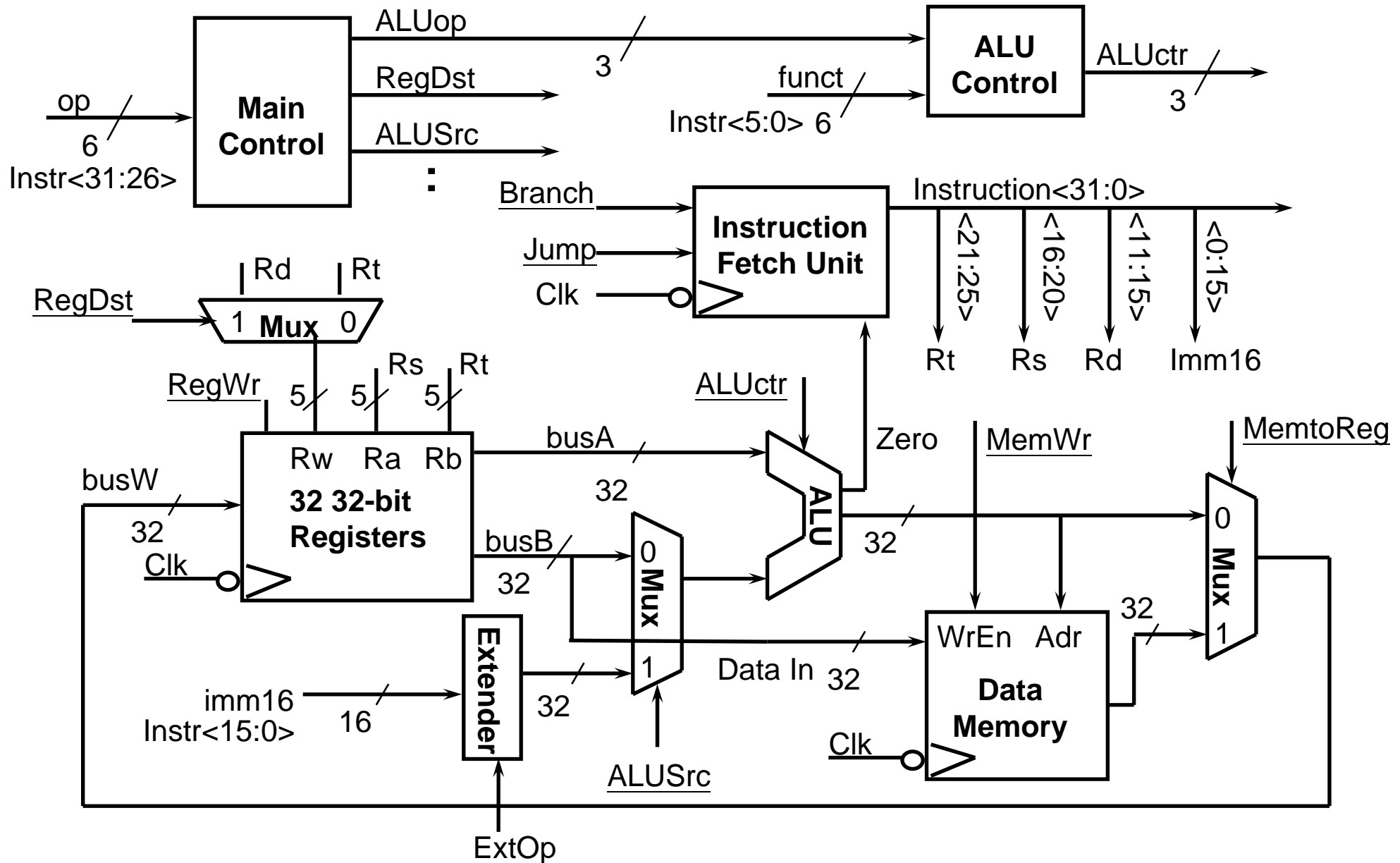Putting it All Together: A Single Cycle Processor



Single Cycle Implementation

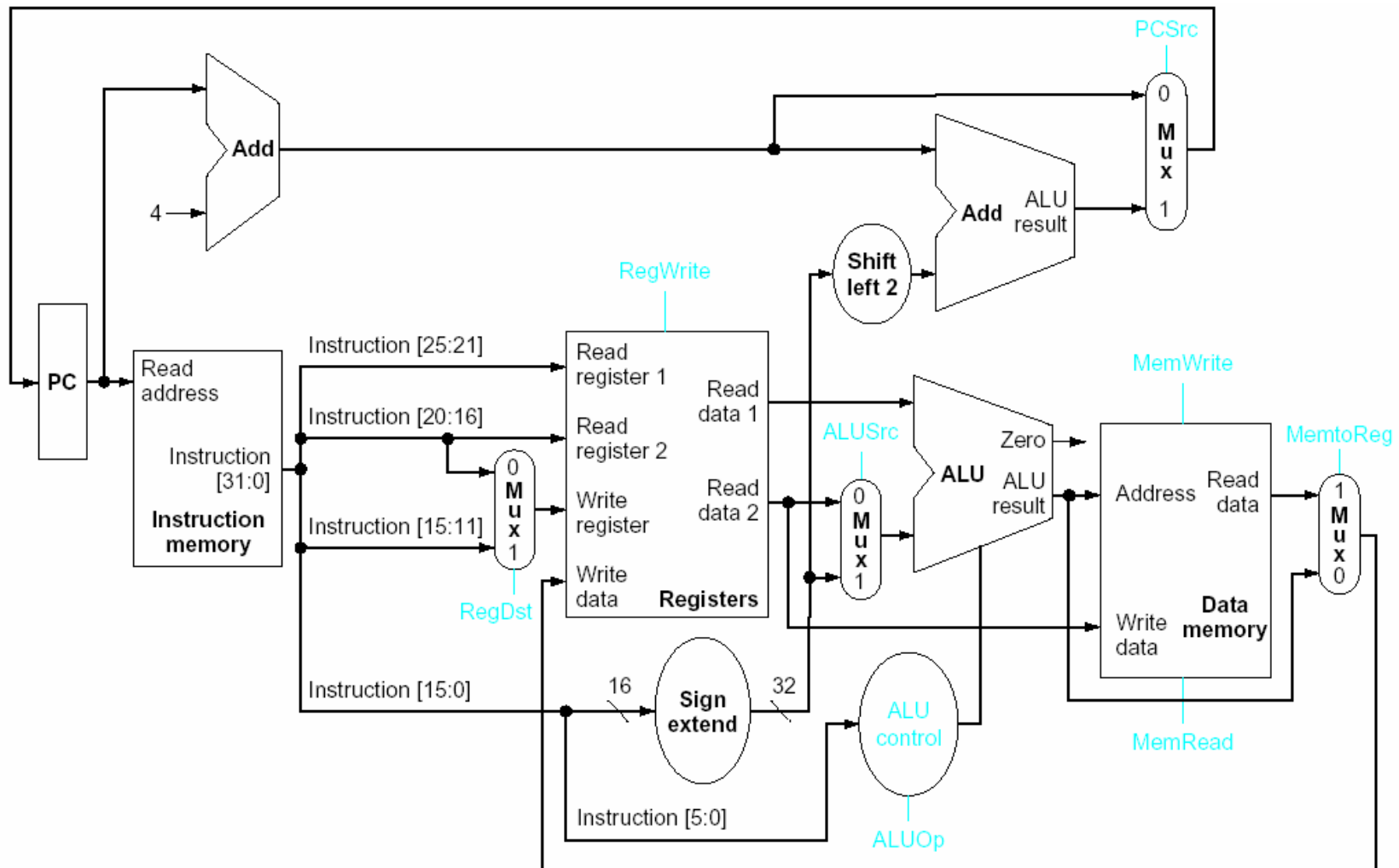- Calculate cycle time assuming negligible delays except:
 - memory (200ps), ALU and adders (100ps), register file access (50ps)




Where we are headed

- **Single Cycle Problems:**

- what if we had a more complicated instruction like floating point?
- wasteful of area

- **One Solution:**

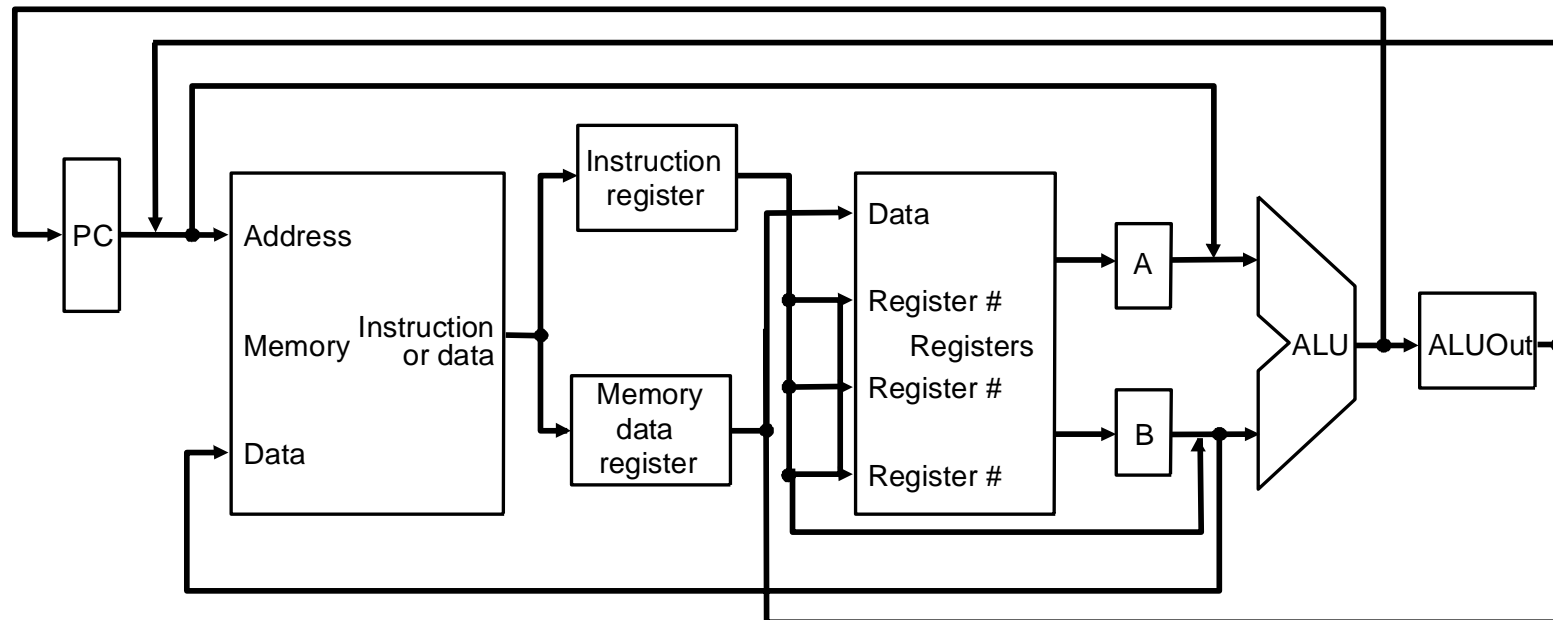- use a “smaller” cycle time
- have different instructions take different numbers of cycles
- a “multicycle” datapath:



How is this Different from a Real MIPS Processor?

- The effect of load in a real MIPS Processor is **delayed**:

⇒ lw	\$1, 100(\$2)	// Load Register R1
⇒ add	\$3, \$1, \$0	// Move “old” R1 into R3
⇒ add	\$4, \$1, \$0	// Move “new” R1 into R4

- The effect of load in our single cycle processor is **NOT** delayed

⇒ lw	\$1, 100(\$2)	// Load Register R1
⇒ add	\$3, \$1, \$0	// Move “new” R1 into R3

- The effect of branch and jump in a real MIPS Processor is **delayed**:

⇒ Instruction Address: 0x00	j 1000
⇒ Instruction Address: 0x04	add \$1, \$2, \$3
⇒ Instruction Address: 0x1000	sub \$1, \$2, \$3

- Branch and jump in our single cycle processor is **NOT** delayed

⇒ Instruction Address: 0x00	j 1000
⇒ Instruction Address: 0x1000	sub \$1, \$2, \$3

Drawback of this Single Cycle Processor

- **Long cycle time:**
 - **Cycle time must be long enough for the load instruction:**
PC's Clock -to-Q +
Instruction Memory Access Time +
Register File Access Time +
ALU Delay (address calculation) +
Data Memory Access Time +
Register File Setup Time +
Clock Skew
- **Cycle time is much longer than needed for all other instructions**

Where to get more information?

- Chapter 5 of your text book:
 - David Patterson and John Hennessy, *Computer Organization & Design: The Hardware / Software Interface*, 3rd Ed., ©2005, Morgan Kaufman Publishers.
- One of the best PhD thesis on processor design:
 - Manolis Katevenis, *Reduced Instruction Set Computer Architecture for VLSI*, Ph.D. Dissertation, EECS, U C Berkeley, 1982.
- For a reference on the MIPS architecture:
 - Gerry Kane, *MIPS RISC Architecture*, ©1992, Prentice Hall.